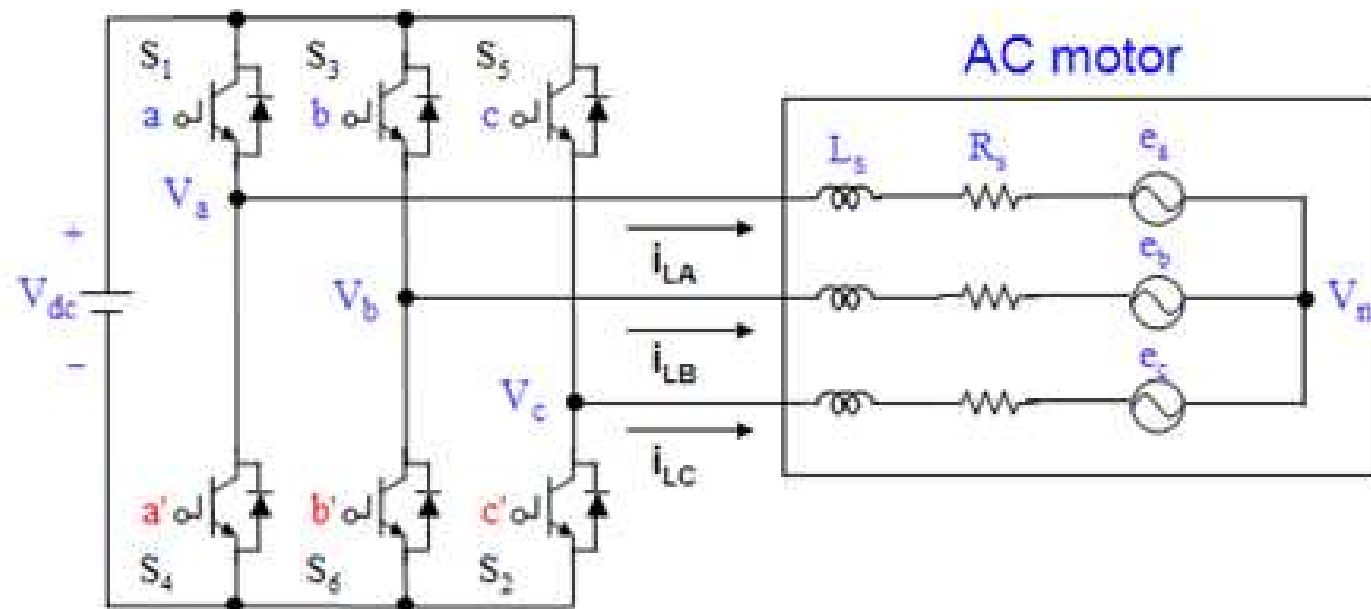


Space Vector PWM

➤ Output voltages of three-phase inverter (1)




where, upper transistors: S_1, S_3, S_5
lower transistors: S_4, S_6, S_2
switching variable vector: a, b, c


Space Vector PWM

Output voltages of three-phase inverter

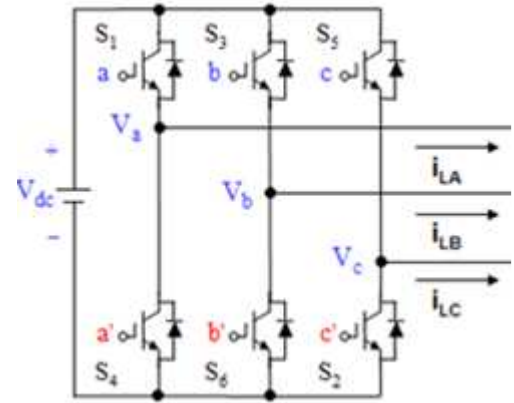- ♦ S_1 through S_6 are the six power transistors that shape the output voltage
- ♦ When an upper switch is turned on (i.e., **a, b or c** is “1”), the corresponding lower switch is turned off (i.e., **a', b' or c'** is “0”)



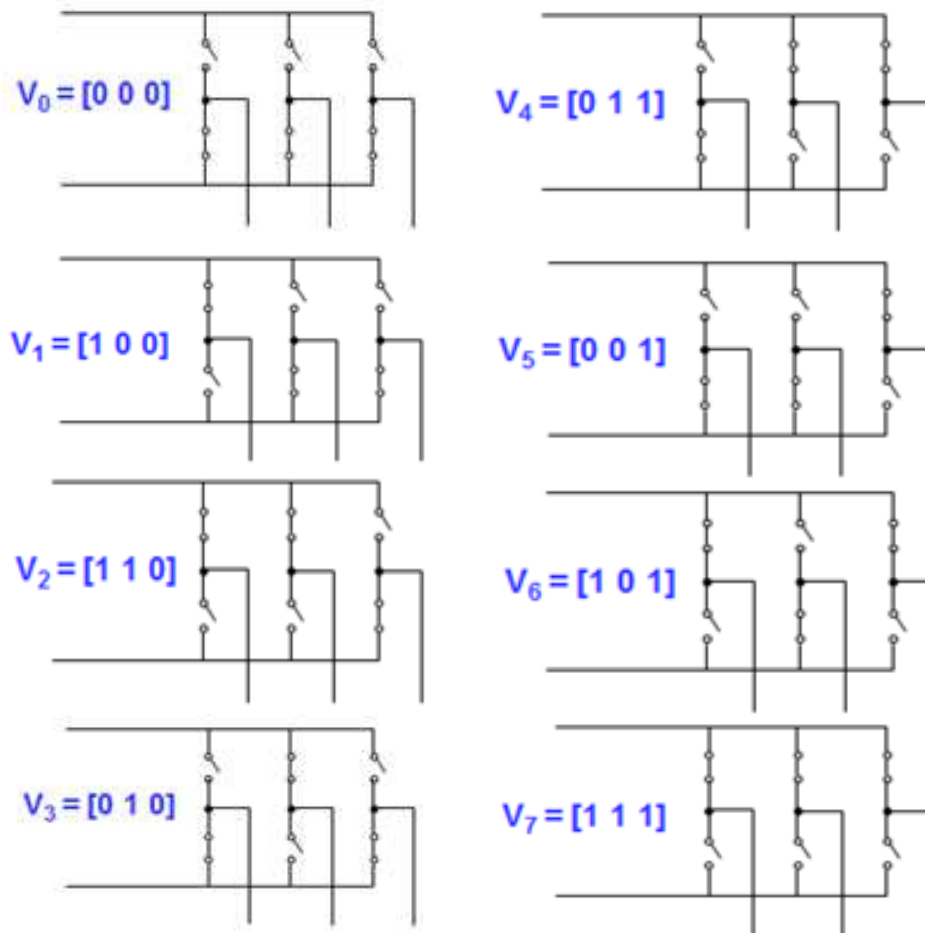Eight possible combinations of on and off patterns for the three upper transistors (S_1, S_3, S_5)



Voltage Vectors	Switching Vectors			Line to neutral voltage			Line to line voltage		
	a	b	c	V_{an}	V_{bn}	V_{cn}	V_{ab}	V_{bc}	V_{ca}
V_0	0	0	0	0	0	0	0	0	0
V_1	1	0	0	$2/3$	$-1/3$	$-1/3$	1	0	-1
V_2	1	1	0	$1/3$	$1/3$	$-2/3$	0	1	-1
V_3	0	1	0	$-1/3$	$2/3$	$-1/3$	-1	1	0
V_4	0	1	1	$-2/3$	$1/3$	$1/3$	-1	0	1
V_5	0	0	1	$-1/3$	$-1/3$	$2/3$	0	-1	1
V_6	1	0	1	$1/3$	$-2/3$	$1/3$	1	-1	0
V_7	1	1	1	0	0	0	0	0	0

(Note that the respective voltage should be multiplied by V_{dc})

SVPWM

- ♦ **Line to neutral (phase) voltage vector** $[V_{an} \ V_{bn} \ V_{cn}]^t$

$$\begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \frac{1}{3} V_{dc} \begin{bmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} a \\ b \\ c \end{bmatrix}$$

Voltage Vectors	Switching Vectors			Line to neutral voltage			Line to line voltage		
	a	b	c	V_{an}	V_{bn}	V_{cn}	V_{ab}	V_{bc}	V_{ca}
V_0	0	0	0	0	0	0	0	0	0
V_1	1	0	0	2/3	-1/3	-1/3	1	0	-1
V_2	1	1	0	1/3	1/3	-2/3	0	1	-1
V_3	0	1	0	-1/3	2/3	-1/3	-1	1	0
V_4	0	1	1	-2/3	1/3	1/3	-1	0	1
V_5	0	0	1	-1/3	-1/3	2/3	0	-1	1
V_6	1	0	1	1/3	-2/3	1/3	1	-1	0
V_7	1	1	1	0	0	0	0	0	0

(Note that the respective voltage should be multiplied by V_{dc})

- ♦ **Line to line voltage vector** $[V_{ab} \ V_{bc} \ V_{ca}]^t$

$$\begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} = V_{dc} \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} a \\ b \\ c \end{bmatrix}, \text{ where switching variable vector } [a \ b \ c]^t$$

Space Vector PWM

➤ Principle of Space Vector PWM

- ♦ Treats the sinusoidal voltage as a constant amplitude vector rotating at constant frequency
- ♦ This PWM technique approximates the reference voltage V_{ref} by a combination of the eight switching patterns (V_0 to V_7)
- ♦ Coordinate Transformation (abc reference frame to the stationary d-q frame):
A three-phase voltage vector is transformed into a vector in the stationary d-q coordinate frame which represents the spatial vector sum of the three-phase voltage
- ♦ The vectors (V_1 to V_6) divide the plane into six sectors (each sector: 60 degrees)
- ♦ V_{ref} is generated by two adjacent non-zero vectors and two zero vectors

Space Vector PWM

Basic switching vectors and Sectors

♦ 6 active vectors ($V_1, V_2, V_3, V_4, V_5, V_6$)

⇒ Axes of a hexagonal


⇒ DC link voltage is supplied to the load

⇒ Each sector (1 to 6): 60 degrees

♦ 2 zero vectors (V_0, V_7)

⇒ At origin

⇒ No voltage is supplied to the load

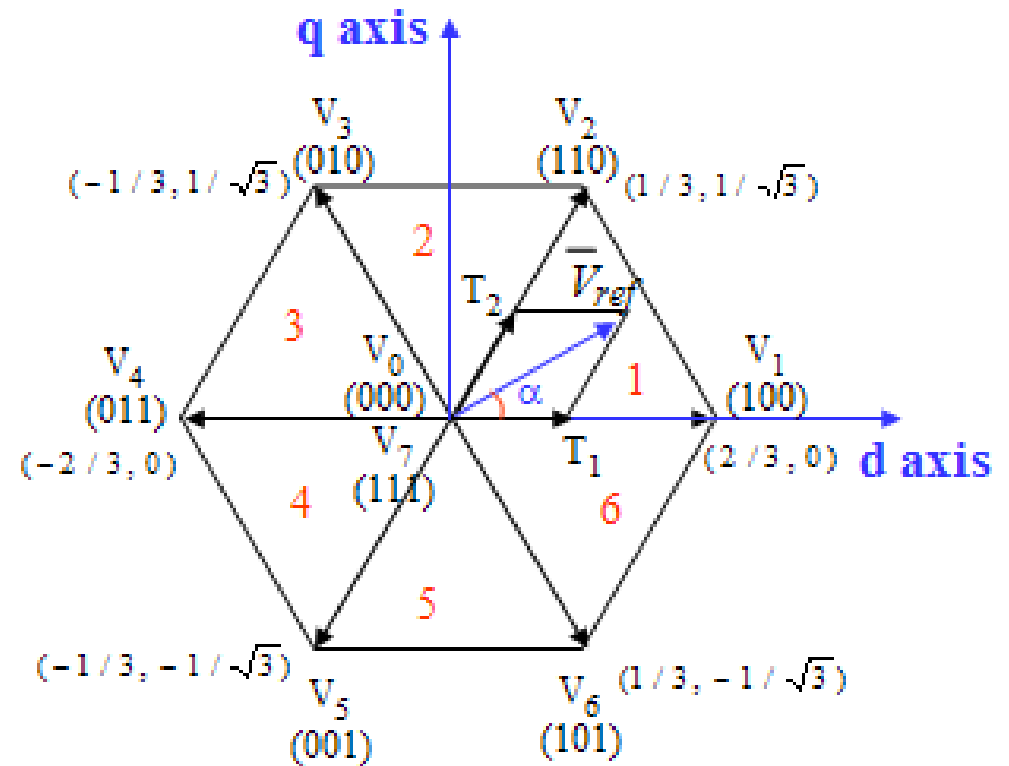

Space Vector PWM


Steps for implementation of Space Vector PWM

- ♦ **Step 1.** Determine V_d , V_q , V_{ref} , and angle (α)
- ♦ **Step 2.** Determine time duration T_1 , T_2 , T_0
- ♦ **Step 3.** Determine the switching time of each transistor (S_1 to S_6)

Space Vector PWM

➤ Step 1. Determine V_d , V_q , V_{ref} , and angle (α)

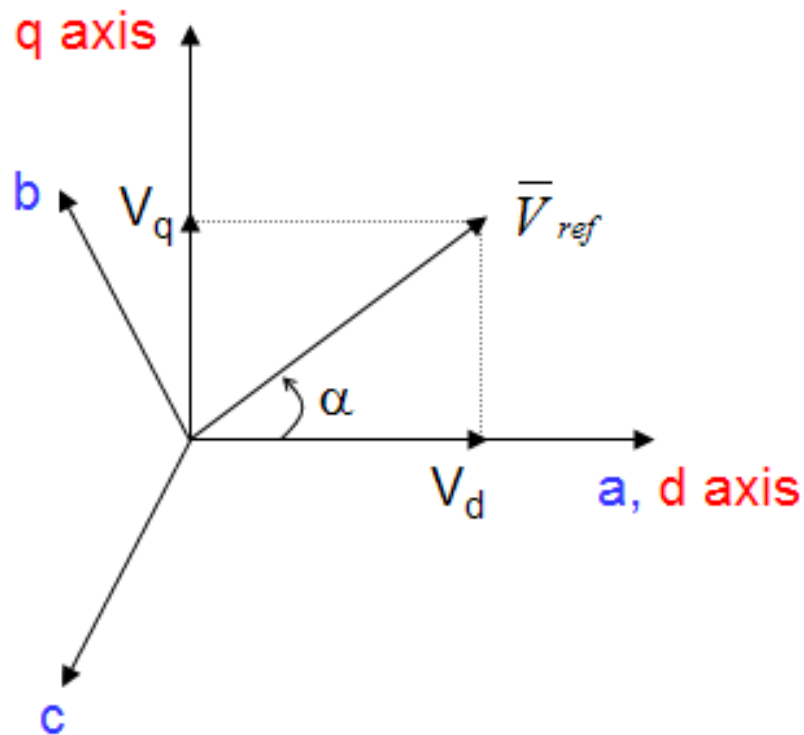- ♦ Coordinate transformation
: abc to dq



Voltage Space Vector and its components in (d, q).

$$\begin{aligned} V_d &= V_{an} - V_{bn} \cdot \cos 60 - V_{cn} \cdot \cos 60 \\ &= V_{an} - \frac{1}{2} V_{bn} - \frac{1}{2} V_{cn} \end{aligned}$$

$$\begin{aligned} V_q &= 0 + V_{bn} \cdot \cos 30 - V_{cn} \cdot \cos 30 \\ &= V_{an} + \frac{\sqrt{3}}{2} V_{bn} - \frac{\sqrt{3}}{2} V_{cn} \end{aligned}$$

$$\therefore \begin{bmatrix} V_d \\ V_q \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix}$$

$$|\bar{V}_{ref}| = \sqrt{V_d^2 + V_q^2}$$

$$\alpha = \tan^{-1}\left(\frac{V_q}{V_d}\right) = \omega_s t = 2\pi f_s t$$

(where f_s = fundamental frequency)

Space Vector PWM

➤ **Step 2.** Determine time duration T_1 , T_2 , T_0 (1)

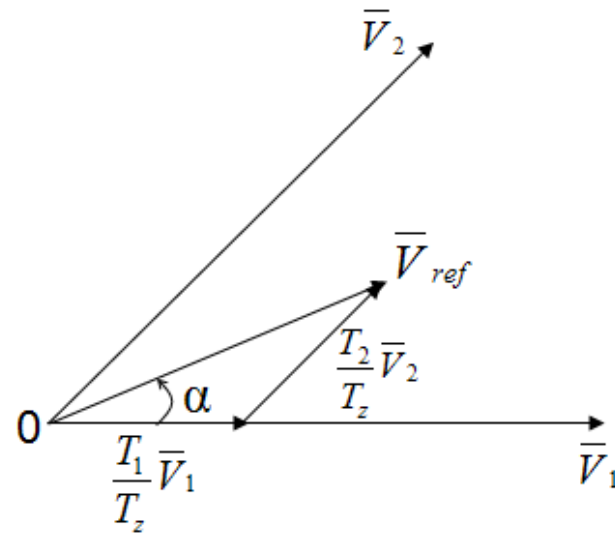


Fig. 14 Reference vector as a combination of adjacent vectors at sector 1.

Space Vector PWM

➤ Step 2. Determine time duration T_1, T_2, T_0 (2)

♦ Switching time duration at Sector 1

$$\int_0^{T_z} \bar{V}_{\text{ref}} dt = \int_0^{T_1} \bar{V}_1 dt + \int_{T_1}^{T_1+T_2} \bar{V}_2 dt + \int_{T_1+T_2}^{T_z} \bar{V}_0 dt$$

$$\therefore T_z \cdot \bar{V}_{\text{ref}} = (T_1 \cdot \bar{V}_1 + T_2 \cdot \bar{V}_2)$$

$$\Rightarrow T_z \cdot |\bar{V}_{\text{ref}}| \cdot \begin{bmatrix} \cos(\alpha) \\ \sin(\alpha) \end{bmatrix} = T_1 \cdot \frac{2}{3} \cdot V_{\text{dc}} \cdot \begin{bmatrix} 1 \\ 0 \end{bmatrix} + T_2 \cdot \frac{2}{3} \cdot V_{\text{dc}} \cdot \begin{bmatrix} \cos(\pi/3) \\ \sin(\pi/3) \end{bmatrix}$$

(where, $0 \leq \alpha \leq 60^\circ$)

$$\therefore T_1 = T_z \cdot a \cdot \frac{\sin(\pi/3 - \alpha)}{\sin(\pi/3)}$$

$$\therefore T_2 = T_z \cdot a \cdot \frac{\sin(\alpha)}{\sin(\pi/3)}$$

$$\therefore T_0 = T_z - (T_1 + T_2), \quad \left(\text{where, } T_z = \frac{1}{f_s} \quad \text{and} \quad a = \frac{|\bar{V}_{\text{ref}}|}{\frac{2}{3} V_{\text{dc}}} \right)$$

Space Vector PWM

➤ Step 2. Determine time duration T_1, T_2, T_0 (3)

♦ Switching time duration at any Sector

$$\begin{aligned}\therefore T_1 &= \frac{\sqrt{3} \cdot T_z \cdot |\bar{V}_{ref}|}{V_{dc}} \left(\sin \left(\frac{\pi}{3} - \alpha + \frac{n-1}{3} \pi \right) \right) \\ &= \frac{\sqrt{3} \cdot T_z \cdot |\bar{V}_{ref}|}{V_{dc}} \left(\sin \frac{n}{3} \pi - \alpha \right) \\ &= \frac{\sqrt{3} \cdot T_z \cdot |\bar{V}_{ref}|}{V_{dc}} \left(\sin \frac{n}{3} \pi \cos \alpha - \cos \frac{n}{3} \pi \sin \alpha \right)\end{aligned}$$


$$\begin{aligned}\therefore T_2 &= \frac{\sqrt{3} \cdot T_z \cdot |\bar{V}_{ref}|}{V_{dc}} \left(\sin \left(\alpha - \frac{n-1}{3} \pi \right) \right) \\ &= \frac{\sqrt{3} \cdot T_z \cdot |\bar{V}_{ref}|}{V_{dc}} \left(-\cos \alpha \cdot \sin \frac{n-1}{3} \pi + \sin \alpha \cdot \cos \frac{n-1}{3} \pi \right)\end{aligned}$$

$$\therefore T_0 = T_z - T_1 - T_2, \quad \left(\begin{array}{l} \text{where, } n = 1 \text{ through } 6 \text{ (that is, Sector 1 to 6)} \\ 0 \leq \alpha \leq 60^\circ \end{array} \right)$$

Switching Sequence in a Sector


➤ **Step 3. Determine the switching time of each transistor**

Vector	State	Time
V1	100	T1
V2	110	T2
V0	000	$T_0/2$
V7	111	$T_0/2$

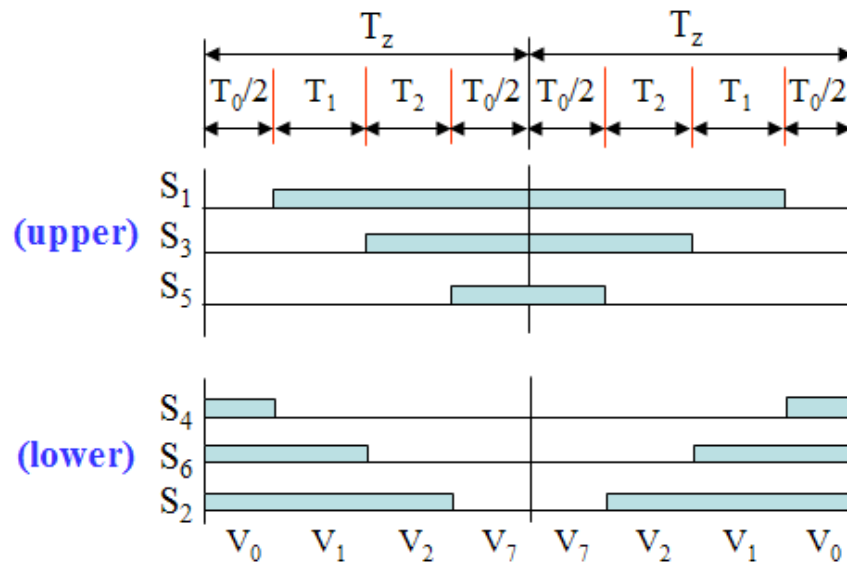

(a) Sector 1.


Vector	State	Time
V2	110	T1
V3	010	T2
V0	000	$T_0/2$
V7	111	$T_0/2$

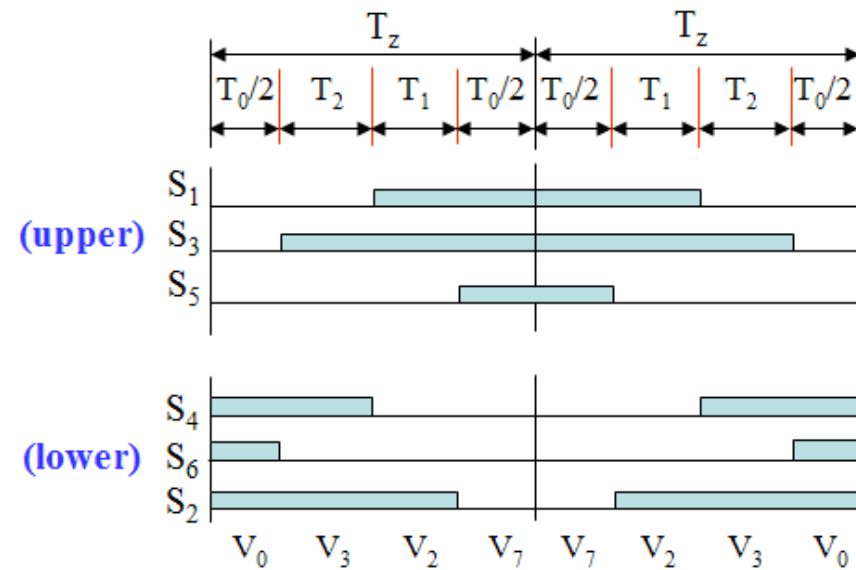

(b) Sector 2.


Switching Sequence in a Sector

Vector	State	Time
V3	010	T1
V4	011	T2
V0	000	$T_0/2$
V7	111	$T_0/2$

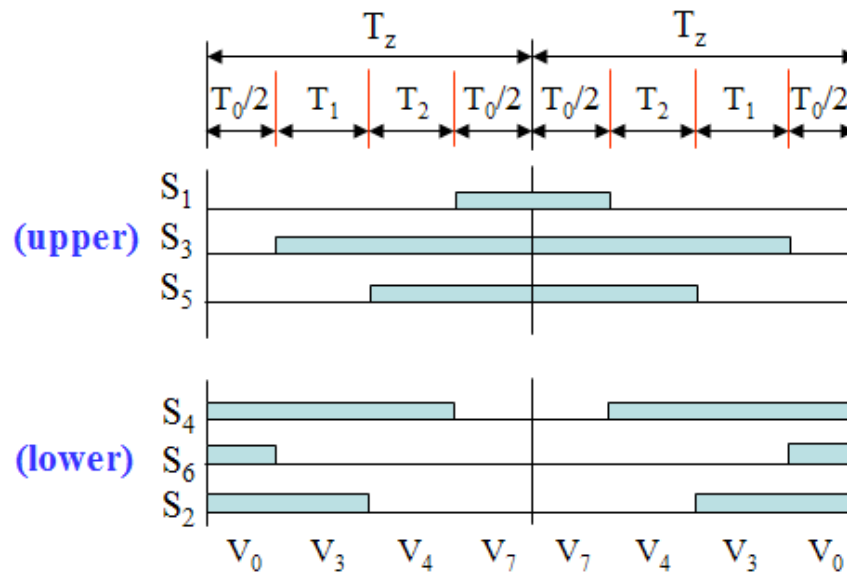

(c) Sector 3.


Vector	State	Time
V4	011	T1
V5	001	T2
V0	000	$T_0/2$
V7	111	$T_0/2$

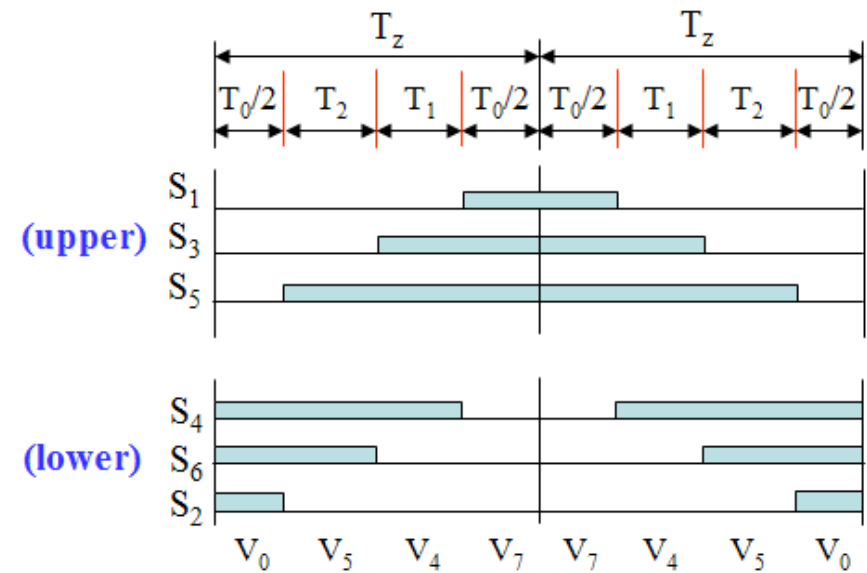

(d) Sector 4.


Switching Sequence in a Sector

Vector	State	Time
V5	001	T1
V6	101	T2
V0	000	$T_0/2$
V7	111	$T_0/2$

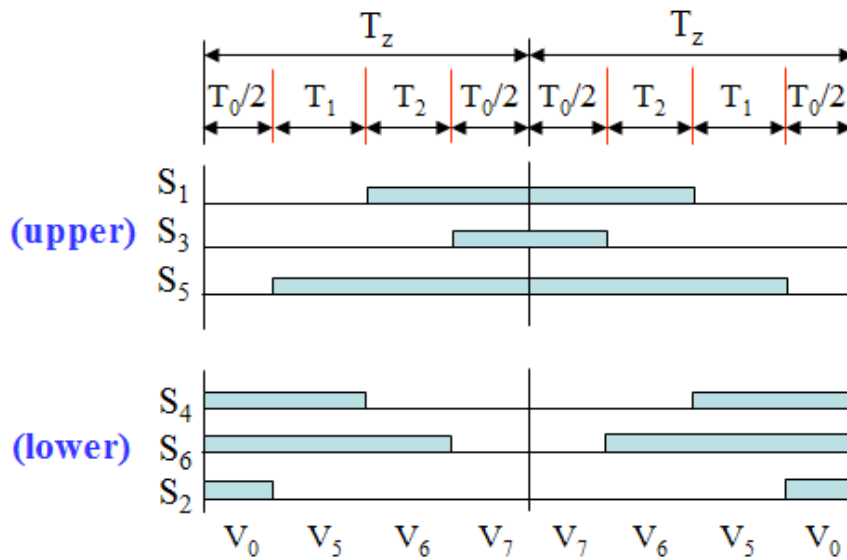

(e) Sector 5.

Vector	State	Time
V6	101	T1
V1	100	T2
V0	000	$T_0/2$
V7	111	$T_0/2$

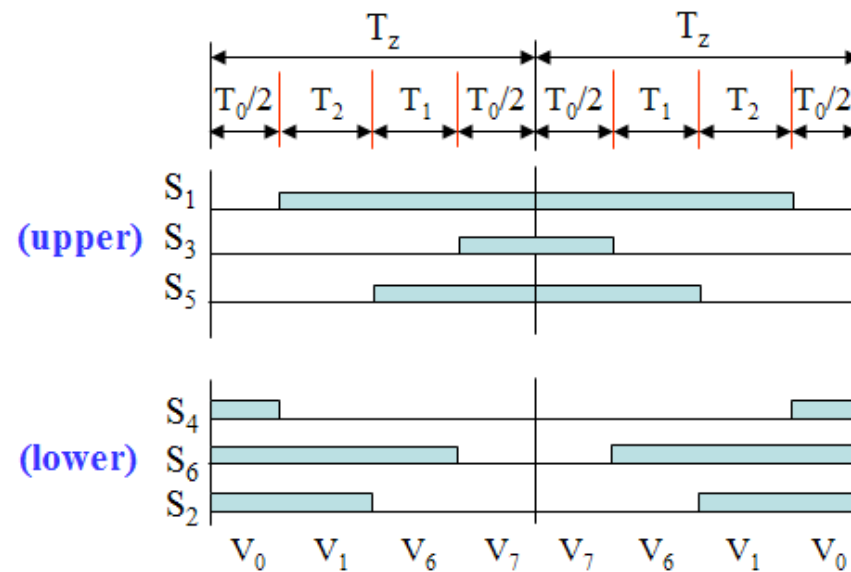

(f) Sector 6.

Implementation of Space Vector PWM

Step 3. Determine the switching time of each transistor (S_1 to S_6)

Table 1. Switching Time Table at Each Sector

Sector	Upper Switches (S_1, S_3, S_5)	Lower Switches (S_4, S_6, S_2)
1	$S_1 = T_1 + T_2 + T_0 / 2$ $S_3 = T_2 + T_0 / 2$ $S_5 = T_0 / 2$	$S_4 = T_0 / 2$ $S_6 = T_1 + T_0 / 2$ $S_2 = T_1 + T_2 + T_0 / 2$
2	$S_1 = T_1 + T_0 / 2$ $S_3 = T_1 + T_2 + T_0 / 2$ $S_5 = T_0 / 2$	$S_4 = T_2 + T_0 / 2$ $S_6 = T_0 / 2$ $S_2 = T_1 + T_2 + T_0 / 2$
3	$S_1 = T_0 / 2$ $S_3 = T_1 + T_2 + T_0 / 2$ $S_5 = T_2 + T_0 / 2$	$S_4 = T_1 + T_2 + T_0 / 2$ $S_6 = T_0 / 2$ $S_2 = T_1 + T_0 / 2$
4	$S_1 = T_0 / 2$ $S_3 = T_1 + T_0 / 2$ $S_5 = T_1 + T_2 + T_0 / 2$	$S_4 = T_1 + T_2 + T_0 / 2$ $S_6 = T_2 + T_0 / 2$ $S_2 = T_0 / 2$
5	$S_1 = T_2 + T_0 / 2$ $S_3 = T_0 / 2$ $S_5 = T_1 + T_2 + T_0 / 2$	$S_4 = T_1 + T_0 / 2$ $S_6 = T_1 + T_2 + T_0 / 2$ $S_2 = T_0 / 2$
6	$S_1 = T_1 + T_2 + T_0 / 2$ $S_3 = T_0 / 2$ $S_5 = T_1 + T_0 / 2$	$S_4 = T_0 / 2$ $S_6 = T_1 + T_2 + T_0 / 2$ $S_2 = T_2 + T_0 / 2$

Space Vector PWM

- A voltage source inverter is supplied from a 620-V dc source and feeds a balance wye connected load. At a certain instant, the inverter is in state 3 and the output currents in phase A and B are -72 and 67A, respectively. Neglect the voltage drops in the inverter and determine all the output voltages and input current.

$$\begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} = V_{dc} \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} a \\ b \\ c \end{bmatrix} = 620 \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \\ 1 \end{bmatrix} = \begin{bmatrix} -620 \\ 0 \\ 620 \end{bmatrix}$$

$$\begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \frac{620}{3} \begin{bmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \\ 1 \end{bmatrix} = \begin{bmatrix} -414 \\ 207 \\ 207 \end{bmatrix}$$