

Lecture #4

(1)

In last lecture we discussed 180° conduction (square wave) inverter

State #	Switching States							Space Vector	
		V_{ab}	V_{bc}	V_{ca}	V_{an}	V_{bn}	V_{cn}	Line Voltage	Phase Voltages
1	1 0 0	V_s	0	$-V_s$	$\frac{2}{3}V_{dc}$	$-\frac{1}{3}V_{dc}$	$-\frac{1}{3}V_{dc}$	$\frac{2}{\sqrt{3}} \angle 30^\circ$	$\frac{2}{3} \angle 0^\circ$
2	1 1 0	0	$+V_s$	$-V_s$	$\frac{1}{3}V_{dc}$	$\frac{1}{3}V_{dc}$	$-\frac{2}{3}V_{dc}$	$\frac{2}{\sqrt{3}} \angle 90^\circ$	$\frac{2}{3} \angle 60^\circ$
3	0 1 0	$-V_s$	V_s	0	$-\frac{1}{3}$	$\frac{2}{3}$	$-\frac{1}{3}$	$\frac{2}{\sqrt{3}} \angle 150^\circ$	$\frac{2}{3} \angle 120^\circ$
4	0 1 1	$-V_s$	0	V_s	$-\frac{2}{3}$	$\frac{1}{3}$	$\frac{1}{3}$	$\frac{2}{\sqrt{3}} \angle 210^\circ$	$\frac{2}{3} \angle 180^\circ$
5	0 0 1	0	$-V_s$	V_s	$-\frac{1}{3}$	$-\frac{1}{3}$	$\frac{2}{3}$	$\frac{2}{\sqrt{3}} \angle 270^\circ$	$\frac{2}{3} \angle 240^\circ$
6	1 0 1	V_s	$-V_s$	0	$\frac{1}{3}$	$-\frac{2}{3}$	$\frac{1}{3}$	$\frac{2}{\sqrt{3}} \angle 330^\circ$	$\frac{2}{3} \angle 300^\circ$
7	1 1 1	0	0	0	0	0	0	0	0
8	0 0 0	0	0	0	0	0	0	0	0

State 1: (1 0 0)

$$Q_s = \frac{2}{3} \left[1 + 0 + 1e^{j4\pi/3} \right]$$

$$= \frac{2}{3} \left[\sqrt{3} \angle 30^\circ \right] = \frac{2}{\sqrt{3}} \angle 30^\circ$$

State 2: (1 1 0)

$$Q_s = \frac{2}{3} \left[0 + e^{j2\pi/3} + e^{j4\pi/3} \right]$$

$$Q_s = \frac{2}{3} \left[\sqrt{3} \angle 90^\circ \right] = \frac{2}{\sqrt{3}} \angle 90^\circ$$

State 3: (0 1 0)

$$Q_s = \frac{2}{3} \left[-1 + e^{j2\pi/3} \right]$$

$$= \frac{2}{3} \left[\sqrt{3} \angle 150^\circ \right] = \frac{2}{\sqrt{3}} \angle 150^\circ$$

State 4: (0 1 1)

$$Q_s = \frac{2}{\sqrt{3}} \angle 210^\circ$$

State 5:

$$Q_s = \frac{2}{\sqrt{3}} \angle 270^\circ$$

State 6

$$Q_s = \frac{2}{3} \angle 330^\circ$$

State 1:

$$Q_s = \frac{2}{3} \left[\frac{2}{3} - \frac{1}{3} e^{j2\pi/3} - \frac{1}{3} e^{j4\pi/3} \right]$$

$$Q_s = \frac{2}{3} \angle 0^\circ$$

State 2


$$Q_s = \frac{2}{3} \left[\frac{1}{3} + \frac{1}{3} e^{j2\pi/3} - \frac{2}{3} e^{j4\pi/3} \right]$$

$$Q_s = \frac{2}{3} \angle 60^\circ$$

In general

$$V_k = \begin{cases} \frac{2}{3} e^{j(V-1)\pi/3} & V = 1, 2, 3, \dots, 6 \\ 0 & V = 0, 7 \end{cases}$$

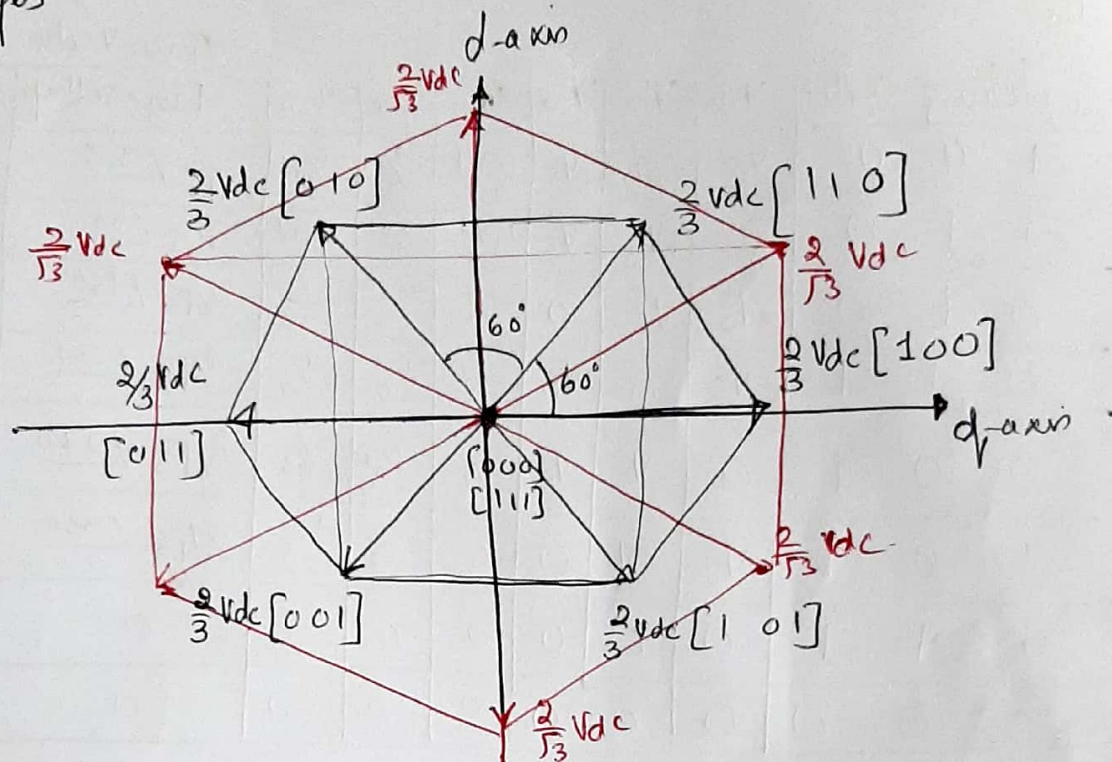- So the space vector representation for phase voltages.



- Red colour shows the position of space vector of line voltage. (higher magnitude & phase difference of 30° with respect to phase voltage space vector).
- Space vector is based upon balancing of root second product of reference vector with adjacent vectors of the sectors.

Line Calculation

Consider the reference vector in sector 1 as shown in the figure

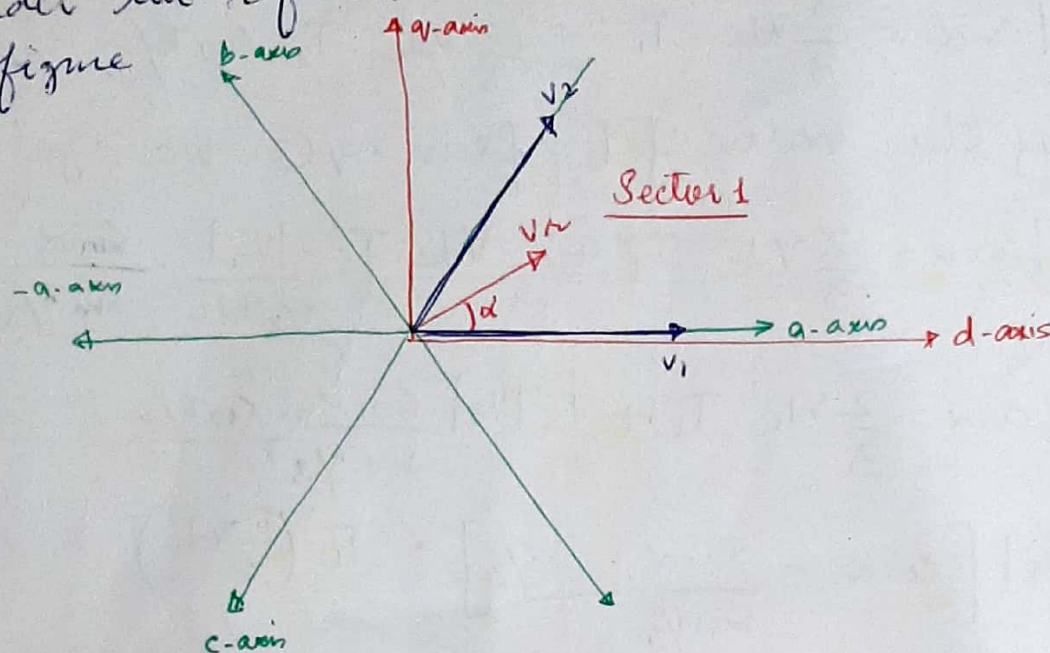


Figure A

① Volt second product in sector 1 can be written as

$$\vec{V}_2 \times T_s = \vec{V}_1 \times T_1 + \vec{V}_2 \times T_2 + \vec{V}_3 \times T_0 \quad (1)$$

$$V_2 = |V_2| \cos \alpha + j |V_2| \sin \alpha$$

$$V_1 = \frac{2}{3} V_{dc} + j(0)$$

$$V_2 = \frac{2}{3} V_{dc} \cos \pi/3 + j \frac{2}{3} V_{dc} \sin \pi/3$$

Equation (1) can be written as

$$T_s |V_2| \begin{bmatrix} \cos \alpha \\ \sin \alpha \end{bmatrix} = T_1 \left(\frac{2}{3} V_{dc} \right) \begin{bmatrix} 1 \\ 0 \end{bmatrix} + T_2 \left(\frac{2}{3} V_{dc} \right) \begin{bmatrix} \cos \pi/3 \\ \sin \pi/3 \end{bmatrix} + 0 \times T_0 \quad (2)$$

from eq (2)

$$T_s |V_2| \sin \alpha = T_2 \left(\frac{2}{3} V_{dc} \right) \sin \pi/3$$

$$T_2 = \frac{|V_2|}{\left[\frac{2}{3} V_{dc} \right]} \cdot T_s \cdot \frac{\sin \alpha}{\sin \pi/3}$$

$$T_2 = T_s \cdot a \frac{\sin \alpha}{\sin \pi/3} \quad (3) \quad \text{where } a = \frac{|V_2|}{\left[\frac{2}{3} V_{dc} \right]}$$

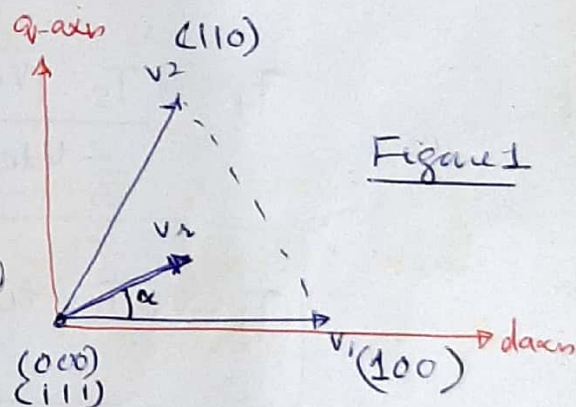


Figure 1

from eq (2)

$$T_s |V_r| \cos \alpha = \frac{2}{3} V_{dc} \cdot T_1 + \frac{2}{3} V_{dc} \cdot T_2 \cos \pi/3$$

placing the value of T_2 from eq (3) we get

$$T_s |V_r| \cos \alpha = \frac{2}{3} V_{dc} \cdot T_1 + \frac{2}{3} V_{dc} \cdot T_s \cdot \frac{|V_r|}{\frac{2}{3} V_{dc}} \cdot \frac{\sin \alpha}{\sin \pi/3} \cdot \cos \pi/3$$

$$T_s |V_r| \cos \alpha = \frac{2}{3} V_{dc} \cdot T_1 + T_s |V_r| \frac{\sin \alpha}{\sin \pi/3} \cdot \cos \pi/3$$

$$T_s |V_r| \left[\cos \alpha - \frac{\sin \alpha \cdot \cos \pi/3}{\sin \pi/3} \right] = T_1 \cdot \left(\frac{2}{3} V_{dc} \right)$$


$$T_1 = \frac{T_s \cdot |V_r|}{\frac{2}{3} V_{dc}} \left[\frac{\cos \alpha \sin \pi/3 - \sin \alpha \cos \pi/3}{\sin \pi/3} \right]$$

$$T_1 = T_s \cdot a \left[\frac{\sin (\pi/3 - \alpha)}{\sin \pi/3} \right] \quad \text{--- (4)}$$

Now

$$T_0 = T_s - (T_1 + T_2) \quad \text{--- (5)}$$

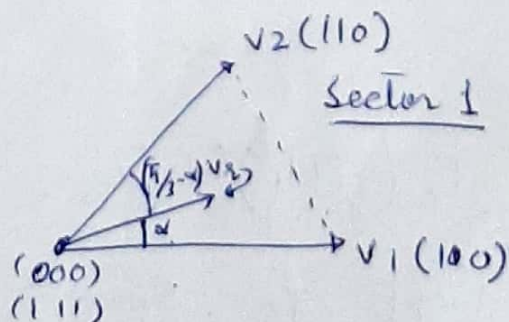* Looking at figure in sector 1 we can generalize the



expression of T_1 & T_2 for any sector 'n'.

→ For second sector

(2)

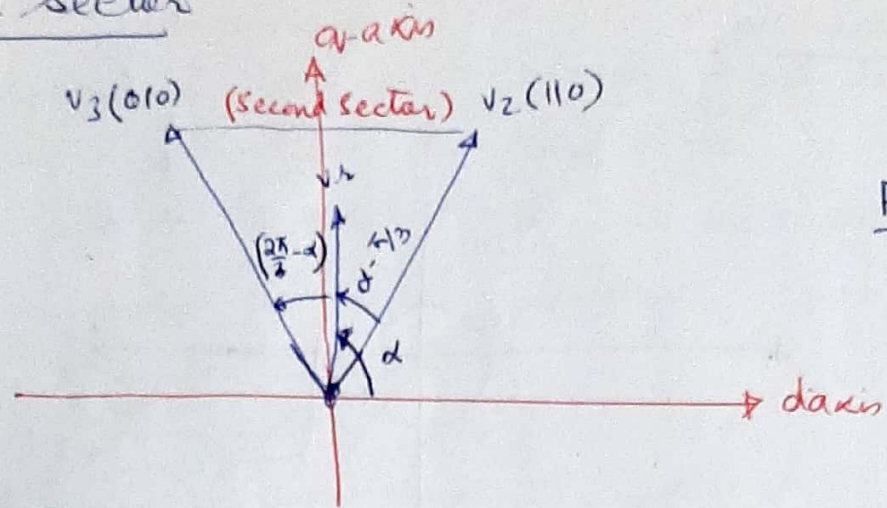


Figure 2

→ For third sector

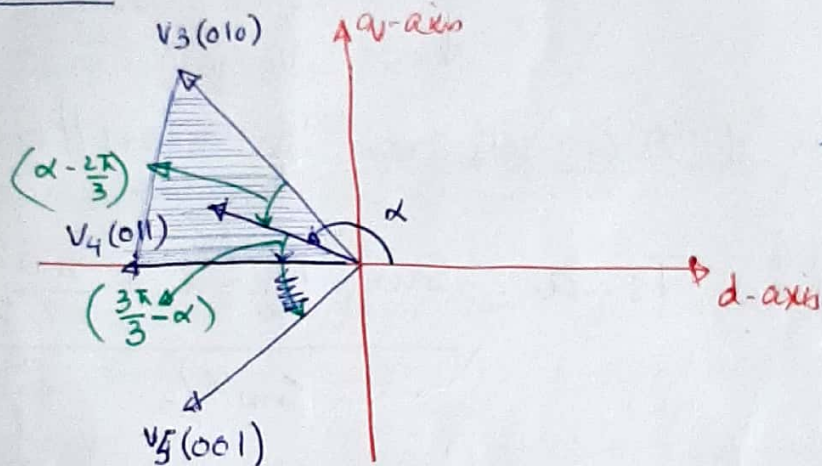


Figure 3

→ For sector no. 4

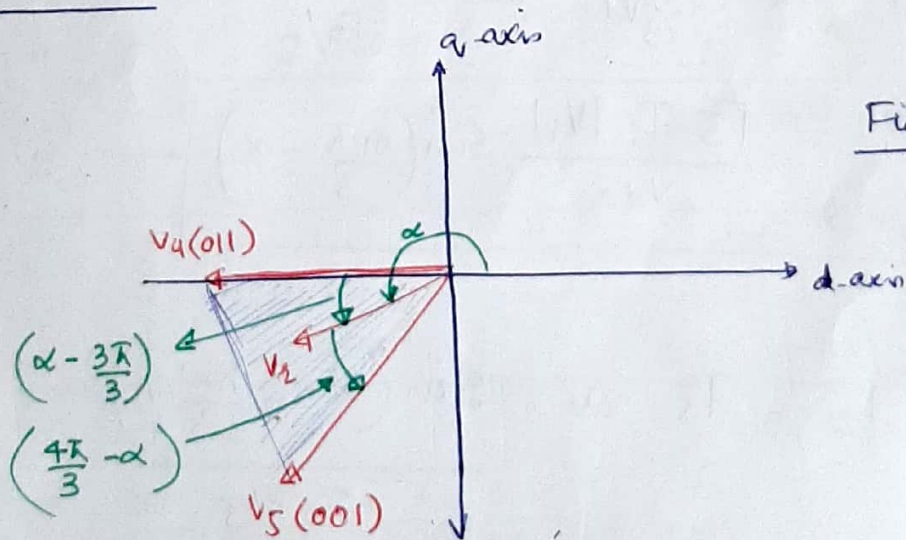


Figure 4

→ For sector no. 5


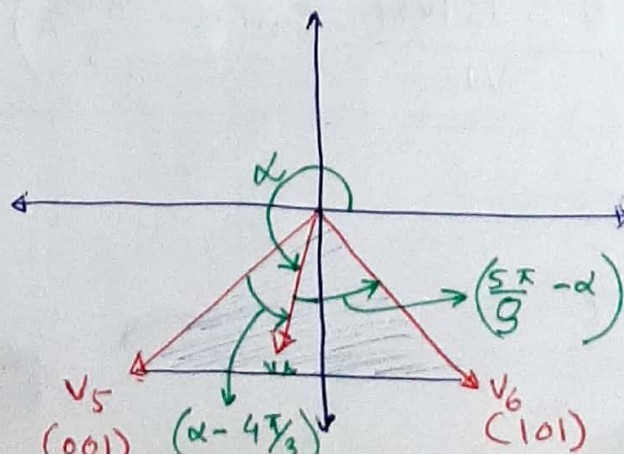


Figure 5

For sector no. 6

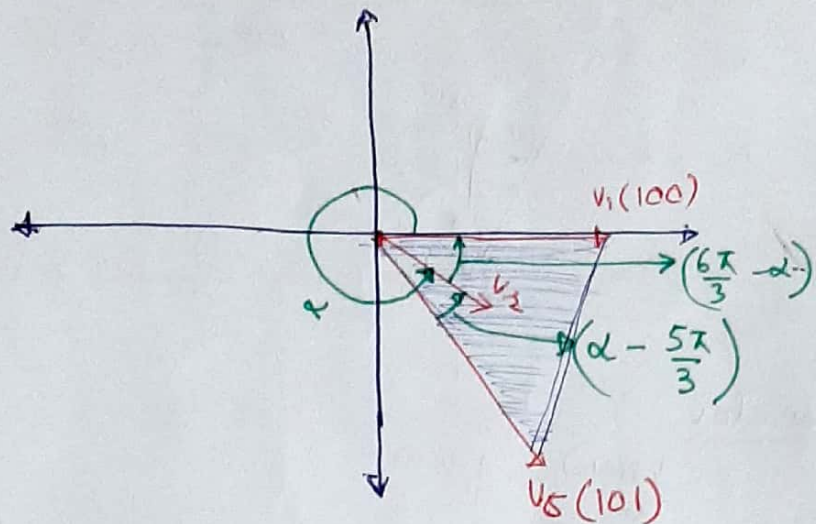

From figure 1 to 6 it can be written as

$$T_1 = T_s \cdot a \cdot \frac{\sin\left(\frac{\pi}{3} - \alpha + \frac{n-1}{3}\pi\right)}{\sin \pi/3}$$

$$T_1 = T_s \cdot \frac{|V_{L1}|}{\frac{2}{3}V_{dc}} \cdot \frac{\sin\left(\frac{\pi}{3} - \alpha + \frac{n\pi}{3} - \frac{\pi}{3}\right)}{\frac{\sqrt{3}}{2}}$$

$$T_1 = \frac{\sqrt{3} T_s |V_{L1}|}{V_{dc}} \sin\left(\frac{n\pi}{3} - \alpha\right) \quad \text{--- (6)}$$

Similarly

$$T_2 = T_s \cdot a \cdot \frac{\sin\left(\alpha - \frac{n-1}{3}\pi\right)}{\sin \pi/3}$$

$$T_2 = \frac{\sqrt{3} T_s |V_{L1}|}{V_{dc}} \sin\left(\alpha - \frac{n-1}{3}\pi\right) \quad \text{--- (7)}$$



Switching Diagrams & Sequences

3

- ① V_0 & V_8 represent the zero vectors and are the part of every sector. Time for zero vector ' T_0 ' can be divided in two parts each of ' $T_0/2$ ' to include both of the zero states in a sector switching

→ Consider the sector 1

Let us start with the switching combination (000). This will be applied for time ' $T_0/2$ '. Then next three/zero switching combination are there i.e. (111) (100) & (110) but we switch to (100) as only one switch goes through transition. Combination (100) represents the voltage vector V_1 & applied for time ' T_1 '. At the end of ' T_1 ' we have possible combinations of (110) & (111) but (110) is switched for time ' T_2 ' and finally (111) is switched for ' $T_0/2$ '.

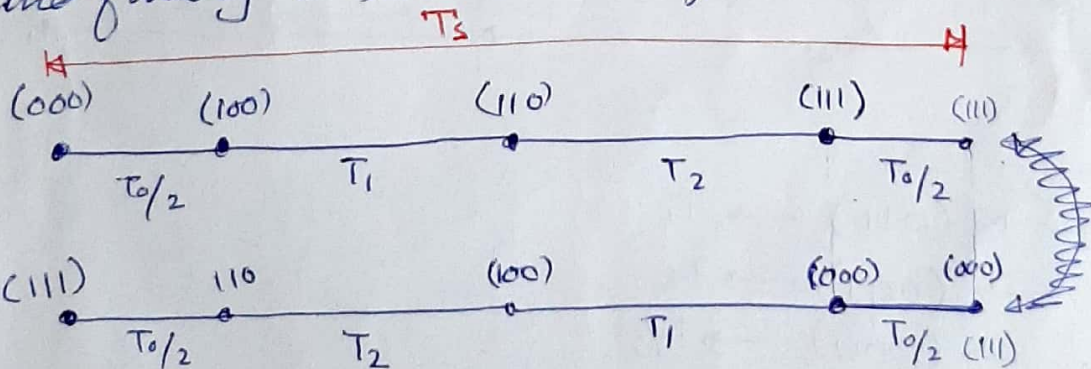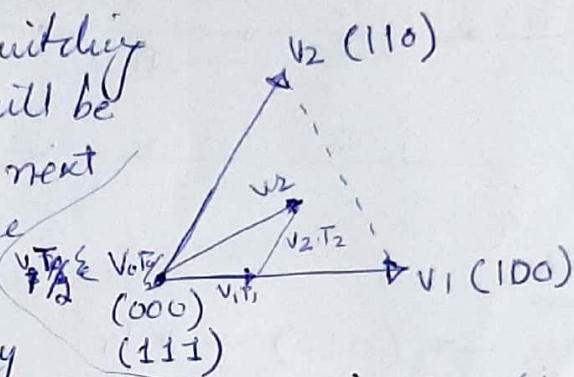

Next Sampling Cycle

	$T_0/2$	T_1	T_2	$T_0/2$	$T_0/2$	T_2	T_1	$T_0/2$
S1	(000)	(000)	(110)	(111)	(111)	(110)	(100)	000
S3								
S5								
S4								
S6								
S2								


Sector 2

$$V_2 \rightarrow (110) \rightarrow T_1$$

$$V_3 \rightarrow (010) \rightarrow T_2$$

$$V_0 \rightarrow (000) \rightarrow T_0/2$$

$$V_7 \rightarrow (111) \rightarrow T_0/2$$

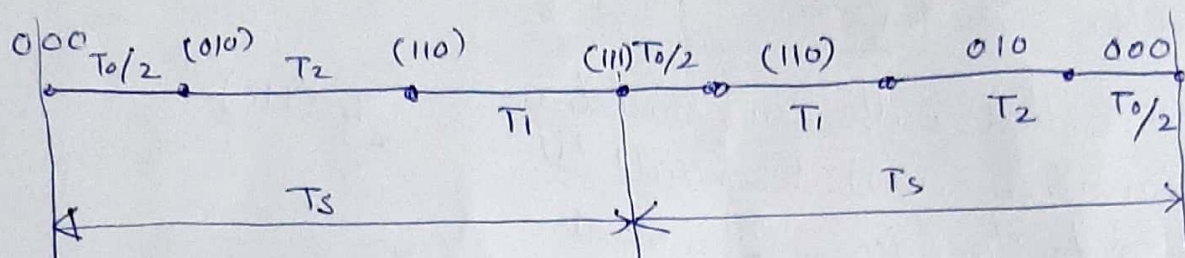


Sector 3

$$V_3 \rightarrow (010) \rightarrow T_1$$

$$V_4 \rightarrow (011) \rightarrow T_2$$

$$V_0 \rightarrow (000) \rightarrow T_0/2$$

$$V_7 \rightarrow (111) \rightarrow T_0/2$$

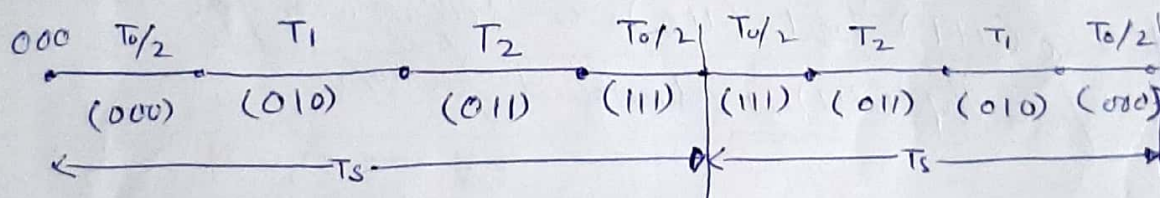


Sector 4

$$V_4 \rightarrow (011) \rightarrow T_1$$

$$V_5 \rightarrow (001) \rightarrow T_2$$


$$V_0 \rightarrow (000) \rightarrow T_0/2$$

$$V_7 \rightarrow (111) \rightarrow T_0/2$$

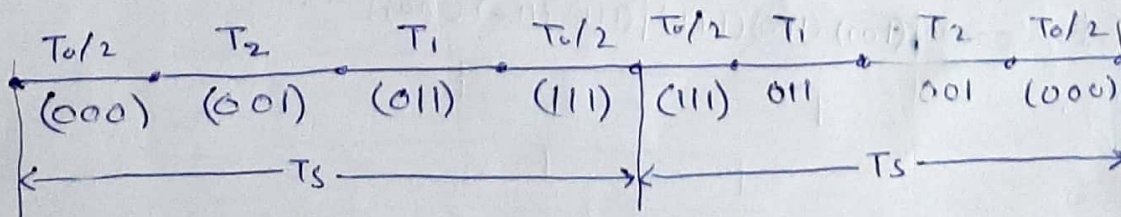


Sector 5

$$\begin{aligned} V_5 &\rightarrow (001) \rightarrow T_1 \\ V_6 &\rightarrow (101) \rightarrow T_2 \\ V_0 &\rightarrow (000) \rightarrow T_0/2 \\ V_7 &\rightarrow (111) \rightarrow T_0/2 \end{aligned}$$

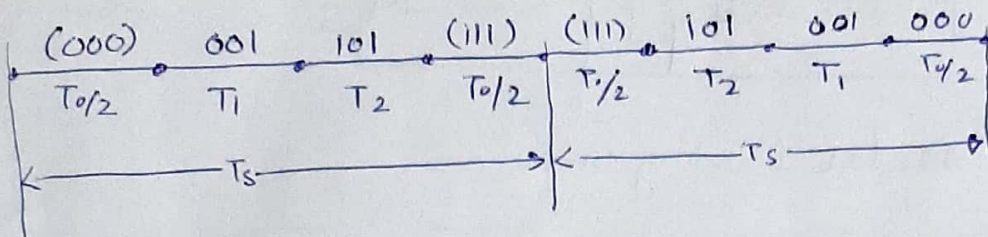


Sector 6

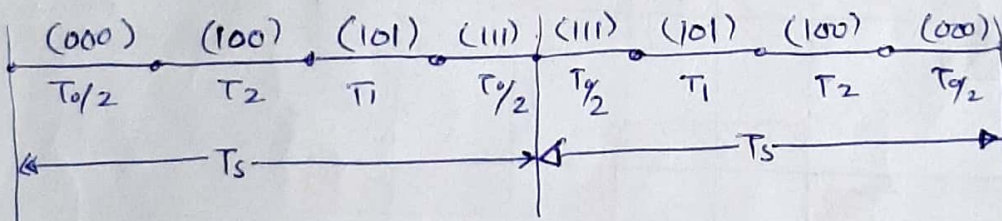
$$\begin{aligned} V_6 &\rightarrow (101) \rightarrow T_1 \\ V_1 &\rightarrow (100) \rightarrow T_2 \\ V_0 &\rightarrow (000) \rightarrow T_0/2 \\ V_7 &\rightarrow (111) \rightarrow T_0/2 \end{aligned}$$



Average Pole Voltages

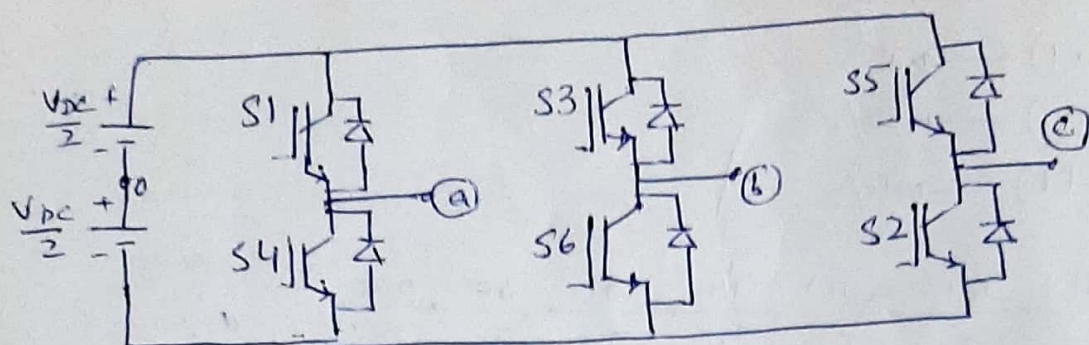

Sequence for sector 1 is given as

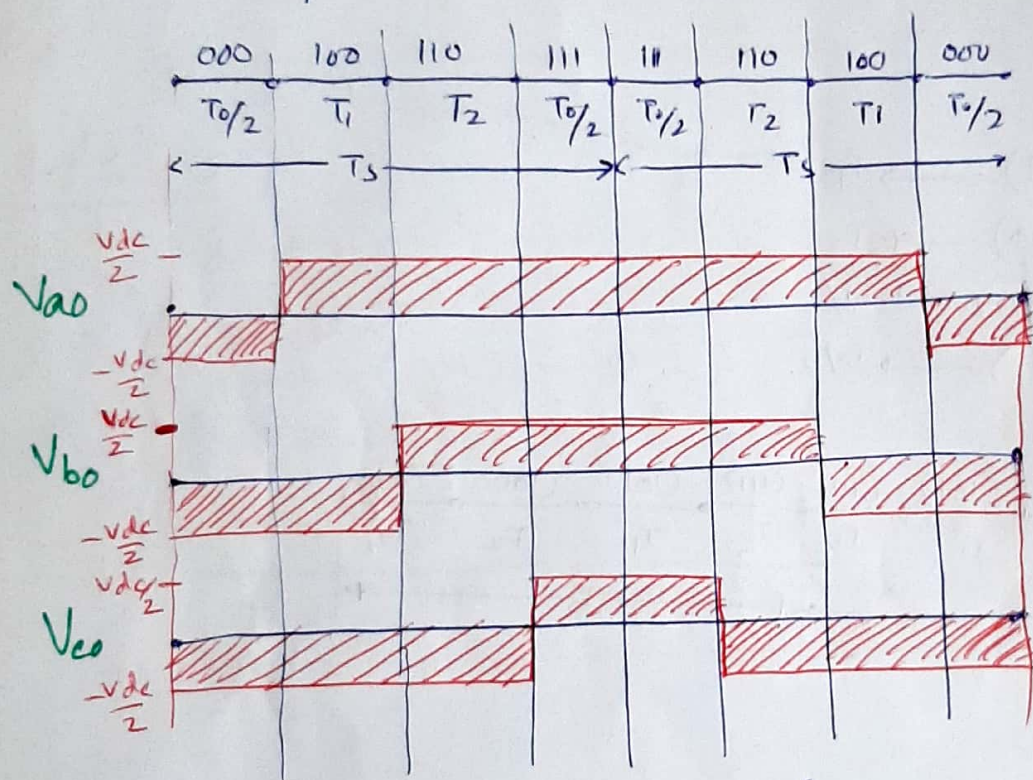

① Similarly we can plot for every sector
 → Looking at the above waveforms.

$$V_{ao}(\text{avg}) = \frac{V_{dc}/2}{T_s} \left[-\frac{T_0}{2} + T_1 + T_2 + \frac{T_0}{2} \right] = \frac{V_{dc}/2}{T_s} [T_1 + T_2]$$


$$V_{bo}(\text{avg}) = \frac{V_{dc}/2}{T_s} \left[-\frac{T_0}{2} - T_1 + T_2 + \frac{T_0}{2} \right] = \frac{V_{dc}/2}{T_s} [-T_1 + T_2]$$

$$V_{co}(\text{avg}) = \frac{V_{dc}/2}{T_s} \left[-\frac{T_0}{2} - T_1 - T_2 + \frac{T_0}{2} \right] = \frac{V_{dc}/2}{T_s} [-T_1 - T_2]$$


Control of Electrical Machine Drives

(1)


Space vector plane of a three phase inverter is shown in Figure that we have discussed in last lecture.

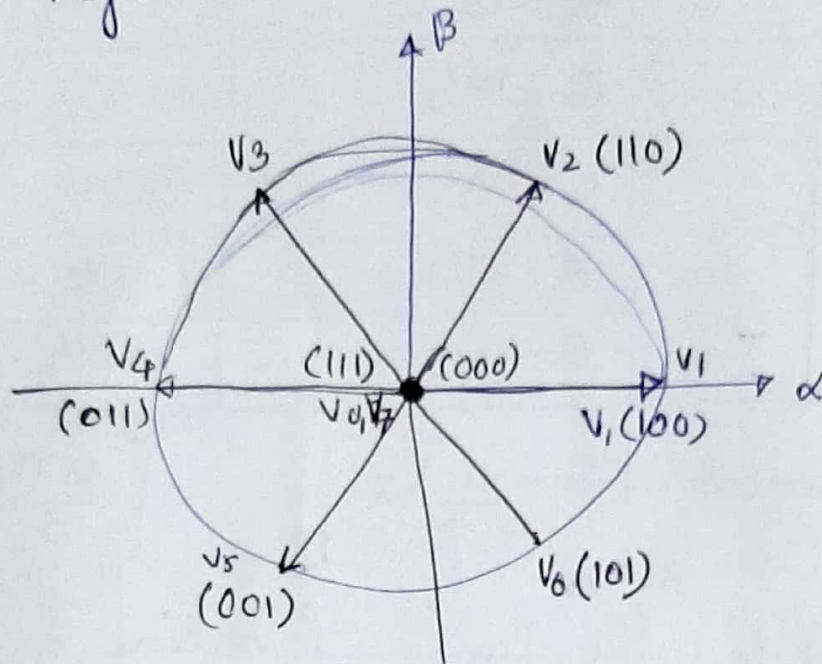


Sector 1:

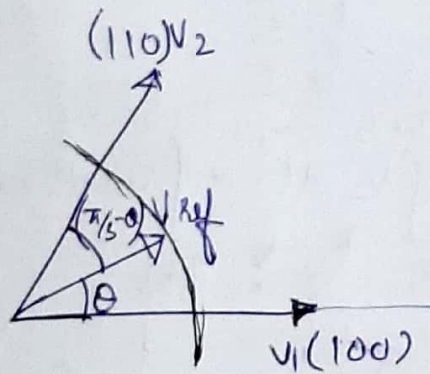


Sector 2:

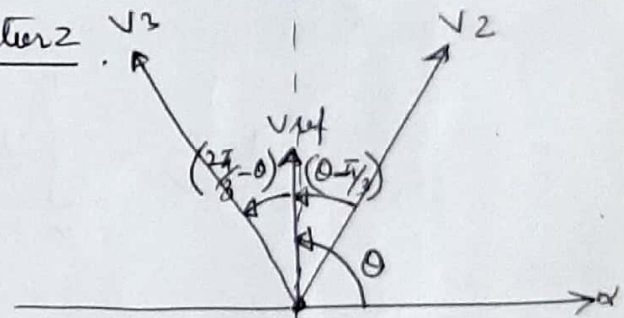


Sector 3:

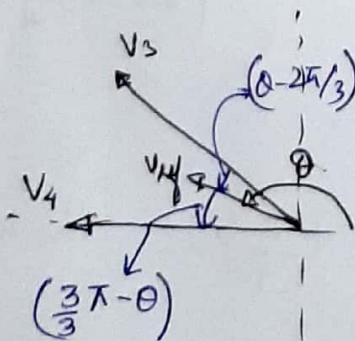


Sector 4:

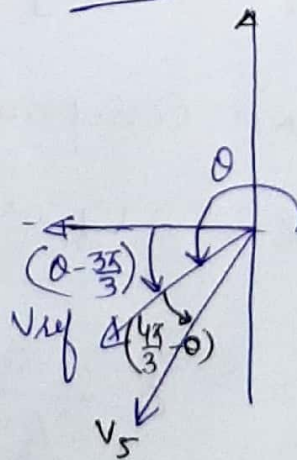

Sector 5:

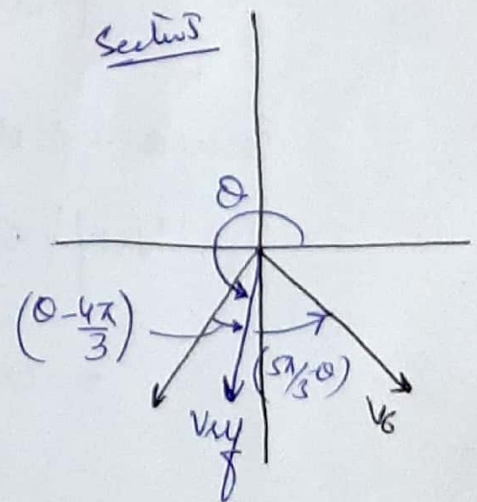

Sector 6:

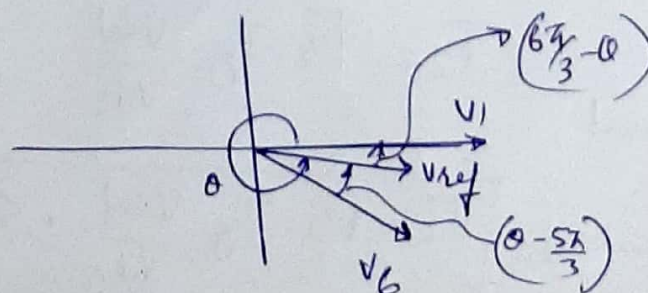

Sector	Angle b/w starting vector & ref	Angle b/w ref & ending vector
1	0	$\pi/3 - 0$
2	$0 - \pi/3$	$2\pi/3 - 0$
3	$0 - 2\pi/3$	$3\pi/3 - 0$
4	$0 - 3\pi/3$	$4\pi/3 - 0$
5	$0 - 4\pi/3$	$5\pi/3 - 0$
6	$0 - 5\pi/3$	$6\pi/3 - 0$

In general $\left[0 - \frac{n-1}{3} \pi \right] \quad \left[\frac{n\pi}{3} - 0 \right]$

We calculated the times of vectors in last lecture using

$$\vec{V}_{ref} \cdot T_g = \int_0^{T_1} V_1 dt + \int_{T_1}^{T_1+T_2} V_2 dt + \int_{T_1+T_2}^{T_1+T_2+T_0/2} V_0 dt + \int_{T_1+T_2+T_0/2}^{T_1+T_2+T_0} V_7 dt$$

$$\Rightarrow |V_{ref}| \begin{bmatrix} \cos \alpha \\ \sin \alpha \end{bmatrix} T_g = \frac{2}{3} V_{dc} \begin{bmatrix} 1 \\ 0 \end{bmatrix} T_1 + \frac{2}{3} V_{dc} \begin{bmatrix} \cos \pi/3 \\ \sin \pi/3 \end{bmatrix} T_2$$

Comparing 'y' axis components.

$$T_g \cdot |V_{ref}| \sin \alpha = \frac{2}{3} V_{dc} \cdot T_1 (0) + \frac{2}{3} V_{dc} \cdot \sin \pi/3 \cdot T_2$$

$$\Rightarrow T_2 = T_g \cdot \frac{|V_{ref}|}{\frac{2}{3} V_{dc}} \cdot \frac{\sin \alpha}{\sin \pi/3}$$

$$T_2 = \sqrt{3} \cdot T_g \cdot \frac{|V_{ref}|}{V_{dc}} \cdot \sin \alpha$$

In general.

$$T_2 = \sqrt{3} \cdot T_g \cdot \frac{|V_{ref}|}{V_{dc}} \cdot \sin \left(\alpha - \frac{n-1}{3} \pi \right)$$

Comparing 'α' axis components we get

(2)

$$T_3 \cdot |V_{ref}| \cos \alpha = \frac{2}{3} V_{dc} \cdot T_1 + \frac{2}{3} V_{dc} \cos \pi/3 \cdot T_2$$

using the value of T_2 and simplifying above expression one can get

$$T_1 = \sqrt{3} \cdot T_3 \frac{V_{ref}}{V_{dc}} \sin(\pi/3 - \alpha)$$





and in general

$$\boxed{T_1 = \sqrt{3} T_3 \frac{V_{ref}}{V_{dc}} \sin\left(\frac{n\pi}{3} - \alpha\right)}$$

Time of zero/null vectors can be calculated as

$$\boxed{T_0 = T_3 - T_1 - T_2}$$

Control Diagram.

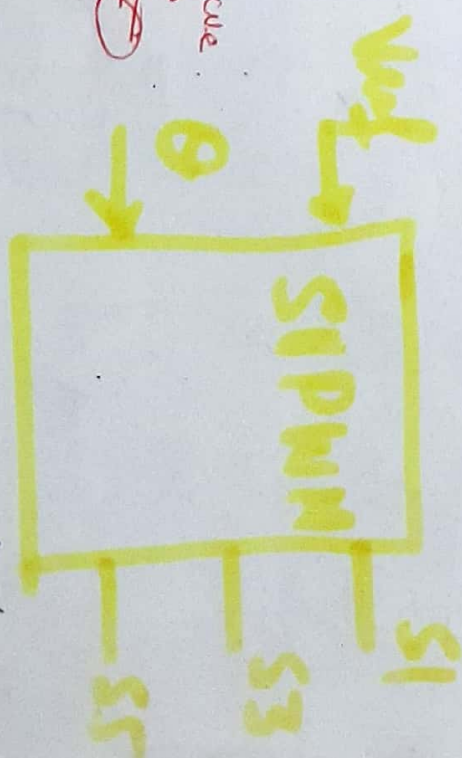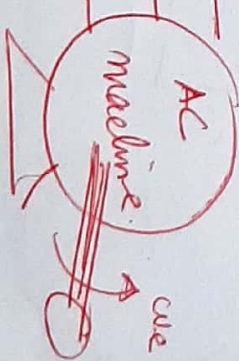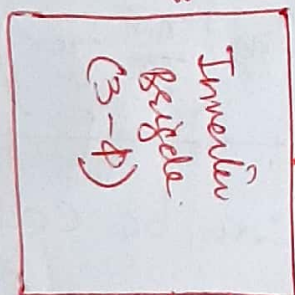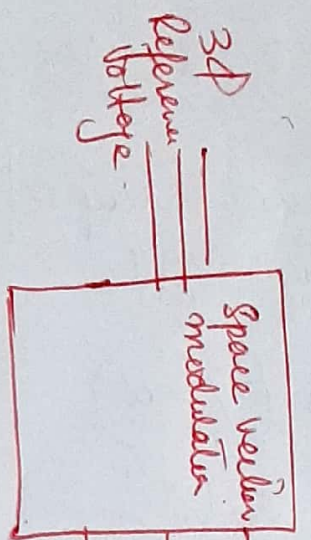

Same time this block is used.

