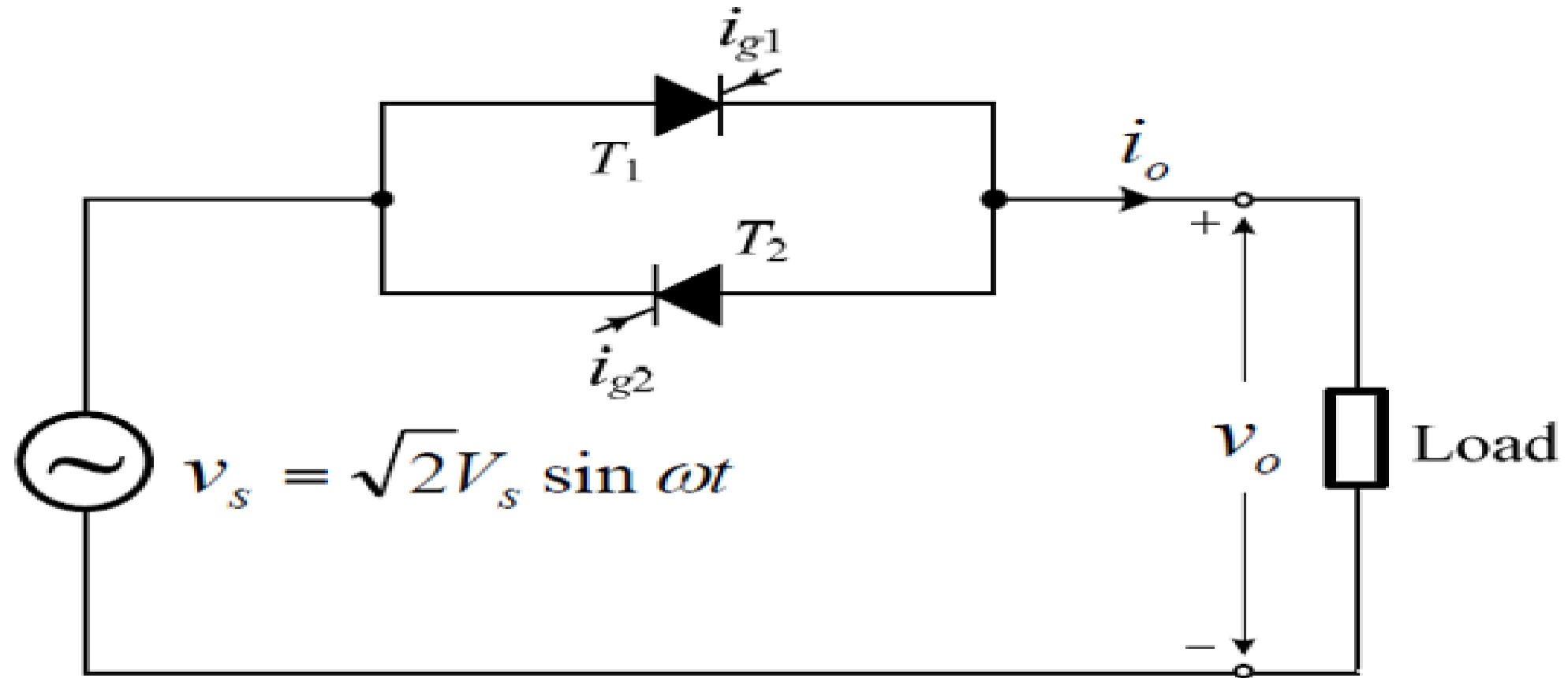


Lecture#

- 3-phase AC Voltage Controller with R load
- Numericals: 4-2 to 4-5

Q. Please design 3-phase AC Voltage Controller using 1-phase AC Voltage Controller?




Q. Also mention that where should we connect 3-phase AC Voltage Controller?

Answer:


- Between the 3-phase power supply and the load.

3-phase AC Voltage Controller

1-phase AC Voltage Controller

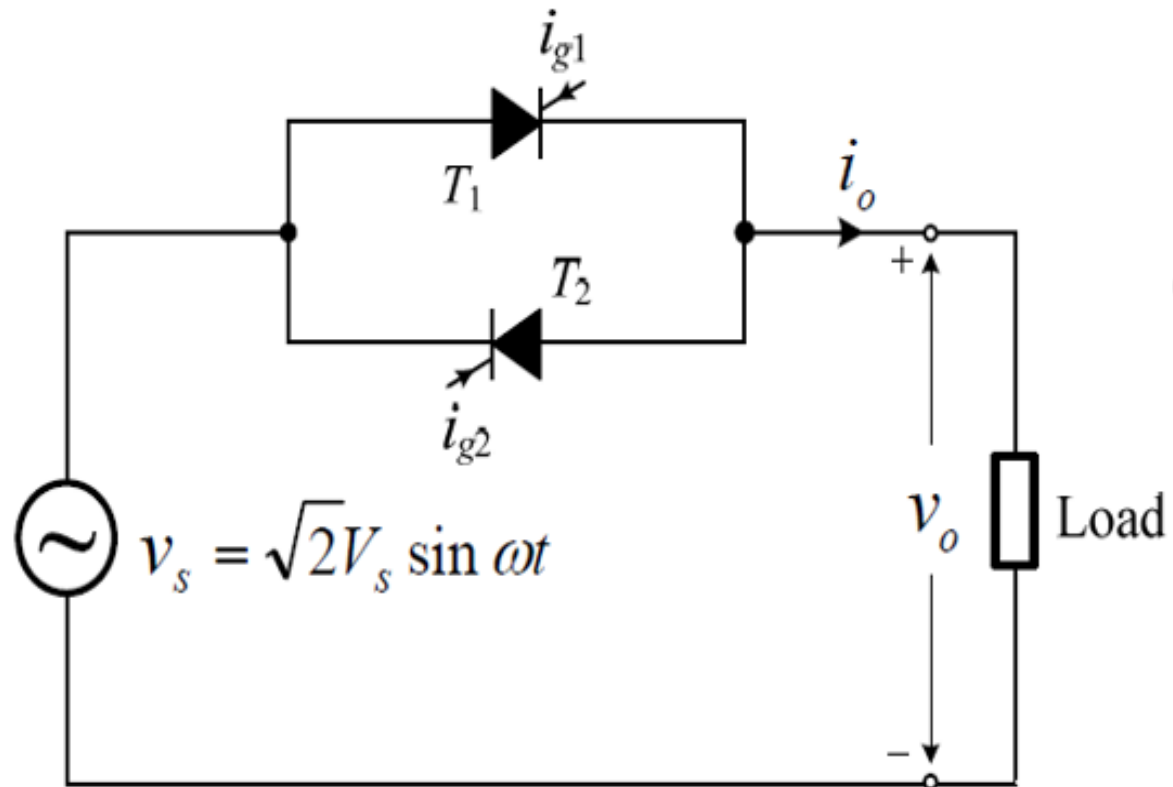

3-phase AC Voltage Controller

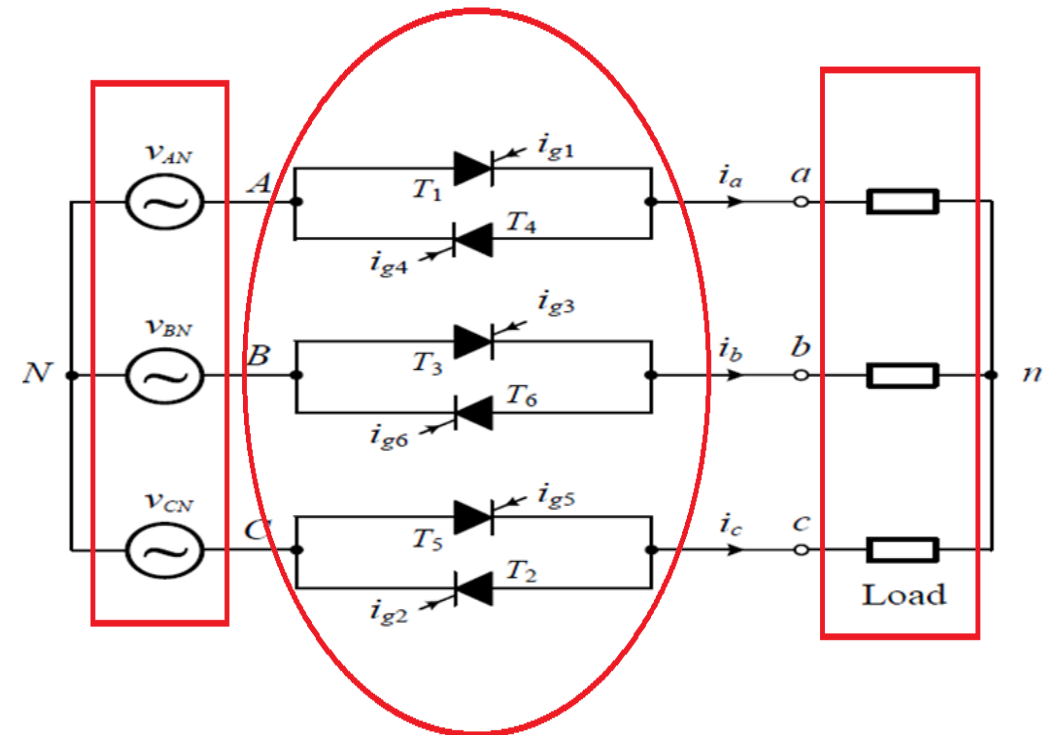


If we define instantaneous input phase voltages as:

$$v_{AN} = \sqrt{2}V_s \sin \omega t$$

$$v_{BN} = \sqrt{2}V_s \sin \left(\omega t - \frac{2\pi}{3} \right)$$
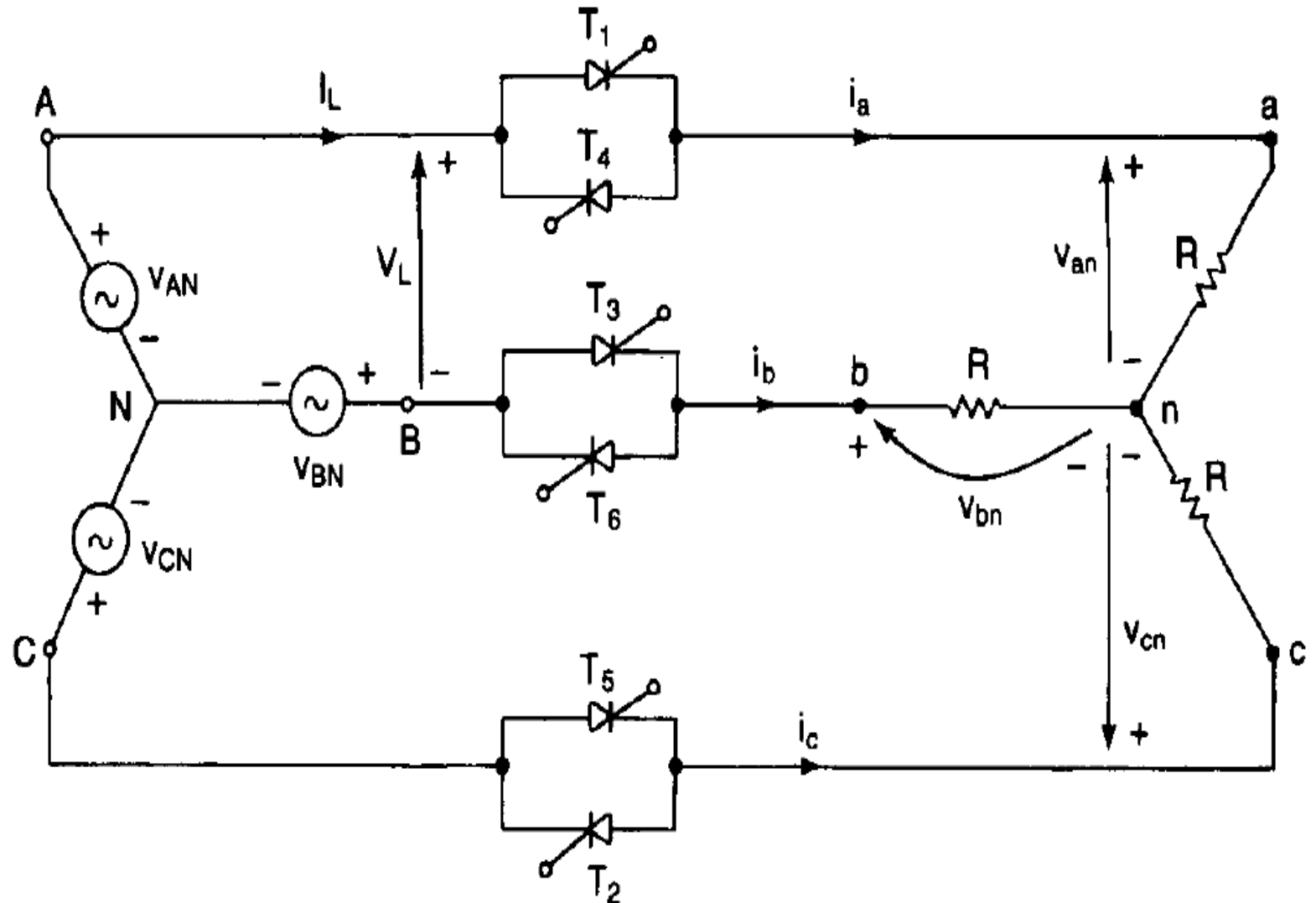
$$v_{CN} = \sqrt{2}V_s \sin \left(\omega t - \frac{4\pi}{3} \right)$$




Q. What would be the values of?

$$V_{AB} =$$


$$V_{BC} =$$

$$V_{CA} =$$

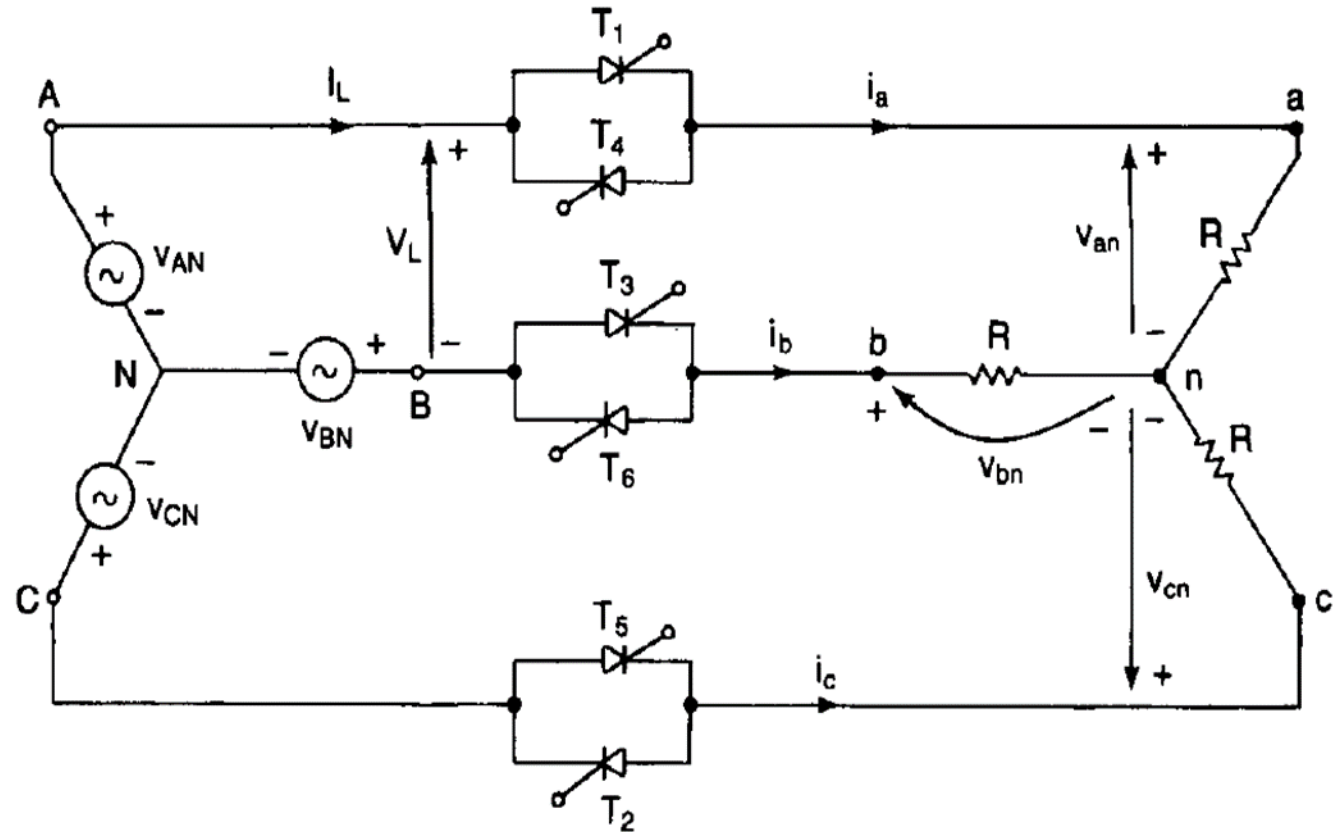

By applying KVL


$$V_{AB} = V_{AN} - V_{BN}$$

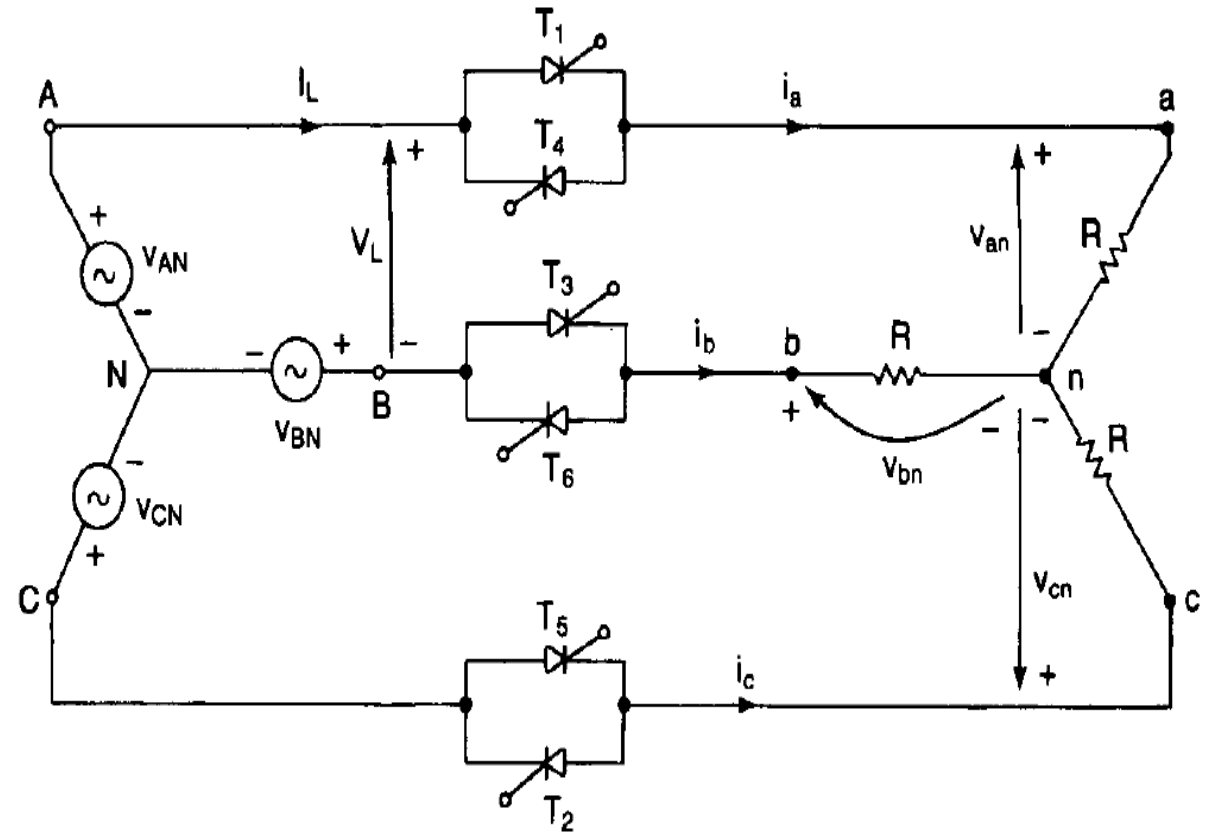

Similarly

$$V_{BC} = V_{BN} - V_{CN}$$

$$V_{CA} = V_{CN} - V_{AN}$$

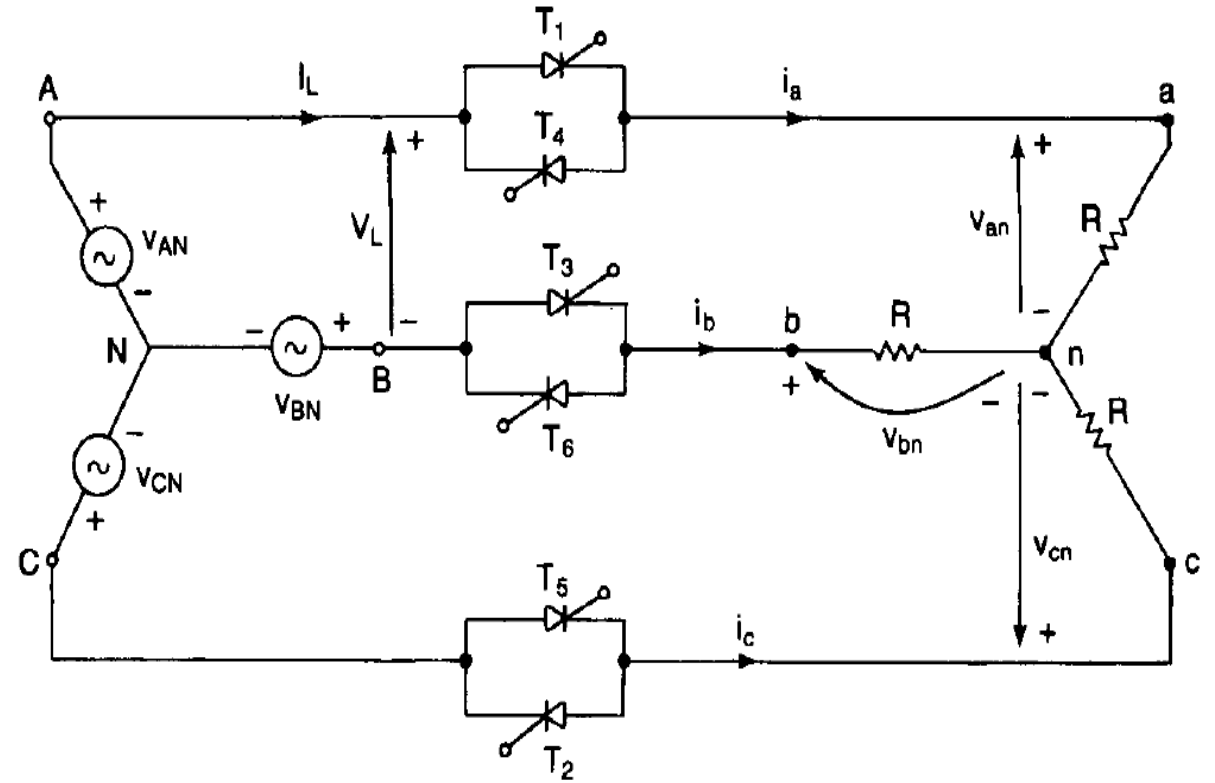

Please evaluate?

$$V_{AB} = V_{AN} - V_{BN}$$

where

$$v_{AN} = \sqrt{2}V_s \sin \omega t$$

$$v_{BN} = \sqrt{2}V_s \sin \left(\omega t - \frac{2\pi}{3} \right)$$

$$V_{AB} = V_{AN} + (-V_{BN})$$

$$V_{AB} = \sqrt{2}V_s [\text{Sin}(\omega t) - \text{Sin}(\omega t - \frac{2\pi}{3})]$$

$$\text{Sin}(a) - \text{Sin}(b) = 2 \text{Cos}(\frac{a+b}{2}) \text{Sin}(\frac{a-b}{2})$$

$$a = \omega t,$$

$$b = (\omega t - \frac{2\pi}{3})$$

$$(\frac{a+b}{2}) = (\omega t - \frac{\pi}{3}), \quad (\frac{a-b}{2}) = \frac{\pi}{3}$$

$$V_{AB} = \sqrt{2}V_s [2 \text{Cos}(\omega t - \frac{\pi}{3}) \text{Sin}(\frac{\pi}{3})]$$

$$V_{AB} = \sqrt{6}V_s \text{Cos}(\omega t - \frac{\pi}{3})$$

$$V_{AB} = \sqrt{6}V_s \text{Sin}(\omega t - \frac{\pi}{3} + \frac{\pi}{2})$$

$$V_{AB} = \sqrt{6}V_s \text{Sin}(\omega t + \frac{\pi}{6})$$

|

Similarly

$$V_{AB} = \sqrt{6} V_s \sin\left(\omega t + \frac{\pi}{6}\right)$$

$$v_{BC} = \sqrt{6} V_s \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$v_{CA} = \sqrt{6} V_s \sin\left(\omega t - \frac{7\pi}{6}\right)$$

Draw Waveforms for the supply voltages(V_{AN}, V_{BN}, V_{CN}) [$4\pi/3-2\pi/3-0=2\pi/3=120^\circ$ i.e all are 120° apart from each other.]

$$v_{AN} = \sqrt{2}V_s \sin \omega t$$


$$v_{BN} = \sqrt{2}V_s \sin \left(\omega t - \frac{2\pi}{3} \right)$$

$$v_{CN} = \sqrt{2}V_s \sin \left(\omega t - \frac{4\pi}{3} \right)$$

$$v_{AN} = \sqrt{2}V_s \sin \omega t$$

$$v_{BN} = \sqrt{2}V_s \sin \left(\omega t - \frac{2\pi}{3} \right)$$
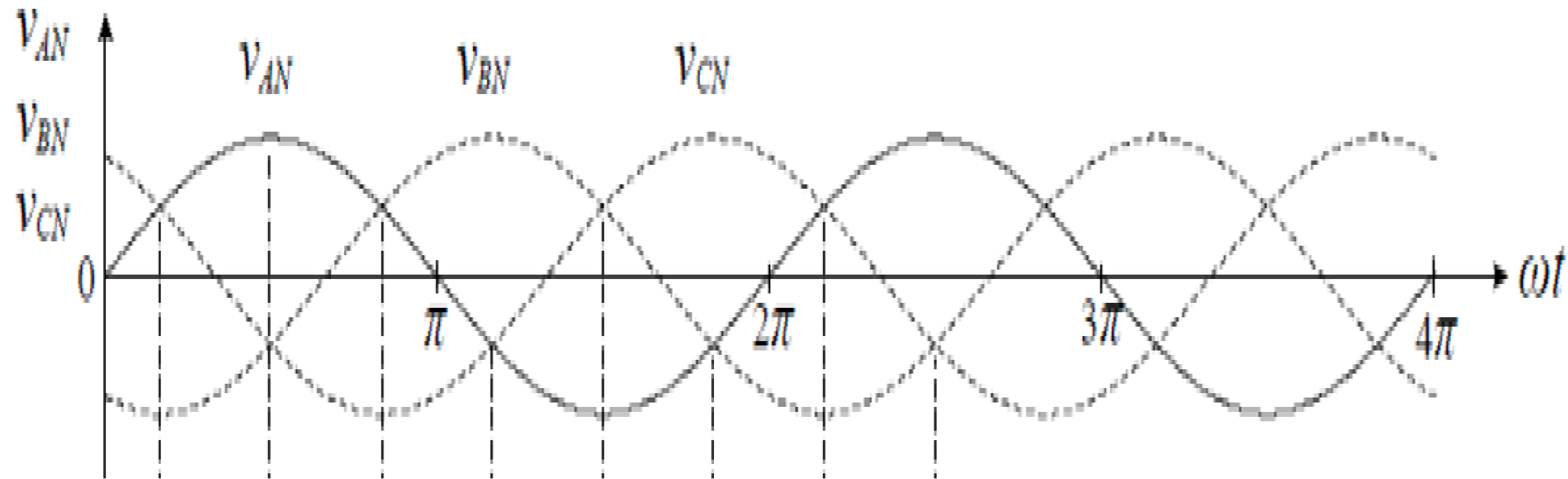
$$v_{CN} = \sqrt{2}V_s \sin \left(\omega t - \frac{4\pi}{3} \right)$$



Line-line voltages

$$V_{AB} = \sqrt{6} V_s \sin\left(\omega t + \frac{\pi}{6}\right)$$

$$v_{BC} = \sqrt{6} V_s \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$v_{CA} = \sqrt{6} V_s \sin\left(\omega t - \frac{7\pi}{6}\right)$$

Can we change the angle of V_{CA} ?

$$v_{CA} = \sqrt{6} V_s \sin \left(\omega t - \frac{7\pi}{6} \right)$$

Angle of V_{CA} can be changed by adding π

$$V_{CA} = \sqrt{6}V_s \sin(\omega t - \frac{7\pi}{6})$$


$$V_{AC} = \sqrt{6}V_s \sin(\omega t - \frac{7\pi}{6} + \pi)$$

$$V_{AC} = \sqrt{6}V_s \sin(\omega t - \frac{\pi}{6})$$


$$V_{AB} = \sqrt{6}V_s \sin(\omega t + \frac{\pi}{6})$$

$$V_{BC} = \sqrt{6}V_s \sin(\omega t - \frac{\pi}{2})$$
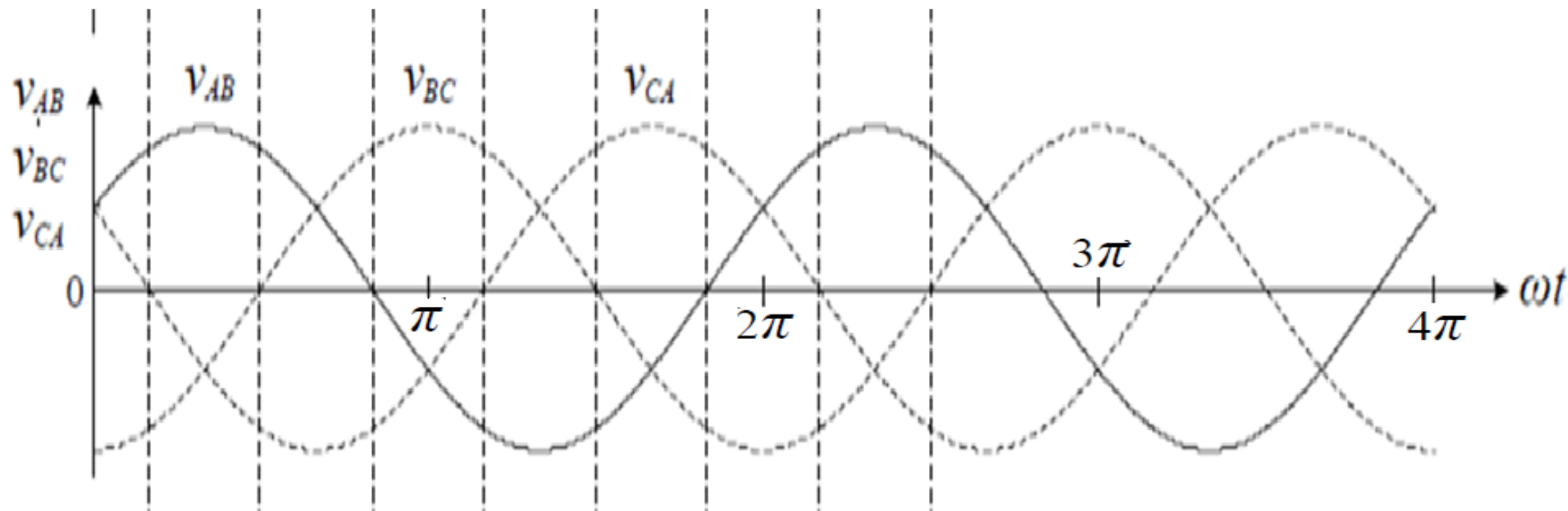
$$V_{AC} = \sqrt{6}V_s \sin(\omega t - \frac{\pi}{6})$$




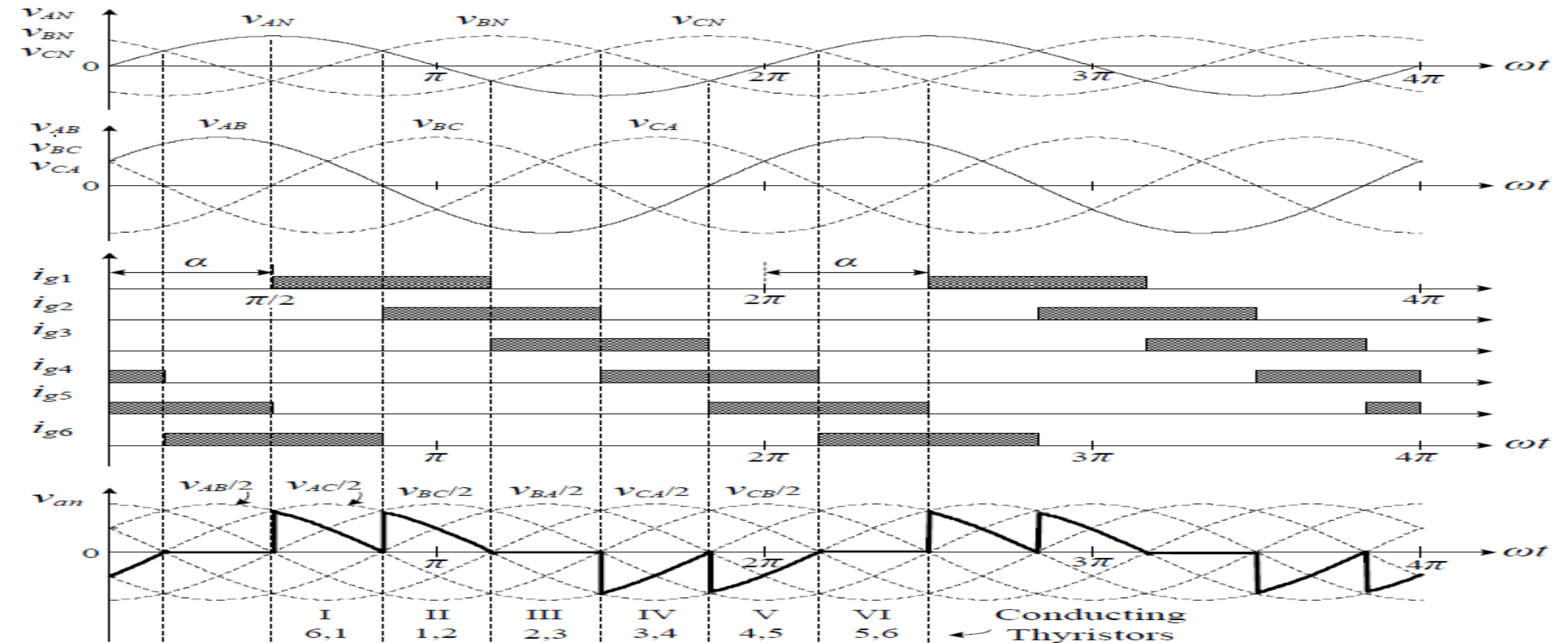Waveforms for supply voltages (V_{AN}, V_{BN}, V_{CN}), thyristor gating currents (ig_1 to ig_6), & phase- a load voltage v_{an}




During period I: $v_{an} = v_{AB}/2$

- Thyristors T_6 & T_1 are turned ON.
- Line-to-line supply voltage v_{AB} is applied to phase- a & b load resistors.
- Since T_5 & T_2 in phase- c are both off, phase- a load voltage $v_{an} = v_{AB}/2$

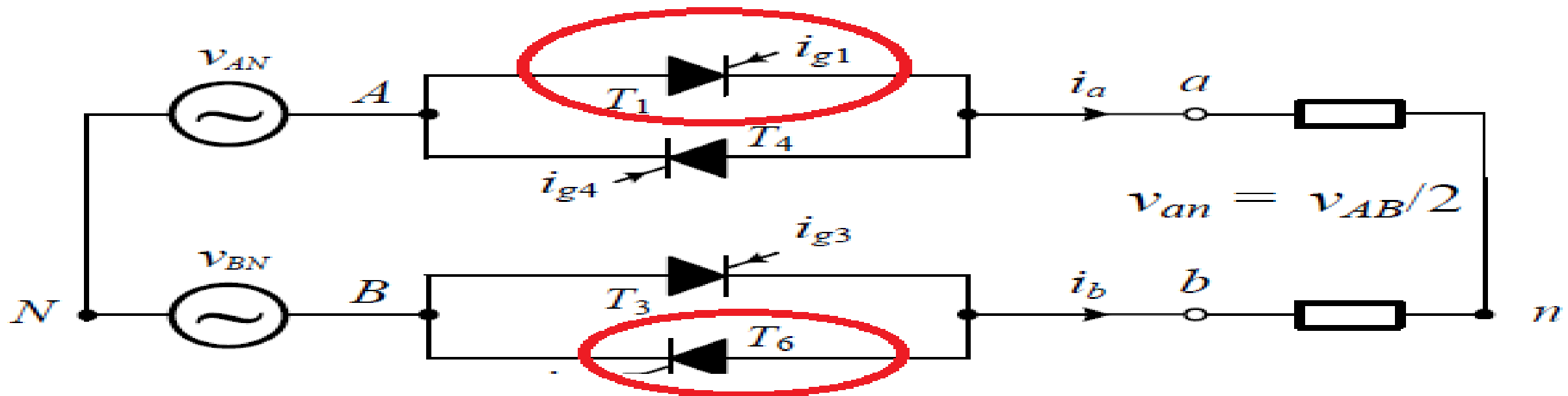


Period II: $v_{an} = v_{AC}/2$

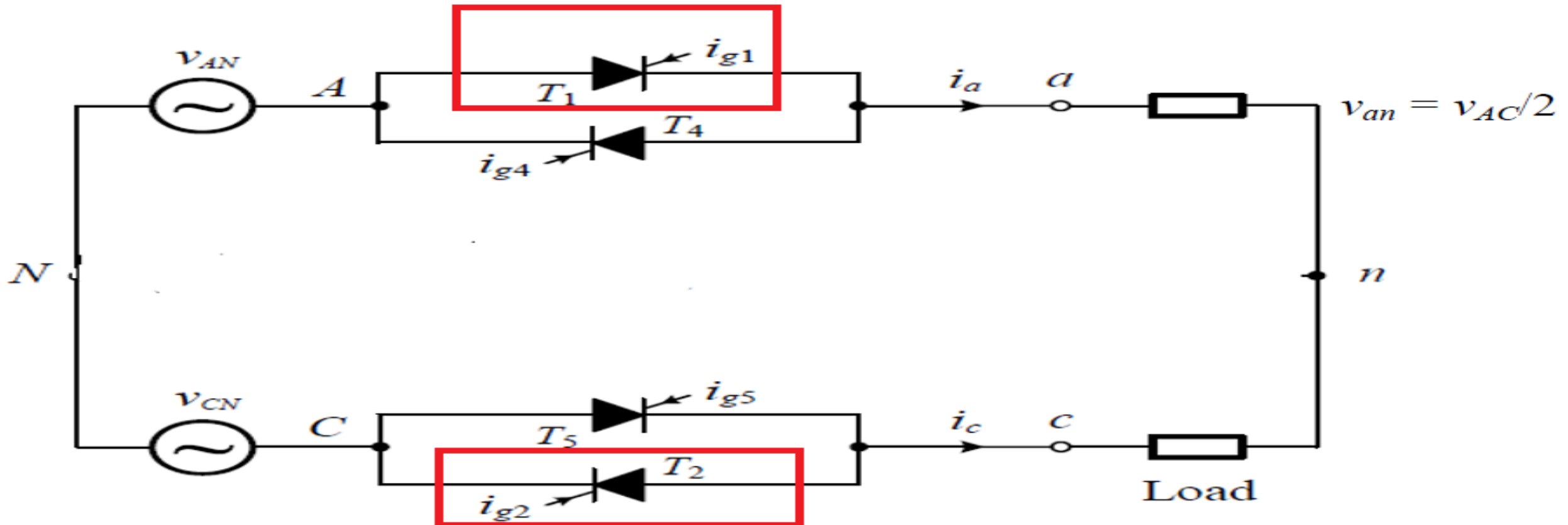- Thyristors T_1 & T_2 conduct, leading to $v_{an} = v_{AC}/2$




Period-III(Thyristors T_2 & T_3 are turned on)

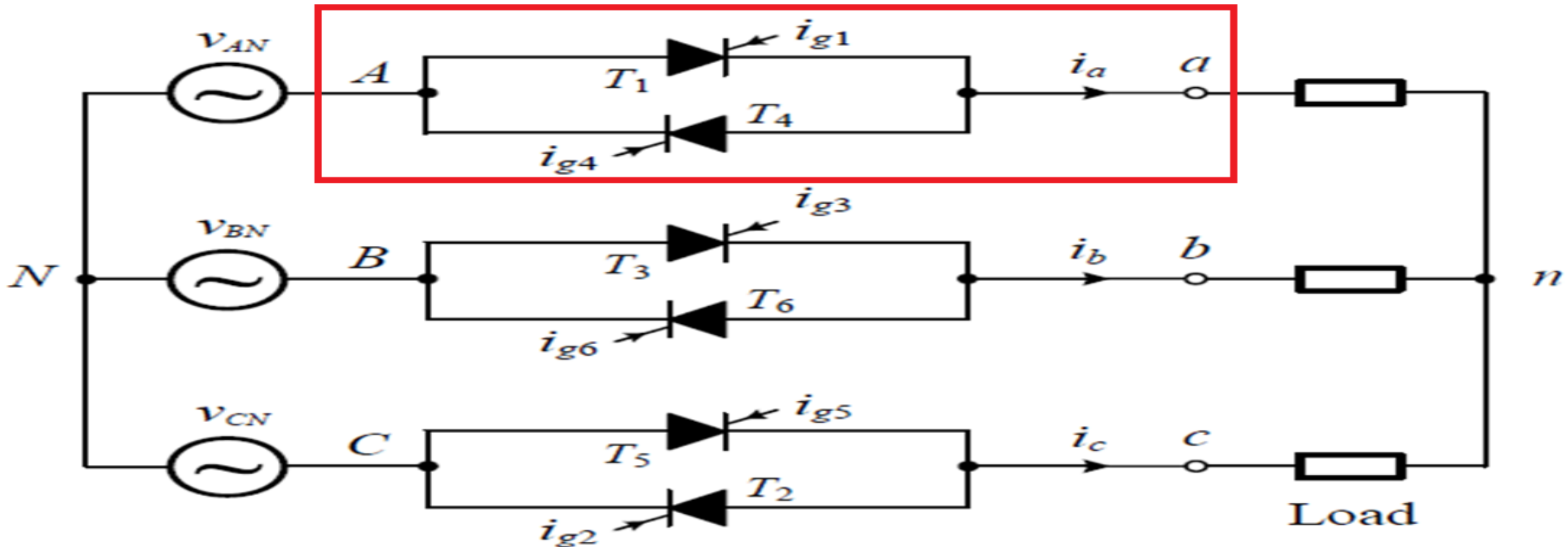
- None of the phase- a thyristors(T_1 & T_4) is ON, so $v_{an} = 0$.



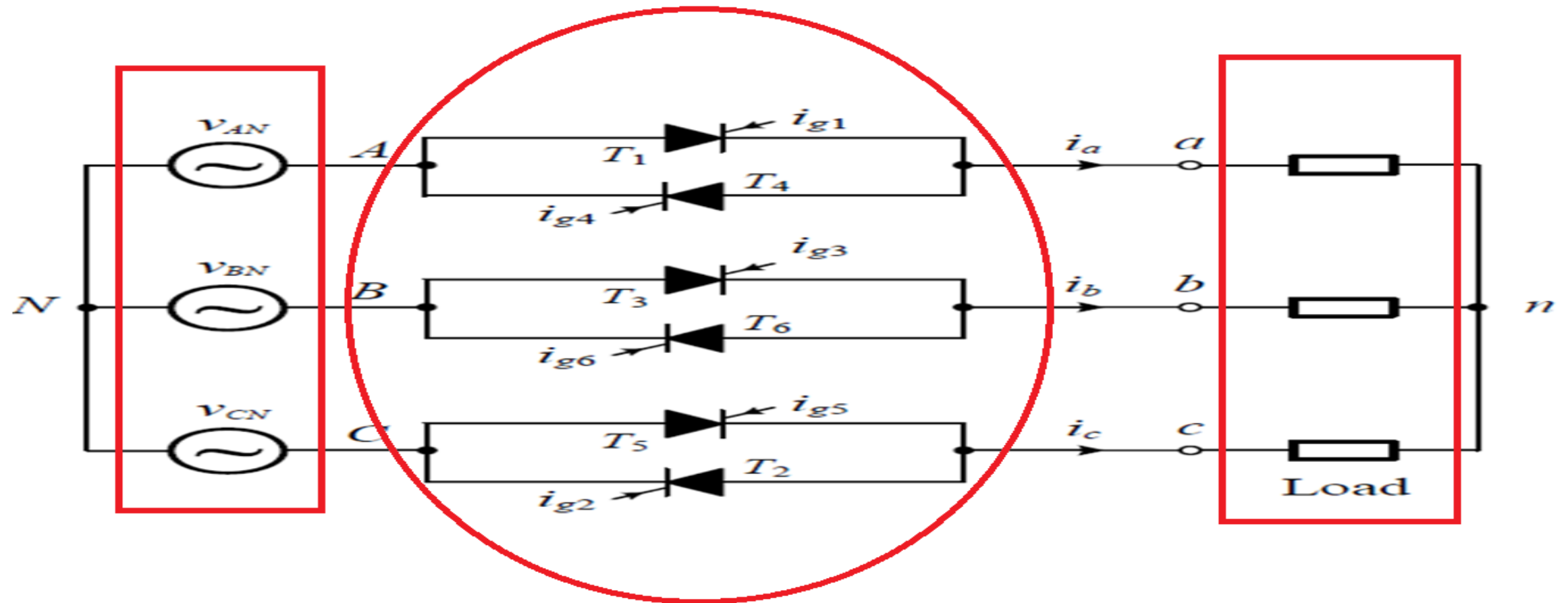
The operating principle of the controller



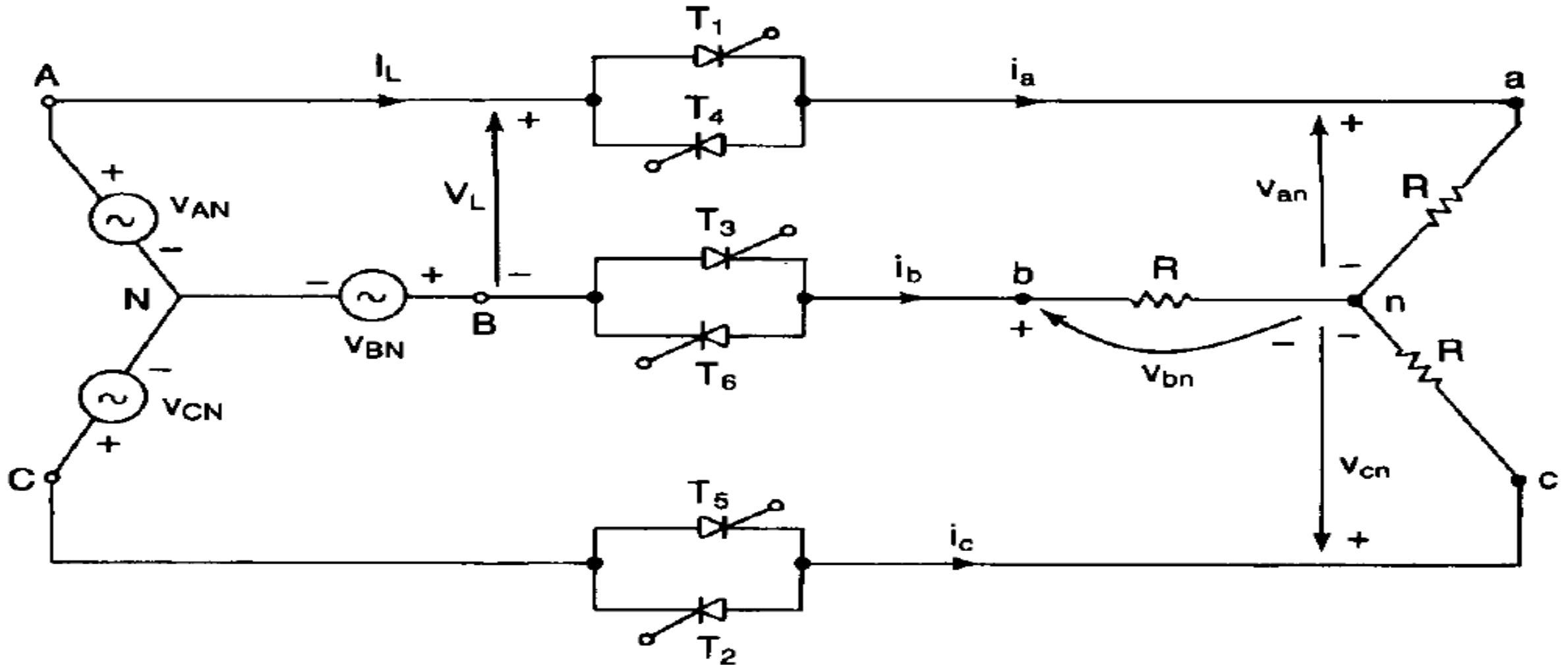Waveforms for load line-to-line voltages (v_{ab} , v_{bc} , v_{ca}):
 $v_{ab} = (v_{an} - v_{bn})$, $v_{bc} = (v_{bn} - v_{cn})$, and $v_{ca} = (v_{cn} - v_{an})$




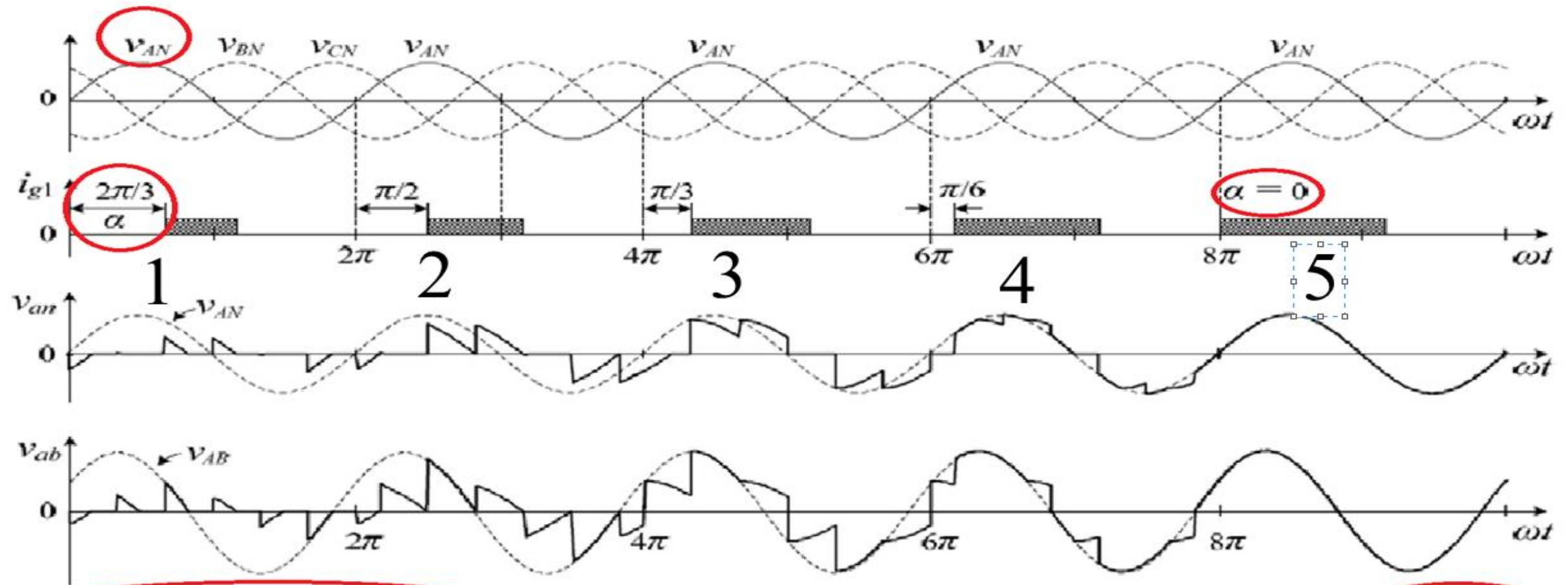Waveforms for v_{an} & v_{ab} with delay angle α changes from $2\pi/3=120^\circ$ to 0 in steps. $[(\pi/2-2\pi/3)=(\pi/2-\pi/3)=(\pi/3-\pi/6)=(\pi/6-0)=\pi/6=30^\circ]$




Delay angle: $\alpha = 2\pi/3$ (1st cycle), $\pi/2$ (2nd cycle), $\pi/3$ (3rd cycle), $\pi/6$ (4th cycle) and 0 (5th cycle)

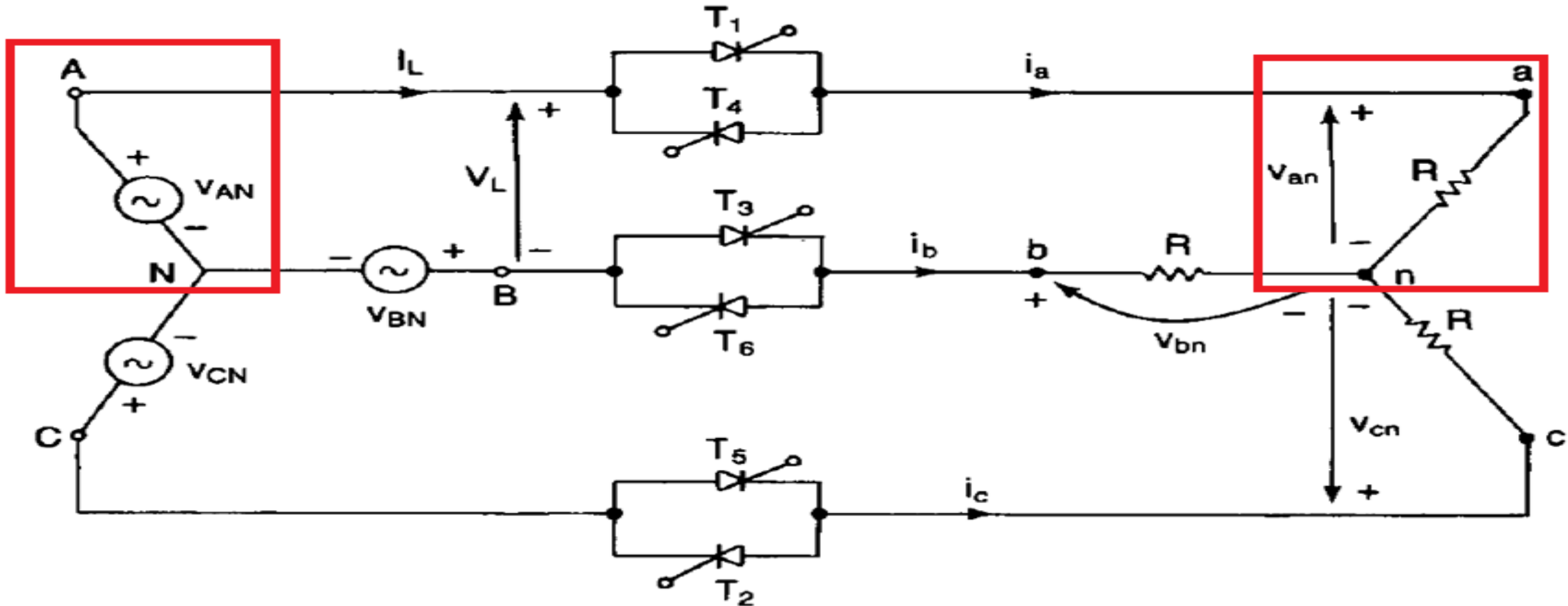At what value of α : Supply phase voltage = Load phase voltage
 i.e $v_{an} = v_{AN}$ & $v_{ab} = v_{AB}$ ($\alpha = 0^\circ, 30^\circ, 60^\circ, 90^\circ, 120^\circ = ?$)



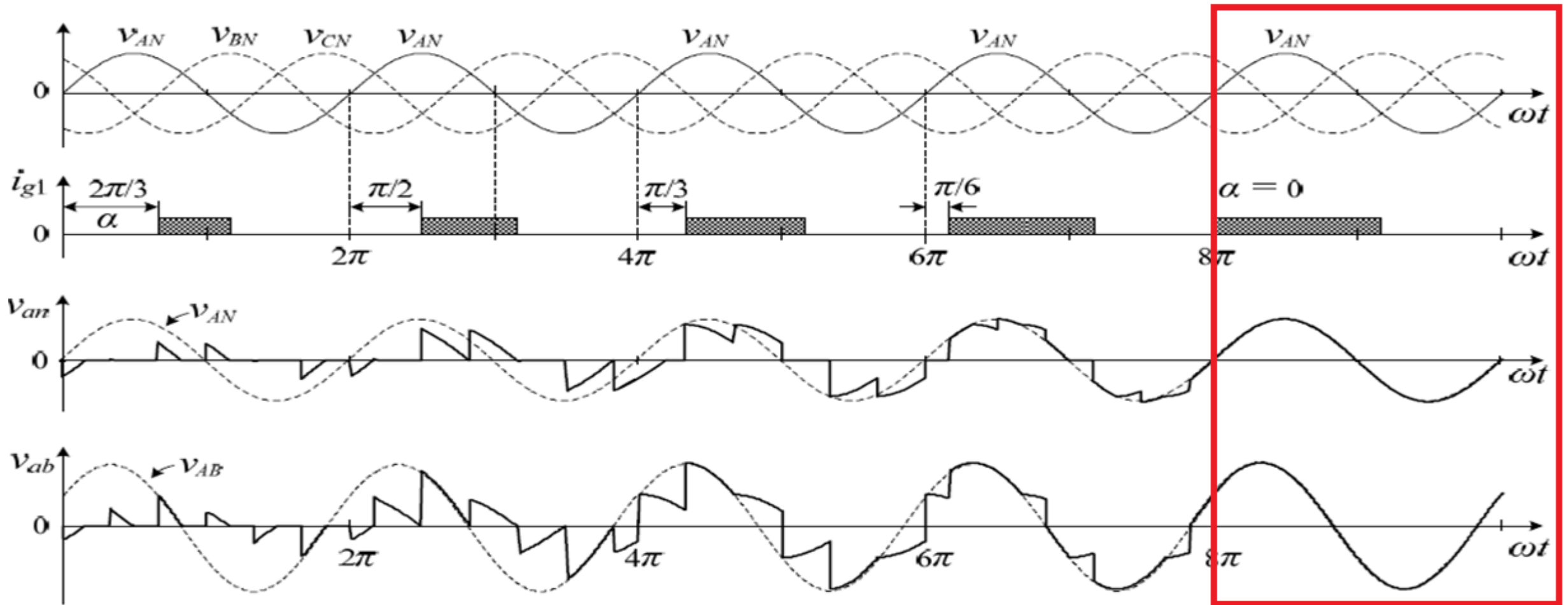By decreasing delay angle α , load phase voltage v_{an} & line-to-line voltage v_{ab} increase accordingly. So at $\alpha = 0$ Supply phase voltage = Load phase voltage i.e $v_{an} = v_{AN}$ and $v_{ab} = v_{AB}$



Delay angle: $\alpha = 2\pi/3$ (1st cycle), $\pi/2$ (2nd cycle), $\pi/3$ (3rd cycle), $\pi/6$ (4th cycle) and 0 (5th cycle)


Depending on delay angle α , operation of 3-phase AC voltage controller can be classified into 3 operating modes.

1. Mode I for $\pi/2 \leq \alpha < 5\pi/6$, during which there are periods when none or 2 thyristors in each phase conduct;
2. Mode II for $\pi/3 \leq \alpha < \pi/2$, during which 2 thyristors in each phase are turned on &
3. Mode III for $0 \leq \alpha < \pi/3$, during which 3 thyristors or 2 thyristors conduct simultaneously .

No need to extend delay angle(α) beyond $5\pi/6$ (150°)?


- Delay angle α is in range of 0 to π , in 1-phase AC voltage controller.
- Delay angle α is in range of 0 to $5\pi/6$ (150°) in 3-phase AC voltage controller
- Beyond which ($5\pi/6 < \alpha \leq \pi$) output voltage of controller is kept 0.

Mode I for $\pi/2 \leq \alpha < 5\pi/6$

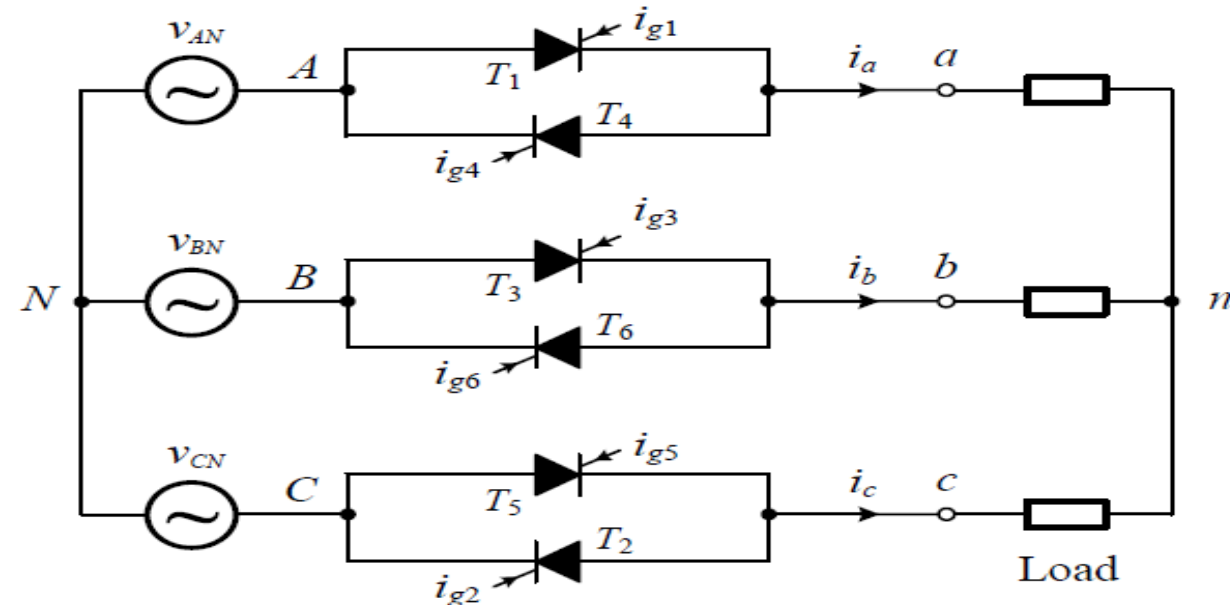


$$\frac{V_{AB}}{2} = \frac{\sqrt{6}}{2} V_s \sin(\omega t + \frac{\pi}{6})$$
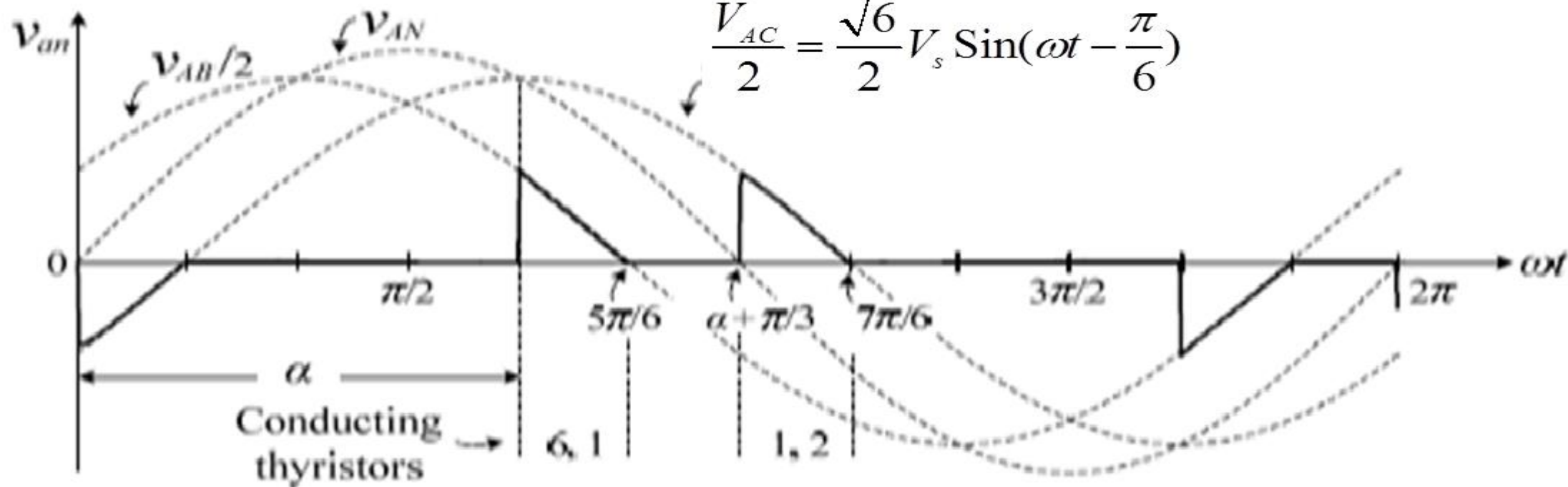
$$\frac{V_{AC}}{2} = \frac{\sqrt{6}}{2} V_s \sin(\omega t - \frac{\pi}{6})$$




(a) $\alpha = 2\pi/3$ (120°, Mode I)

Find $V_{an}=?$

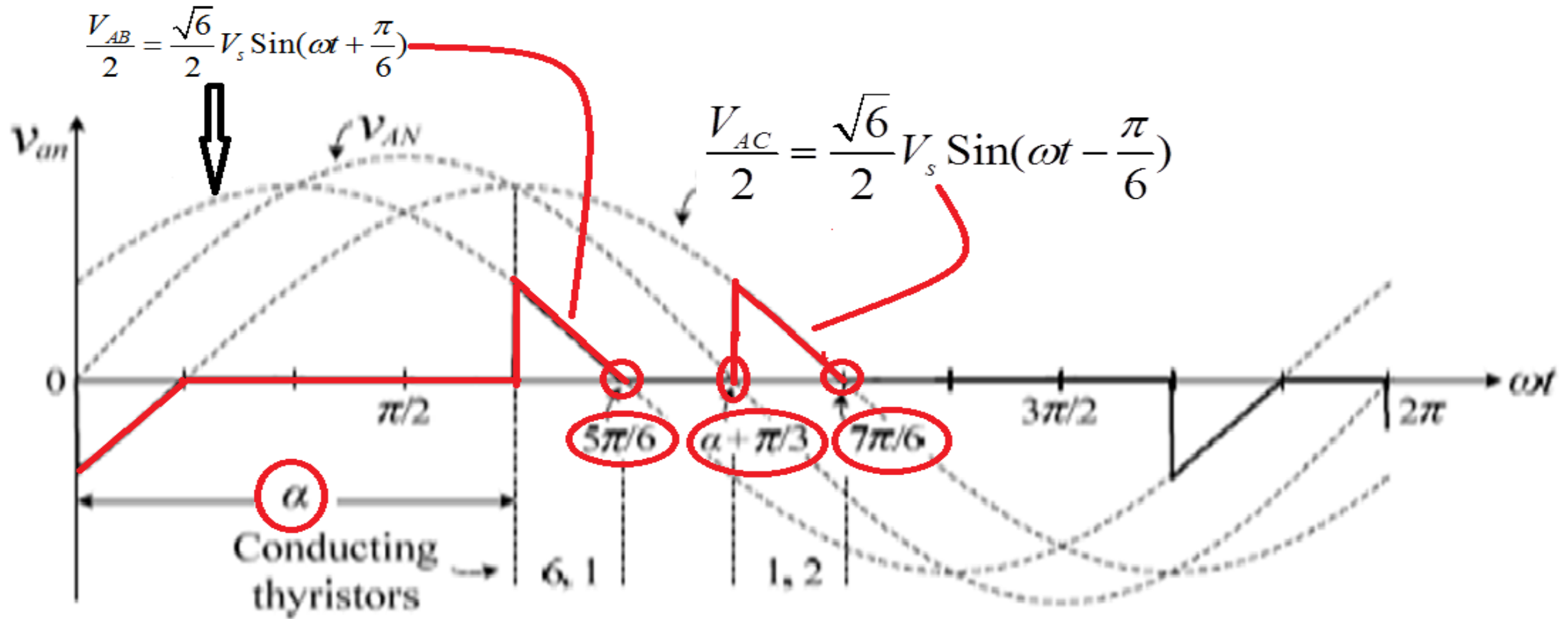

(a) $\alpha = 2\pi/3$ (120° , Mode I)

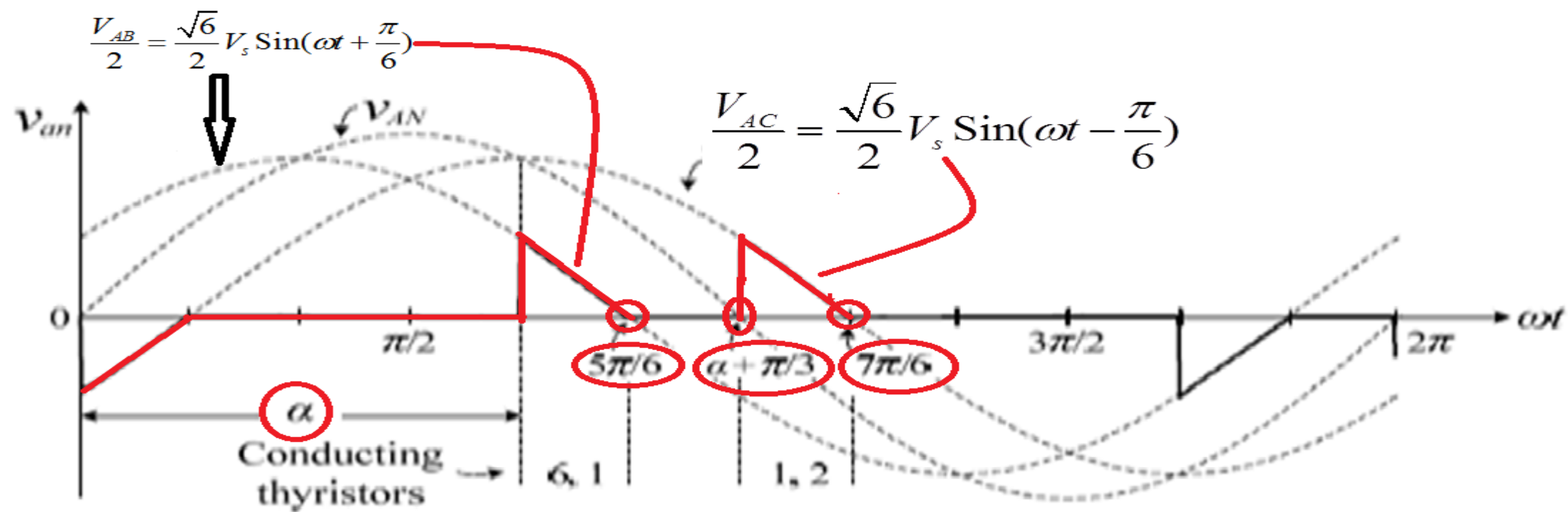


(a) $\alpha = 2\pi/3$ (120°, Mode I)

$$\begin{aligned}
 V_{an} &= \left(\frac{1}{\pi} \left(\int_{\alpha}^{5\pi/6} \left(\frac{\sqrt{6}}{2} V_s \sin(\omega t + \pi/6) \right)^2 d(\omega t) + \int_{\alpha + \pi/3}^{7\pi/6} \left(\frac{\sqrt{6}}{2} V_s \sin(\omega t - \pi/6) \right)^2 d(\omega t) \right) \right)^{1/2} \\
 &= V_s \left(\frac{5}{4} - \frac{3\alpha}{2\pi} + \frac{3 \sin(2\alpha + \pi/3)}{4\pi} \right)^{1/2} \quad \text{for Mode I } (\pi/2 \leq \alpha < 5\pi/6)
 \end{aligned}$$


Mode II for $\pi/3 \leq \alpha < \pi/2$

Mode II for $\pi/3 \leq \alpha < \pi/2$

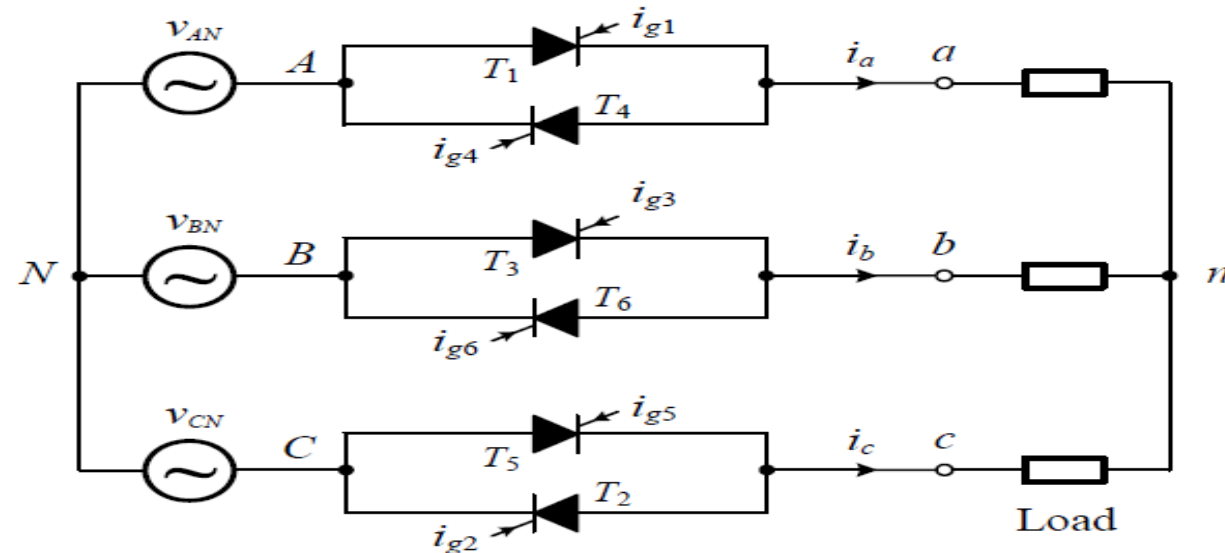

$$\frac{V_{AB}}{2} = \frac{\sqrt{6}}{2} V_s \sin(\omega t + \frac{\pi}{6})$$

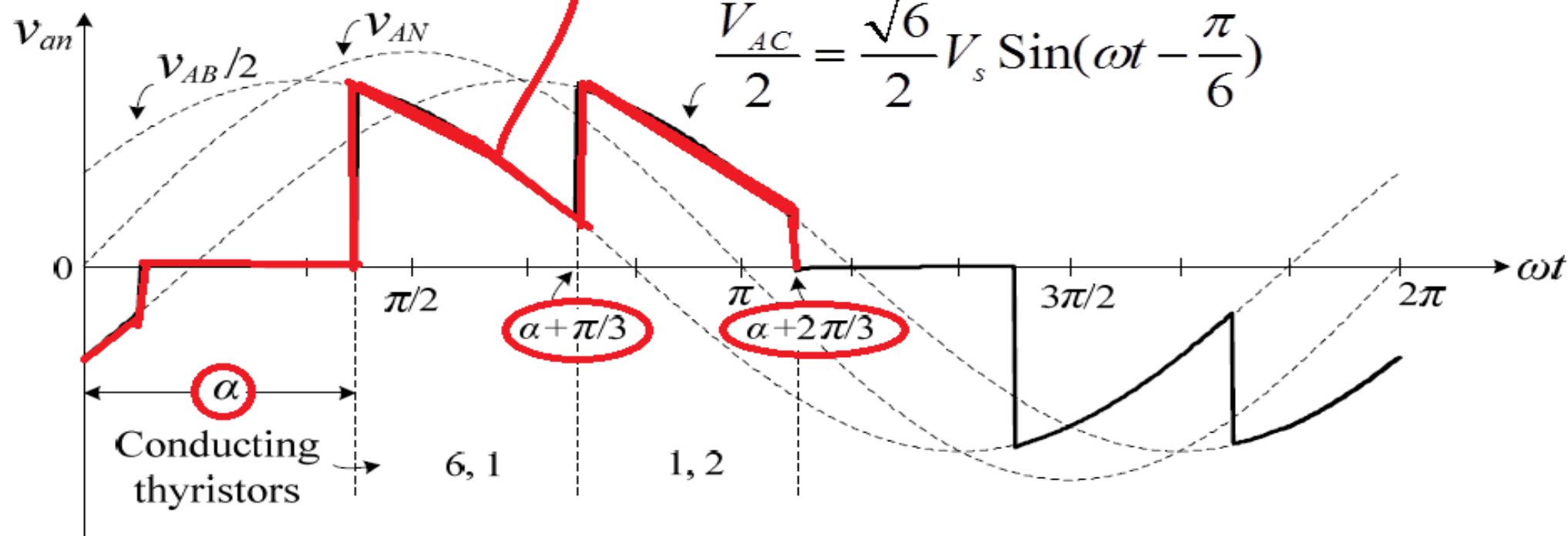
$$\frac{V_{AC}}{2} = \frac{\sqrt{6}}{2} V_s \sin(\omega t - \frac{\pi}{6})$$




Find $V_{an}=?$

$$\frac{V_{AB}}{2} = \frac{\sqrt{6}}{2} V_s \sin\left(\omega t + \frac{\pi}{6}\right)$$
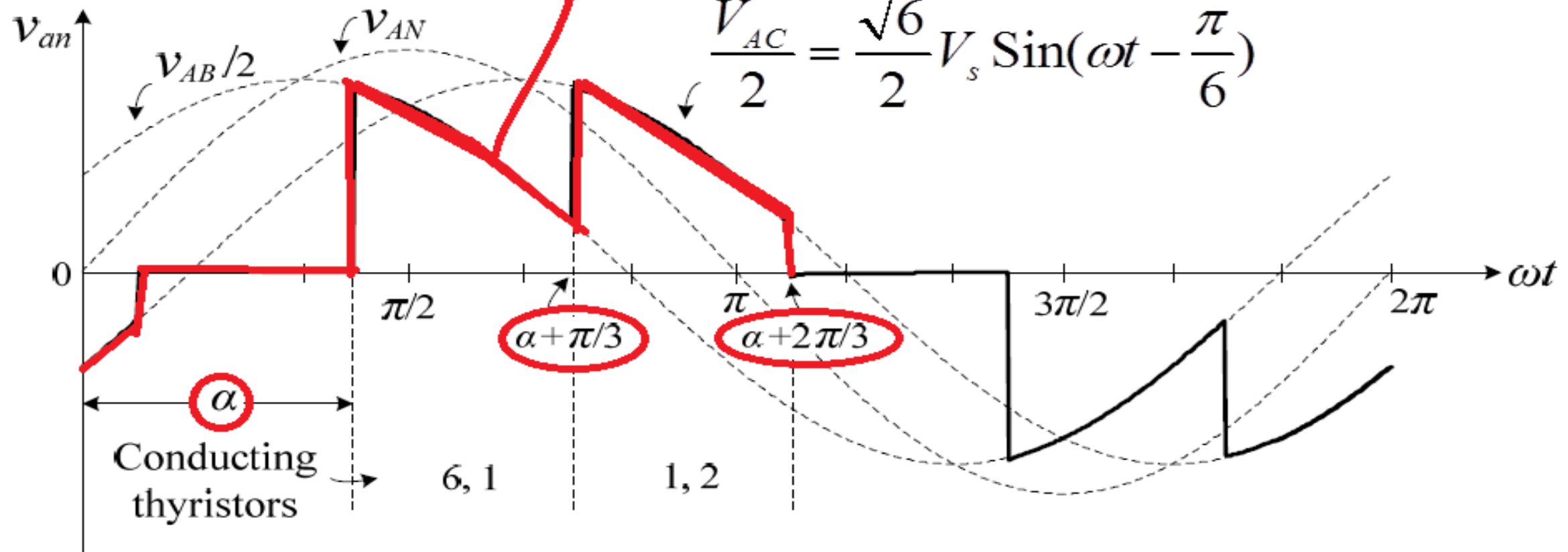
$$\frac{V_{AC}}{2} = \frac{\sqrt{6}}{2} V_s \sin\left(\omega t - \frac{\pi}{6}\right)$$


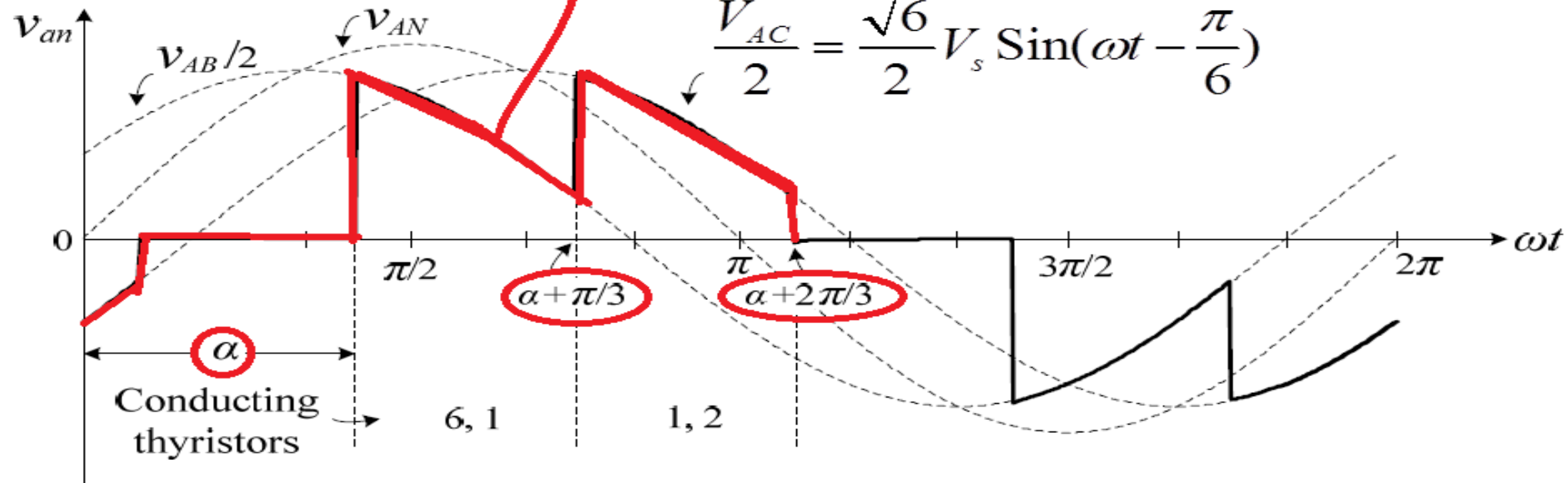
$$\frac{V_{AB}}{2} = \frac{\sqrt{6}}{2} V_s \sin(\omega t + \frac{\pi}{6})$$





$$V_{an} = \left(\frac{1}{\pi} \left(\int_{\alpha}^{\alpha + \pi/3} \left(\frac{\sqrt{6}}{2} V_s \sin(\omega t + \pi/6) \right)^2 d(\omega t) + \int_{\alpha + \pi/3}^{\alpha + 2\pi/3} \left(\frac{\sqrt{6}}{2} V_s \sin(\omega t - \pi/6) \right)^2 d(\omega t) \right) \right)^{1/2}$$

$$= V_s \left(\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \sin(2\alpha + \pi/6) \right)^{1/2} \quad \text{for Mode II } (\pi/3 \leq \alpha < \pi/2)$$

Mode III for $0 \leq \alpha < \pi/3$

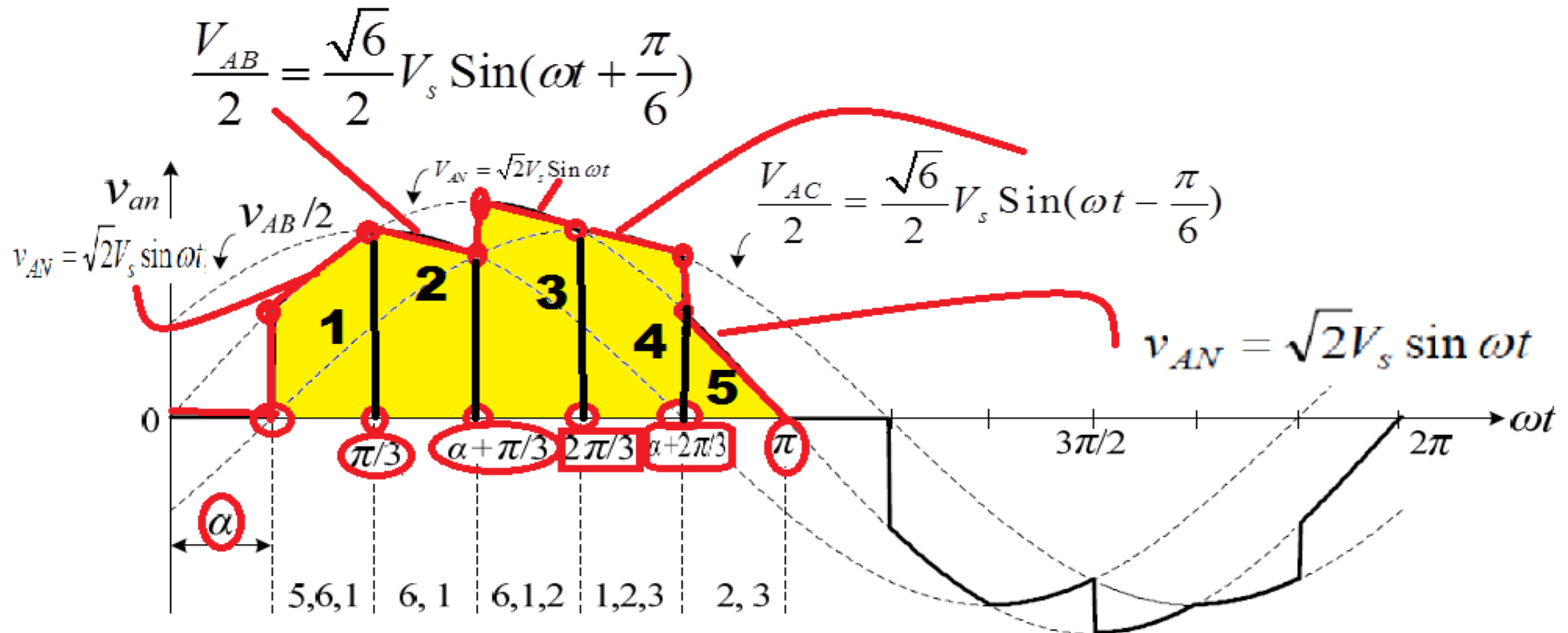Find v_{an} for in Mode III, where delay angle $\pi/6 = (30^\circ)$?



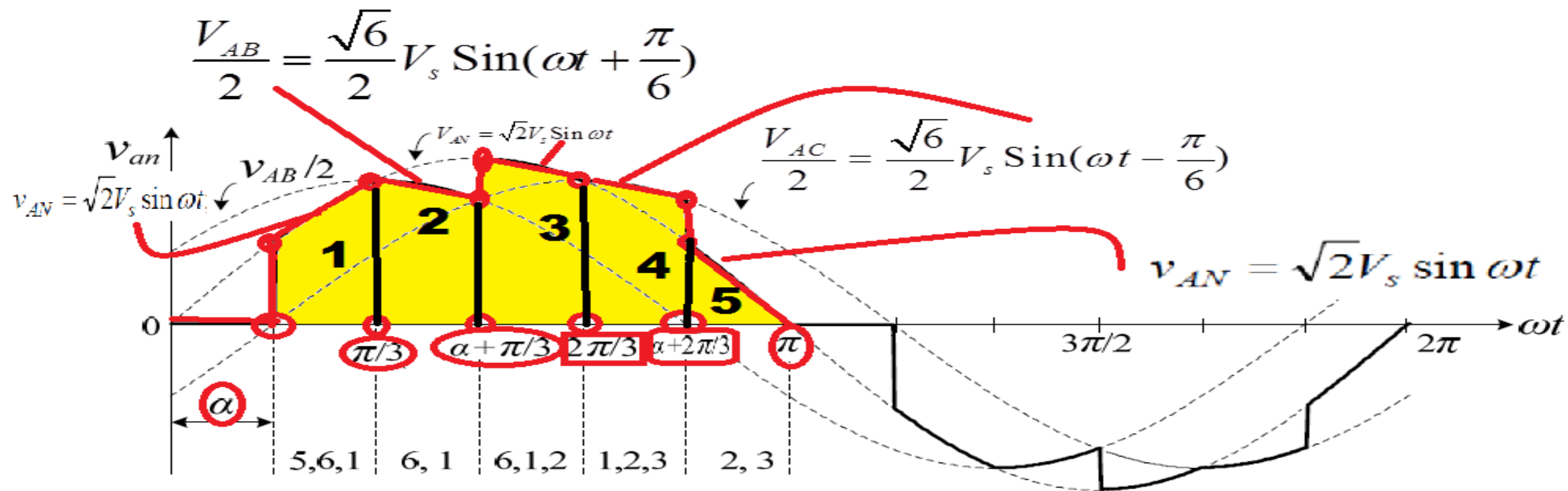

$$\begin{aligned}
 V_{an} = & \left(\frac{1}{\pi} \left(\int_{\alpha}^{\pi/3} (\sqrt{2} V_s \sin \omega t)^2 d(\omega t) + \int_{\pi/3}^{\alpha+\pi/3} \left(\frac{\sqrt{6}}{2} V_s \sin(\omega t + \pi/6) \right)^2 d(\omega t) + \int_{\alpha+\pi/3}^{2\pi/3} (\sqrt{2} V_s \sin \omega t)^2 d(\omega t) + \right. \right. \\
 & \left. \left. \int_{2\pi/3}^{\alpha+2\pi/3} \left(\frac{\sqrt{6}}{2} V_s \sin(\omega t - \pi/6) \right)^2 d(\omega t) + \int_{\alpha+2\pi/3}^{\pi} (\sqrt{2} V_s \sin \omega t)^2 d(\omega t) \right) \right)^{1/2}
 \end{aligned}$$

4 **5**


van for in Mode III

$$V_{an} = V_s \left(1 - \frac{3\alpha}{2\pi} + \frac{3\sin 2\alpha}{4\pi} \right)^{1/2} \quad \text{for Mode III } (0 \leq \alpha < \pi/3)$$


03-phase AC voltage controller with inductive load

- Analysis of 3-phase AC voltage controller with inductive load is quite complex since thyristors do not cease conducting when supply voltage falls down to 0 & becomes -ve, the same phenomenon as discussed in single-phase AC voltage controller.
- Computer simulation provides an effective means of obtaining load voltage & current waveforms.

Fig. shows simulated waveforms for phase- a load voltage v_{an} , line-to-line voltage v_{ab} & load current i_a when voltage controller operates with a 3-phase Y-connected RL load having a power factor of 0.9 at different delay angles.

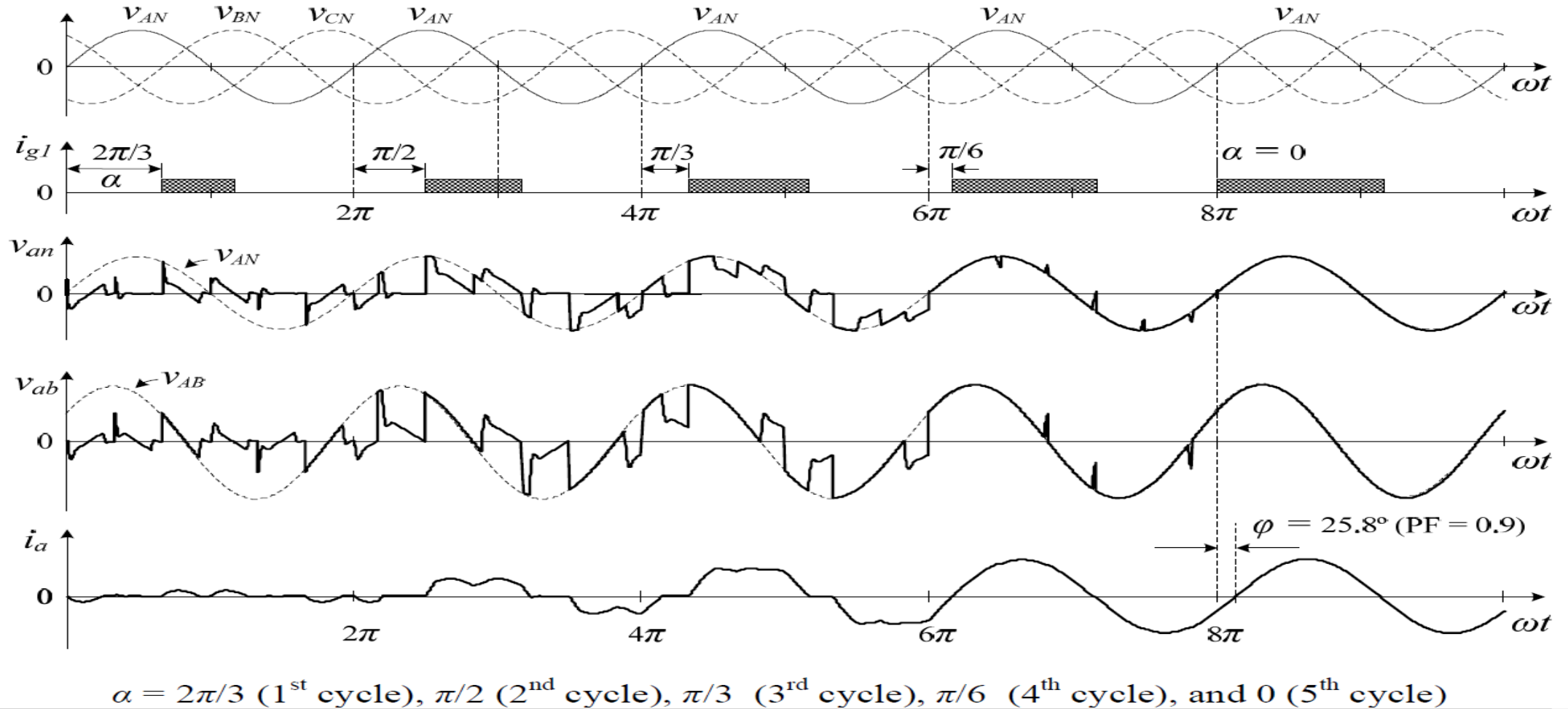

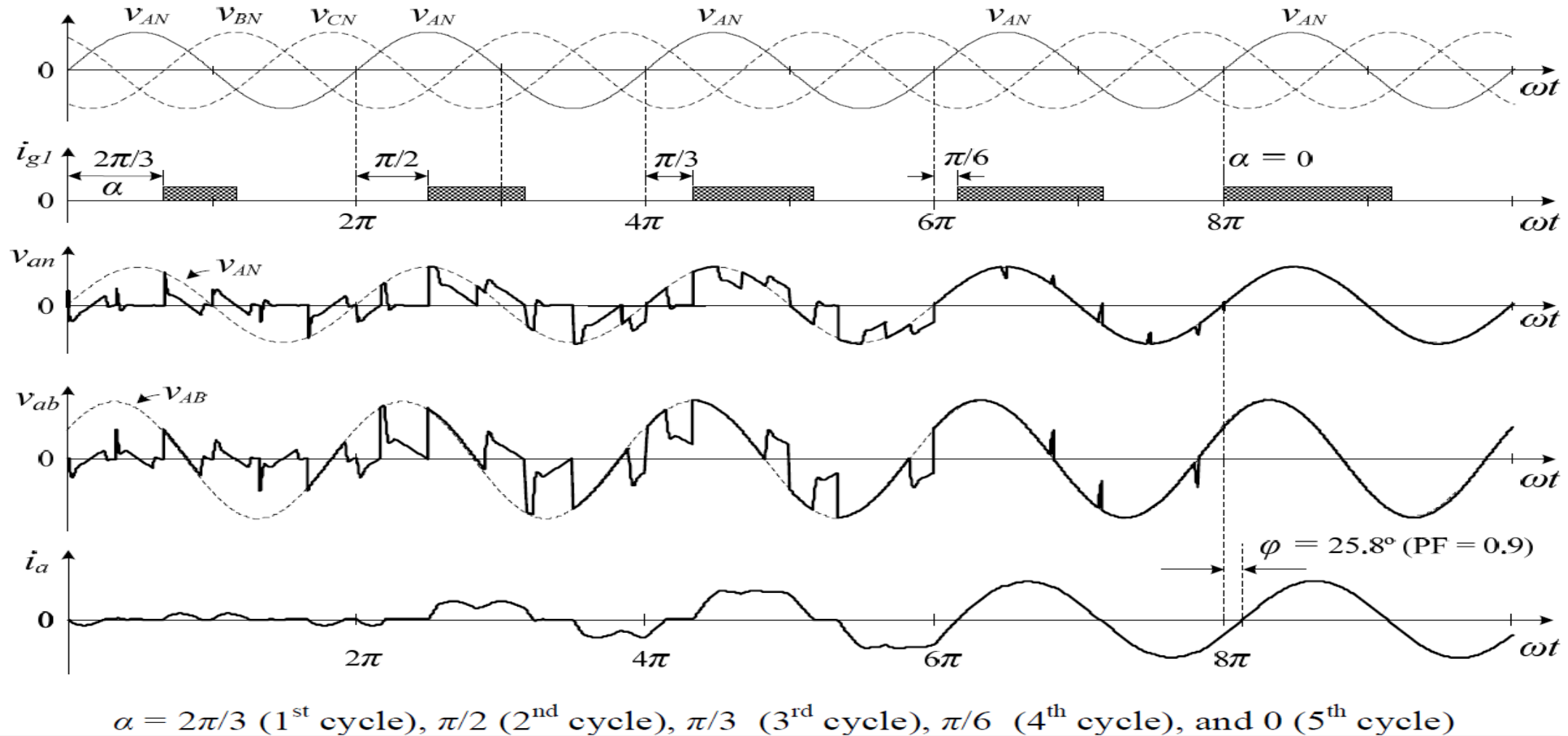
Waveform for phase- a load current i_a is much smoother than its phase voltage v_{an} due to filtering effect of load inductance. Load power factor angle $\phi = 25.8^\circ$ as indicated in figure.



With pure inductive load ($\varphi = \pi/2$) rms value of load voltage v_{an} of 3-phase AC voltage controller is given by

$$V_{an} = \begin{cases} V_s & \text{for } 0 \leq \alpha < \pi/2 \\ V_s \left(\frac{5}{2} - \frac{3\alpha}{\pi} + \frac{3\sin(2\alpha)}{2\pi} \right)^{1/2} & \text{for } \pi/2 \leq \alpha < 2\pi/3 \\ V_s \left(\frac{5}{2} - \frac{3\alpha}{\pi} + \frac{3\sin(2\alpha + \pi/3)}{2\pi} \right)^{1/2} & \text{for } 2\pi/3 \leq \alpha < 5\pi/6 \end{cases}$$

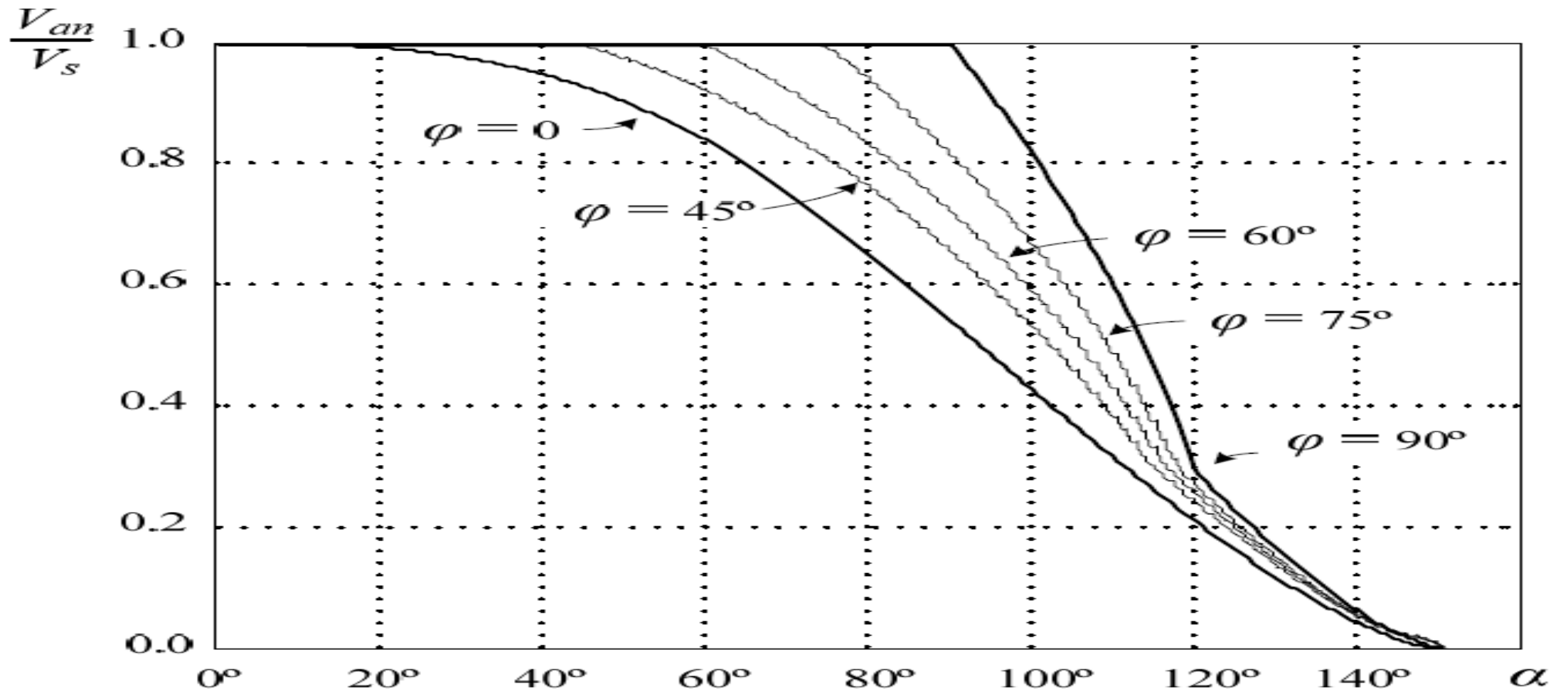Load voltage to supply voltage ratio V_{an}/V_s versus delay angle α for three-phase AC voltage controller



It is noted that when delay angle α < load power factor angle φ

- Load voltage V_{an} is equal to supply voltage V_s i.e $V_{an} = V_s$
- So it is no longer adjustable
- Same phenomenon as discussed in 1-phase AC voltage controller.

VIDEO 3-PHASE FULL WAVE AC VOLTAGE CONTROLLER (BIDIRECTIONAL CONTROLLER) WITH RL LOAD


THREE PHASE FULL CONVERTER WITH RL LOAD

LEARN
AND
GROW

LEARN
AND
GROW

Numericals

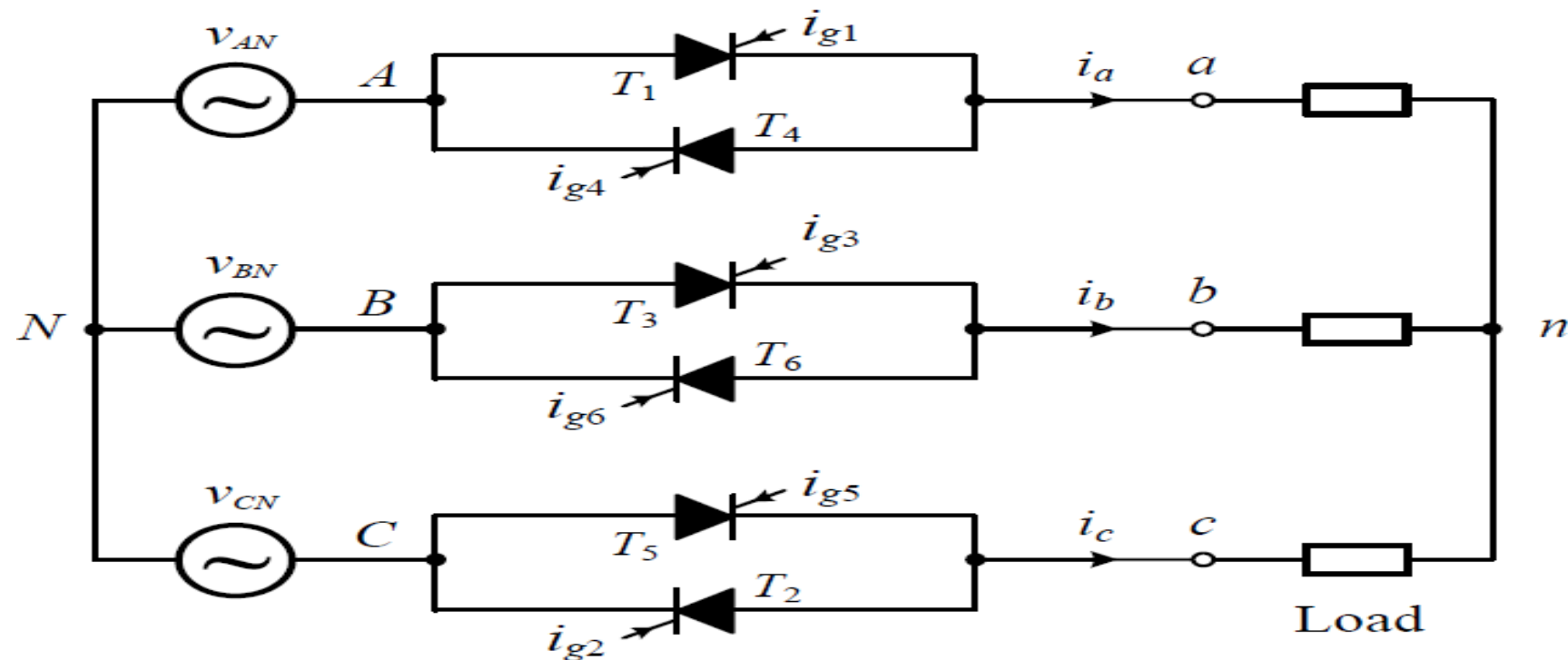4-3 (Solved Problem) A 3-phase 690V/2.3MVA AC voltage controller is loaded with a star-connected R load of 1.0 pu per phase. The controller is supplied by a 3-phase utility voltage of 690V & 50Hz & operates at a firing angle of 120°



Assuming that power converter is ideal, calculate/answer following:

- a) load resistance value,
- b) rms load phase voltage and line current
- c) 3-phase apparent, active and reactive powers of the load,
- d) rms input line current,
- e) 3-phase input apparent, active, reactive powers and power factor. State the reason why the input power factor is not unity even though the controller is loaded with a pure resistive load, and
- f) using template given in Fig. P4-3, draw waveform for phase-*a* load voltage *v_{an}* .

Solution:

a) Load resistance value:

$$S_B = \frac{2300 \times 10^3}{3} = 766.67 \times 10^3 \text{ VA (1.0 pu)},$$

$$V_s = V_B = \frac{690}{\sqrt{3}} = 398.38 \text{ V (1.0 pu)}$$

$$I_B = \frac{S_B}{V_B} = \frac{766.67 \times 10^3}{398.38} = 1924.5 \text{ A (1.0 pu)},$$

$$Z_B = \frac{V_B}{I_B} = \frac{398.38}{1924.5} = 0.207 \Omega \text{ (1.0 pu)}$$

$$R = Z_B \times R_{pu} = 0.207 \times 1.0 = 0.207 \Omega$$

b) The load phase voltage:

$$V_{an} = V_s \left(\frac{5}{4} - \frac{3\alpha}{2\pi} + \frac{3\sin(2\alpha + \pi/3)}{4\pi} \right)^{1/2}$$
$$= 398.37 \times \left(\frac{5}{4} - \frac{3 \times (2\pi/3)}{2\pi} + \frac{3\sin(2 \times (2\pi/3) + \pi/3)}{4\pi} \right)^{1/2} = 82.85 \text{ V (rms)}$$

(α is in radians)

The load line current: $I_a = \frac{V_{an}}{R} = \frac{82.85}{0.207} = 400.24 \text{ A (rms)}$

c) 3-phase apparent power of load:

$$S_o = 3 \times V_{an} \times I_a = 3 \times 82.85 \times 400.24 = 99.48 \times 10^3 \text{ VA}$$

3-phase active power consumed by load:

$$P_o = 3 \times I_a^2 \times R = 3 \times 400.24^2 \times 0.207 = 99.48 \times 10^3 \text{ W}$$

3-phase reactive power consumed by load:

$$Q_o = \sqrt{S_o^2 - P_o^2} = \sqrt{99478^2 - 99478^2} = 0 \text{ VAR}$$

d) The input line current:

$$I_A = I_a = 400.24 \text{ A (rms)}$$

e) 3-phase input apparent power:

$$S_s = 3 \times V_s \times I_A = 3 \times 398.38 \times 400.24 = 478.33 \times 10^3 \text{ VA}$$

The input active power:

$$P_s = S_s \times \cos \varphi_s = 3 \times V_s \times I_A \times \cos \varphi_s = 3 \times 398.38 \times 400.24 \times 0.208 = 99.48 \times 10^3 \text{ W}$$


The input reactive power:

$$Q_s = \sqrt{S_s^2 - P_s^2} = \sqrt{478330^2 - 99478^2} = 467.87 \times 10^3 \text{ VAR}$$

The input power factor:

$$PF_s = \frac{P_s}{S_s} = \frac{99.48 \times 10^3}{478.33 \times 10^3} = 0.208$$

f) Waveforms

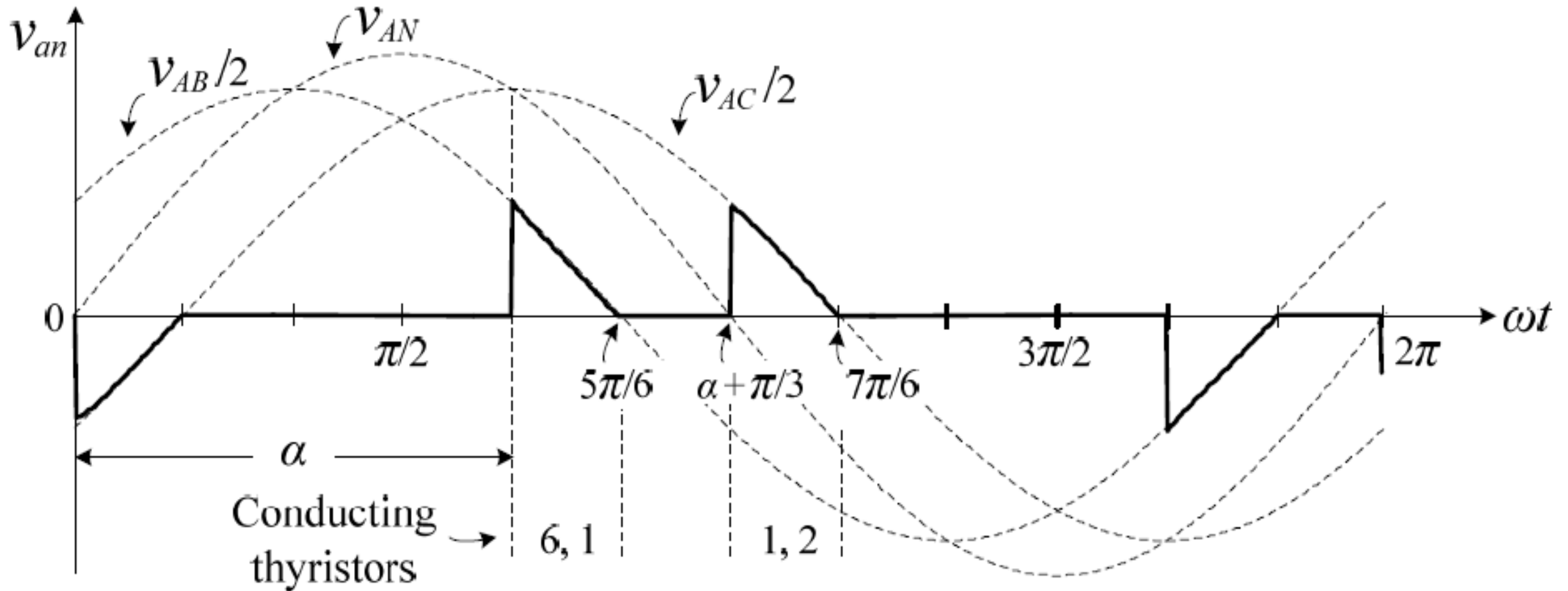

(a) $\alpha = 2\pi/3$ (120°, Mode I)

4-4 Repeat the Problem 4-3 with a firing angle of 75° . Compare the input power factor and explain why the input power factor is improved?

Answers:

a) $R = 0.207 \, \Omega$ b) $V_{an} = 281.69 \, \text{V}$, $I_a = 1360.8 \, \text{A}$


c) $S_o = 1150 \times 10^3 \, \text{VA}$, $P_o = 1150 \times 10^3 \, \text{W}$, $Q_o = 0 \, \text{VAR}$

d) $I_A = 1360.8 \, \text{A}$

e) $S_s = 1626.3 \times 10^3 \, \text{VA}$, $P_s = 1150 \times 10^3 \, \text{W}$, $Q_s = 1150 \times 10^3 \, \text{VAR}$, $PF_s = 0.7071$

f) Waveforms: See Fig. 4.2-8b.

f) Waveforms

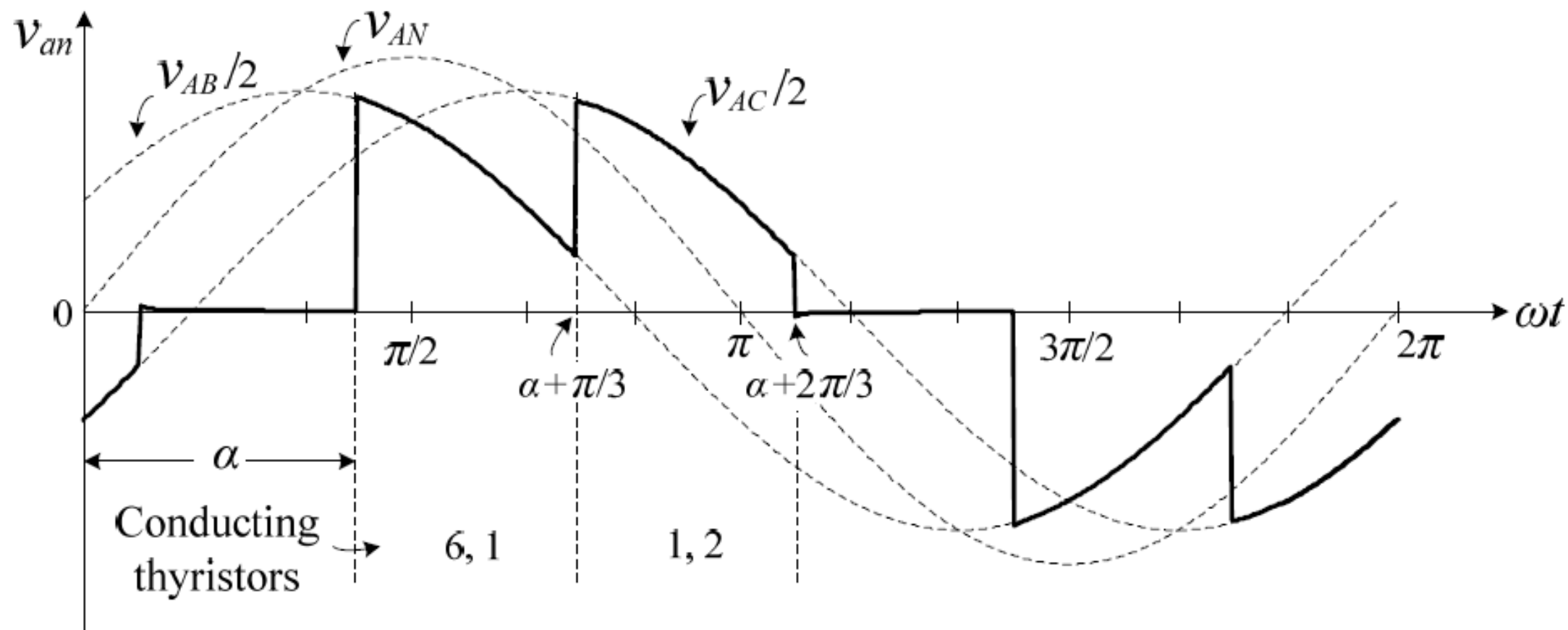

(b) $\alpha = 5\pi/12$ (75° , Mode II)

4-5 Repeat the Problem 4-3 with a firing angle of 30° and compare the input power factor and explain why the input power factor is improved?

Answers:

a) $R = 0.207 \, \Omega$ b) $V_{an} = 389.7 \, \text{V}$, $I_a = 1882.4 \, \text{A}$


c) $S_o = 2200.5 \times 10^3 \, \text{VA}$, $P_o = 2200.5 \times 10^3 \, \text{W}$, $Q_o = 0 \, \text{VAR}$

d) $I_A = 1882.4 \, \text{A}$

e) $S_s = 2249.7 \times 10^3 \, \text{VA}$, $P_s = 2200.5 \times 10^3 \, \text{W}$, $Q_s = 467.8 \times 10^3 \, \text{VAR}$, $PF_s = 0.978$

f) Waveforms: See Fig. 4.2-8c.

f) Waveforms

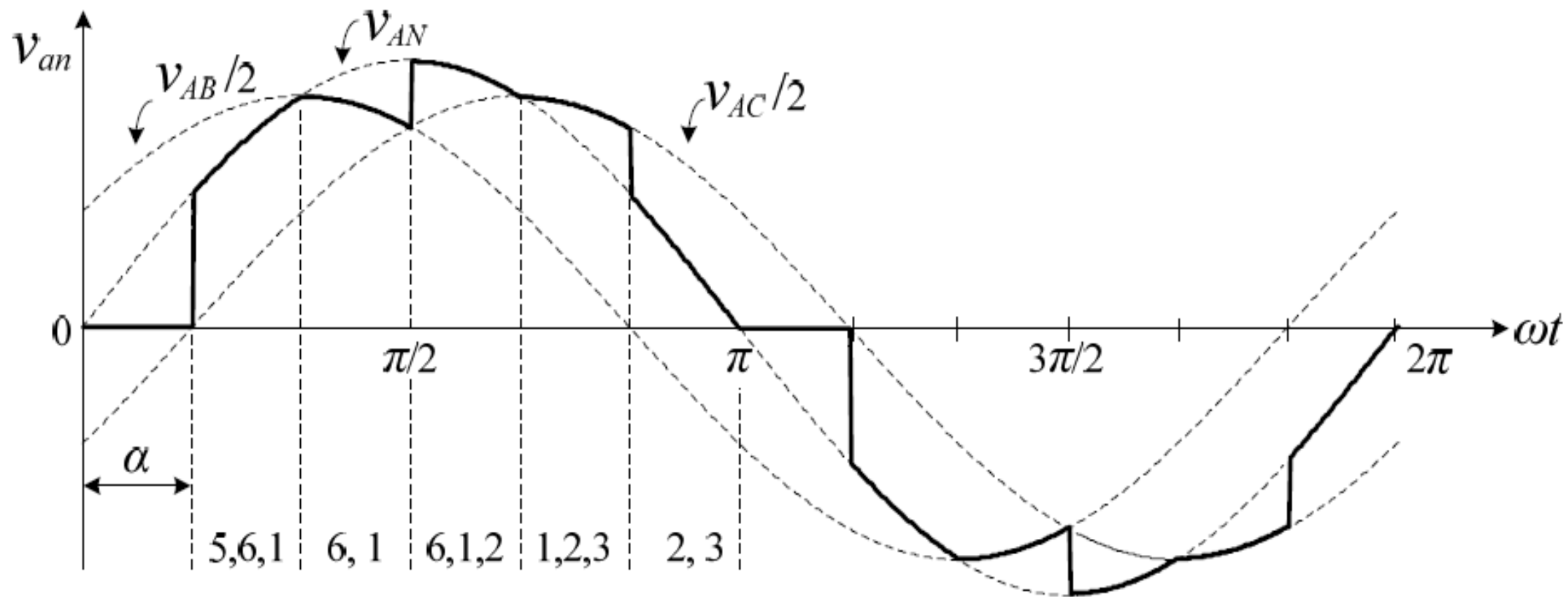

(c) $\alpha = \pi/6$ (30° , Mode III)