

# Lecture#


- **4.4.2 Space Vector Modulation?**

## 4.4.2 Space Vector Modulation

- Space vector modulation (SVM) is one of real-time modulation techniques.
- It is widely used for digital control of voltage source inverters.


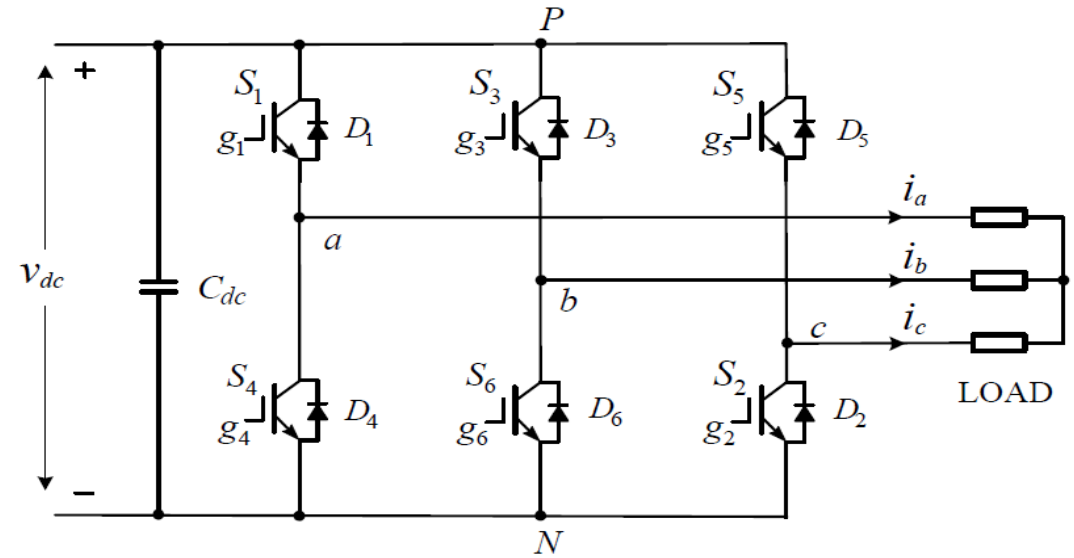
## a) Switching States

- Operating status of switches in 2-level inverter in Fig. can be represented by switching states.





Switching State	Leg <i>a</i>			Leg <i>b</i>			Leg <i>c</i>		
	$S_1$	$S_4$	$v_{aN}$	$S_3$	$S_6$	$v_{bN}$	$S_5$	$S_2$	$v_{cN}$
P	On	Off	$V_{dc}$	On	Off	$V_{dc}$	On	Off	$V_{dc}$
O	Off	On	0	Off	On	0	Off	On	0

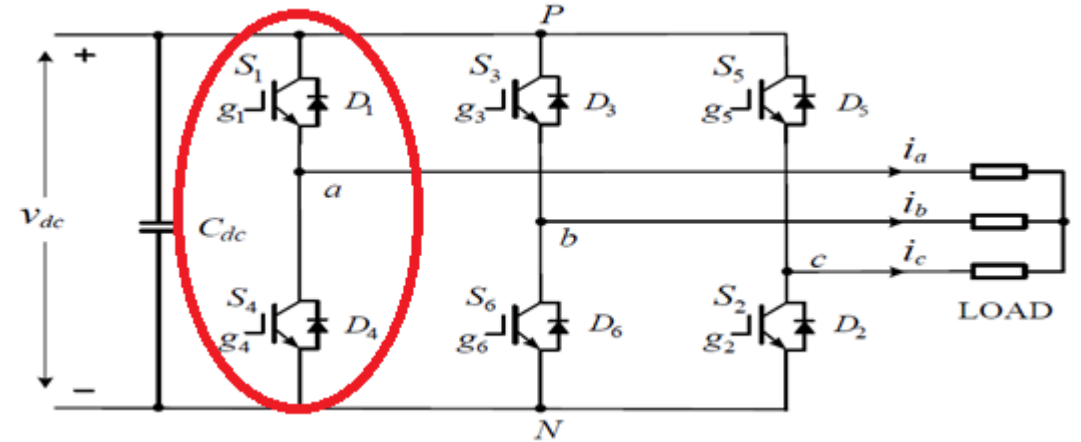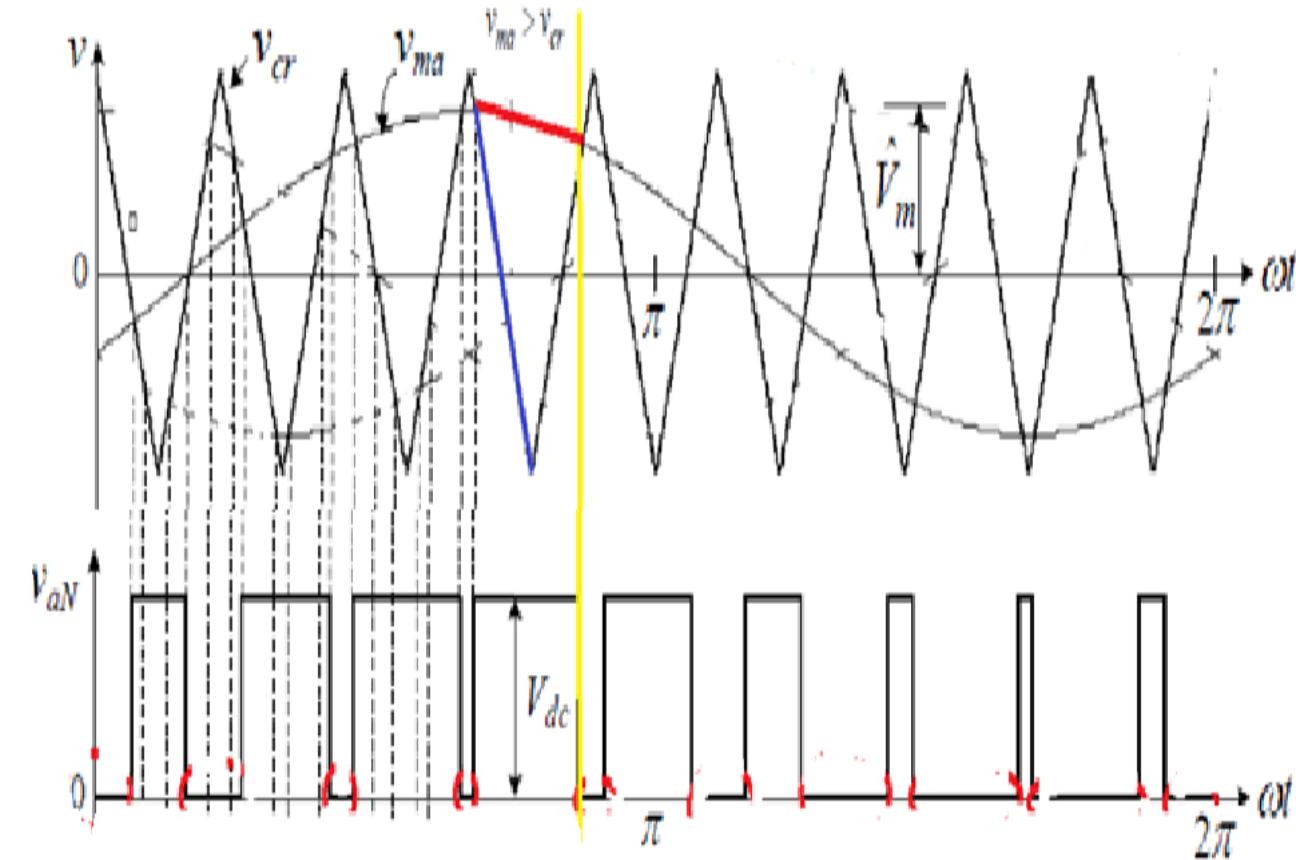When  $v_{ma} > v_{cr}$ , upper switch  $S_1$  in inverter leg  $a$  is turned on. Lower switch  $S_4$  operates in a complementary manner & thus is switched off.



Switching State	Leg a			Leg b			Leg c		
	$S_1$	$S_4$	$v_{aN}$	$S_3$	$S_6$	$v_{bN}$	$S_5$	$S_2$	$v_{cN}$
P	On	Off	$V_{dc}$	On	Off	$V_{dc}$	On	Off	$V_{dc}$
O	Off	On	0	Off	On	0	Off	On	0

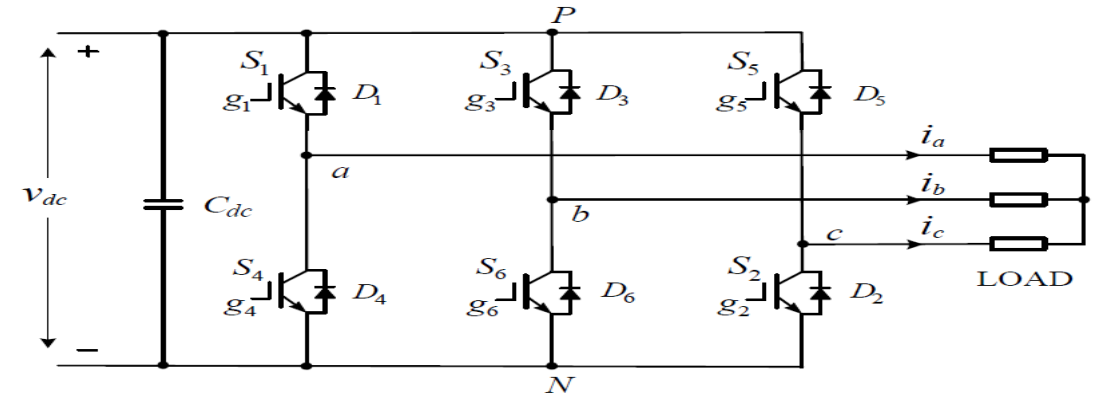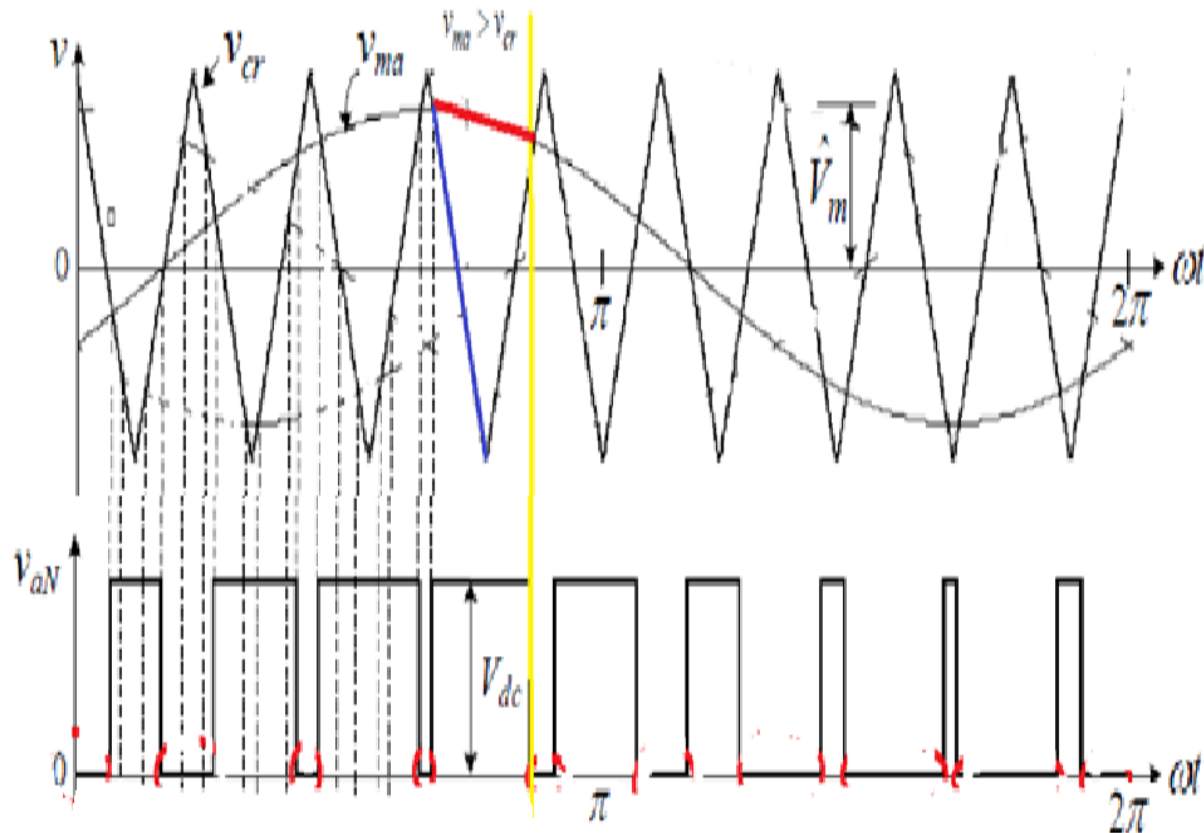Resultant inverter terminal voltage  $v_{aN}$ , which is voltage at phase- $a$  terminal w.r.t -ve dc bus  $N$ , =dc voltage  $V_{dc}$ , viz.  $v_{aN} = V_{dc}$




Switching State	Leg $a$			Leg $b$			Leg $c$		
	$S_1$	$S_4$	$v_{aN}$	$S_3$	$S_6$	$v_{bN}$	$S_5$	$S_2$	$v_{cN}$
P	On	Off	$V_{dc}$	On	Off	$V_{dc}$	On	Off	$V_{dc}$
O	Off	On	0	Off	On	0	Off	On	0

From table , switching state 'P' denotes that upper switches( $S_1, S_3$  &  $S_5$ ) in an inverter leg is on

- Inverter terminal voltage (  $v_{aN}$  ,  $v_{bN}$  or  $v_{cN}$  ) is +ve (  $+V_{dc}$  )
- 'O' indicates that inverter terminal voltage is 0 due to conduction of lower switch.



Switching State	Leg a			Leg b			Leg c		
	$S_1$	$S_4$	$v_{aN}$	$S_3$	$S_6$	$v_{bN}$	$S_5$	$S_2$	$v_{cN}$
P	On	Off	$V_{dc}$	On	Off	$V_{dc}$	On	Off	$V_{dc}$
O	Off	On	0	Off	On	0	Off	On	0

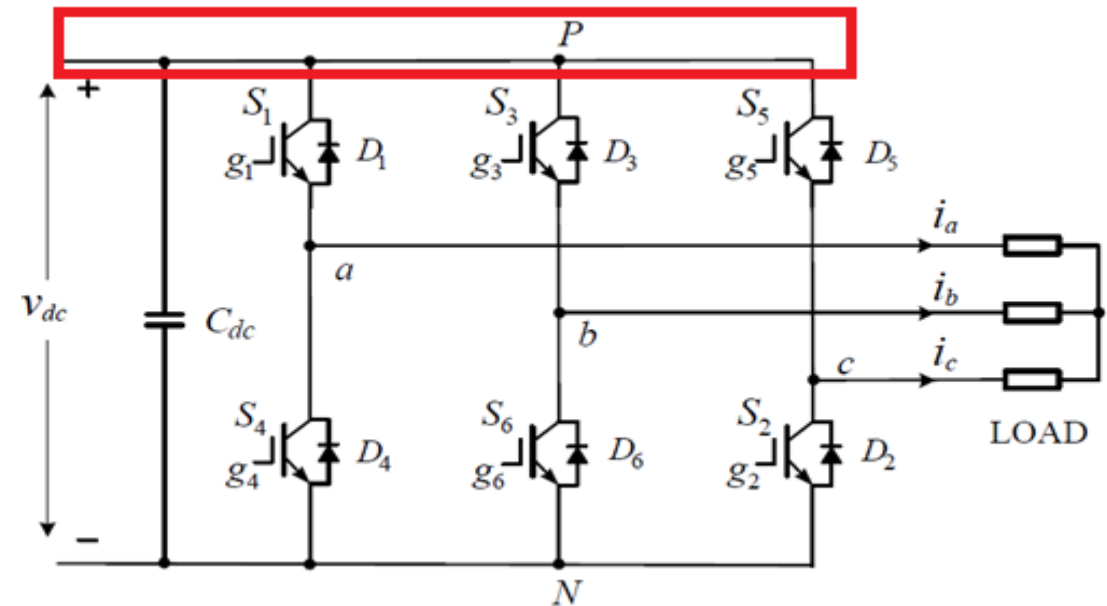

Q. Two-level inverter has 3 phases so how many possible combinations of switching states?


Answer. There can be 8 possible combinations( $2^3$ ) of switching states in 2-level inverter as listed in Table

Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	$\vec{V}_0$	[PPP]	$S_1, S_3, S_5$	$\vec{V}_0 = 0$
		[OOO]	$S_4, S_6, S_2$	
Active Vector	$\vec{V}_1$	[POO]	$S_1, S_6, S_2$	$\vec{V}_1 = \frac{2}{3} V_{dc} e^{j0}$
	$\vec{V}_2$	[PPO]	$S_1, S_3, S_2$	$\vec{V}_2 = \frac{2}{3} V_{dc} e^{j\frac{\pi}{3}}$
	$\vec{V}_3$	[OPO]	$S_4, S_3, S_2$	$\vec{V}_3 = \frac{2}{3} V_{dc} e^{j\frac{2\pi}{3}}$
	$\vec{V}_4$	[OPP]	$S_4, S_3, S_5$	$\vec{V}_4 = \frac{2}{3} V_{dc} e^{j\frac{3\pi}{3}}$
	$\vec{V}_5$	[OOP]	$S_4, S_6, S_5$	$\vec{V}_5 = \frac{2}{3} V_{dc} e^{j\frac{4\pi}{3}}$
	$\vec{V}_6$	[POP]	$S_1, S_6, S_5$	$\vec{V}_6 = \frac{2}{3} V_{dc} e^{j\frac{5\pi}{3}}$

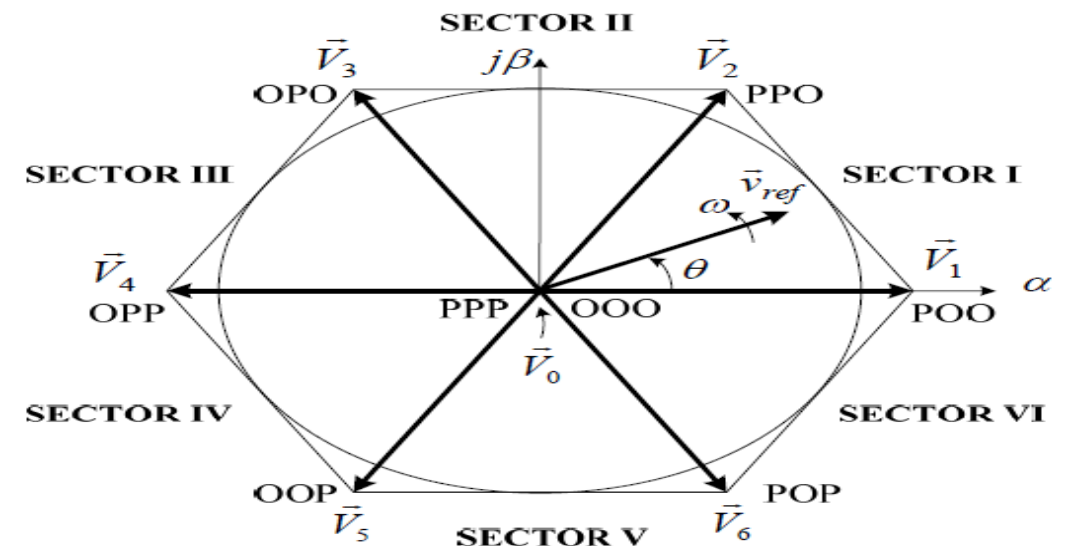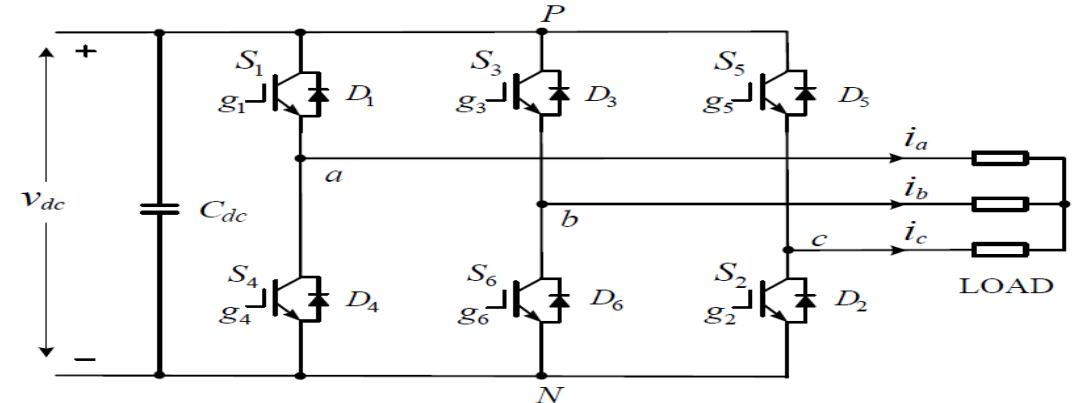




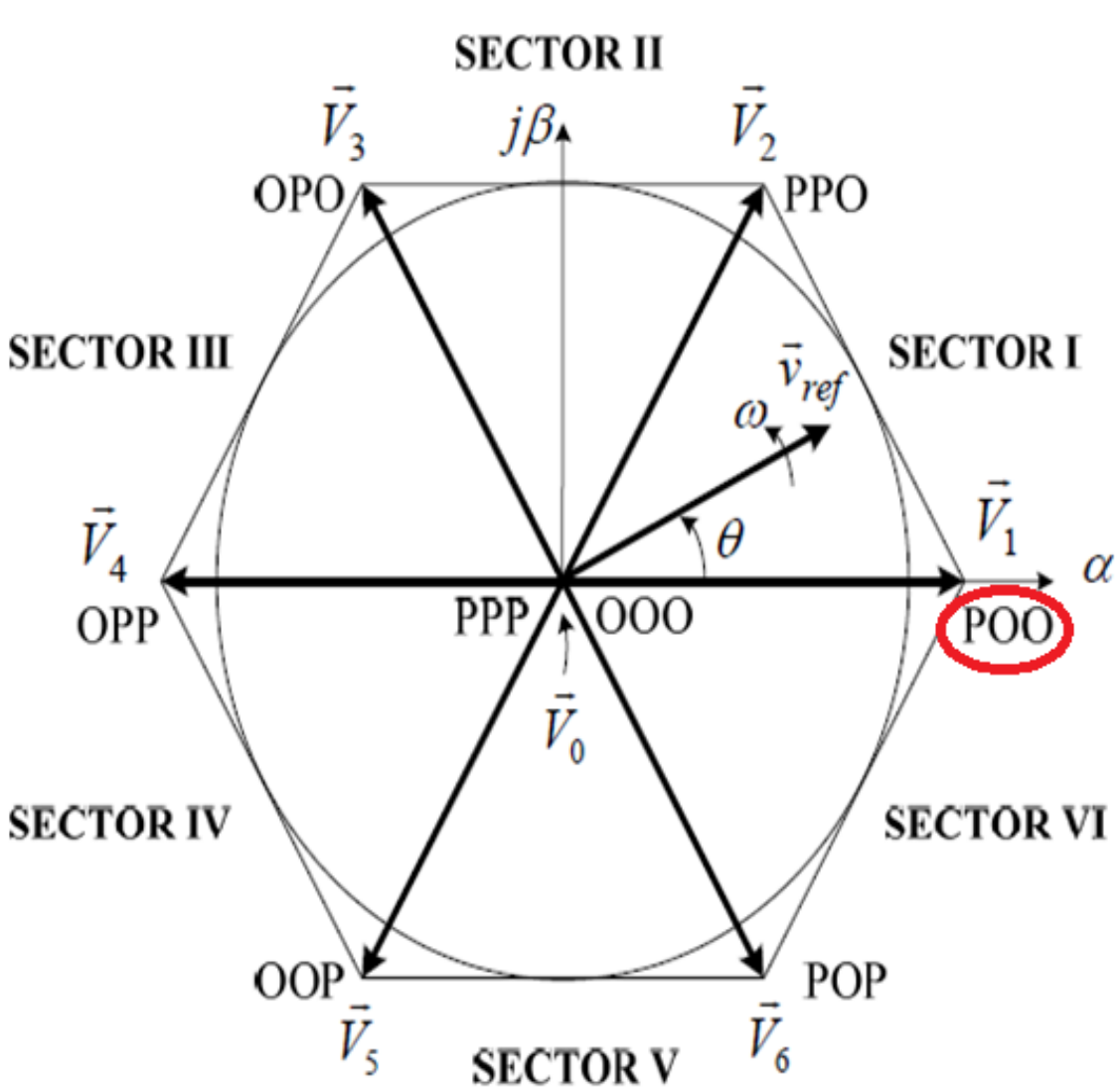
Switching state [POO] corresponds to conduction of  $S_1$ ,  $S_6$  &  $S_2$  in inverter legs  $a$ ,  $b$  and  $c$ , respectively.




Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	$\vec{V}_0$	[PPP]	$S_1, S_3, S_5$	$\vec{V}_0 = 0$
		[OOO]	$S_4, S_6, S_2$	
Active Vector	$\vec{V}_1$	[POO]	$S_1, S_6, S_2$	$\vec{V}_1 = \frac{2}{3} V_{dc} e^{j0}$
	$\vec{V}_2$	[PPO]	$S_1, S_3, S_2$	$\vec{V}_2 = \frac{2}{3} V_{dc} e^{j\frac{\pi}{3}}$
	$\vec{V}_3$	[OPO]	$S_4, S_3, S_2$	$\vec{V}_3 = \frac{2}{3} V_{dc} e^{j\frac{2\pi}{3}}$
	$\vec{V}_4$	[OPP]	$S_4, S_3, S_5$	$\vec{V}_4 = \frac{2}{3} V_{dc} e^{j\frac{3\pi}{3}}$
	$\vec{V}_5$	[OOP]	$S_4, S_6, S_5$	$\vec{V}_5 = \frac{2}{3} V_{dc} e^{j\frac{4\pi}{3}}$
	$\vec{V}_6$	[POP]	$S_1, S_6, S_5$	$\vec{V}_6 = \frac{2}{3} V_{dc} e^{j\frac{5\pi}{3}}$

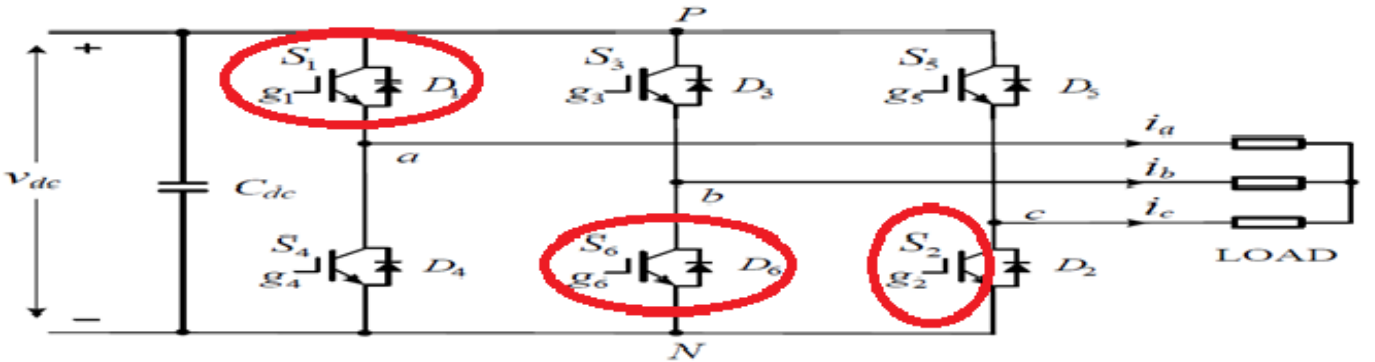

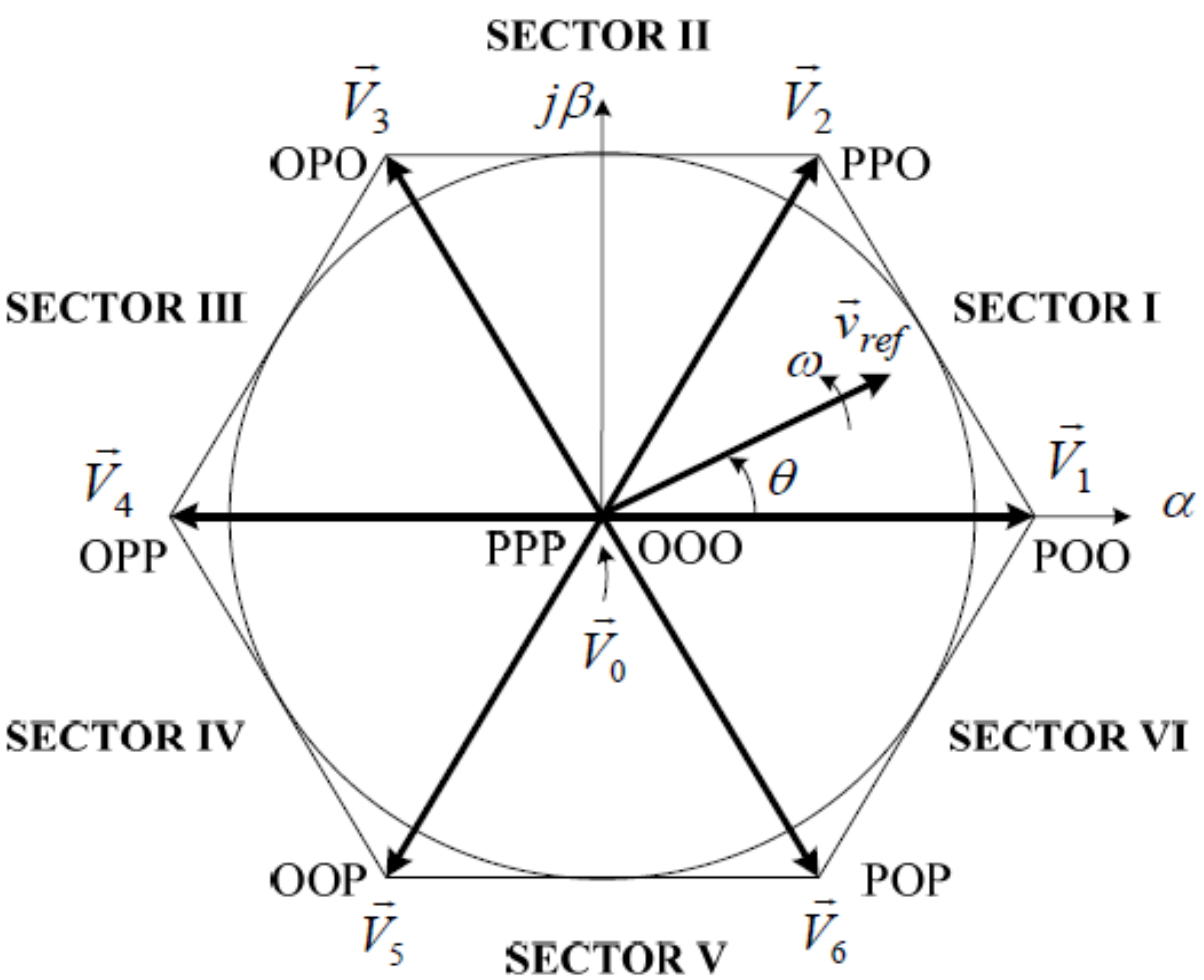
Among 8 switching states, which states are zero states?




Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	$\vec{V}_0$	[PPP]	$S_1, S_3, S_5$	$\vec{V}_0 = 0$
		[OOO]	$S_4, S_6, S_2$	
Active Vector	$\vec{V}_1$	[POO]	$S_1, S_6, S_2$	$\vec{V}_1 = \frac{2}{3} V_{dc} e^{j0}$
	$\vec{V}_2$	[PPO]	$S_1, S_3, S_2$	$\vec{V}_2 = \frac{2}{3} V_{dc} e^{j\frac{\pi}{3}}$
	$\vec{V}_3$	[OPO]	$S_4, S_3, S_2$	$\vec{V}_3 = \frac{2}{3} V_{dc} e^{j\frac{2\pi}{3}}$
	$\vec{V}_4$	[OPP]	$S_4, S_3, S_5$	$\vec{V}_4 = \frac{2}{3} V_{dc} e^{j\frac{3\pi}{3}}$
	$\vec{V}_5$	[OOP]	$S_4, S_6, S_5$	$\vec{V}_5 = \frac{2}{3} V_{dc} e^{j\frac{4\pi}{3}}$
	$\vec{V}_6$	[POP]	$S_1, S_6, S_5$	$\vec{V}_6 = \frac{2}{3} V_{dc} e^{j\frac{5\pi}{3}}$

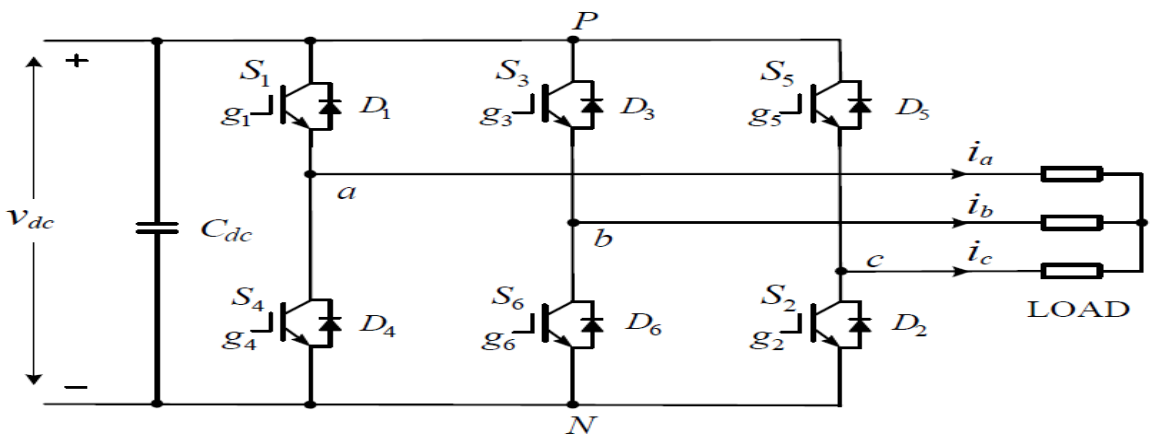

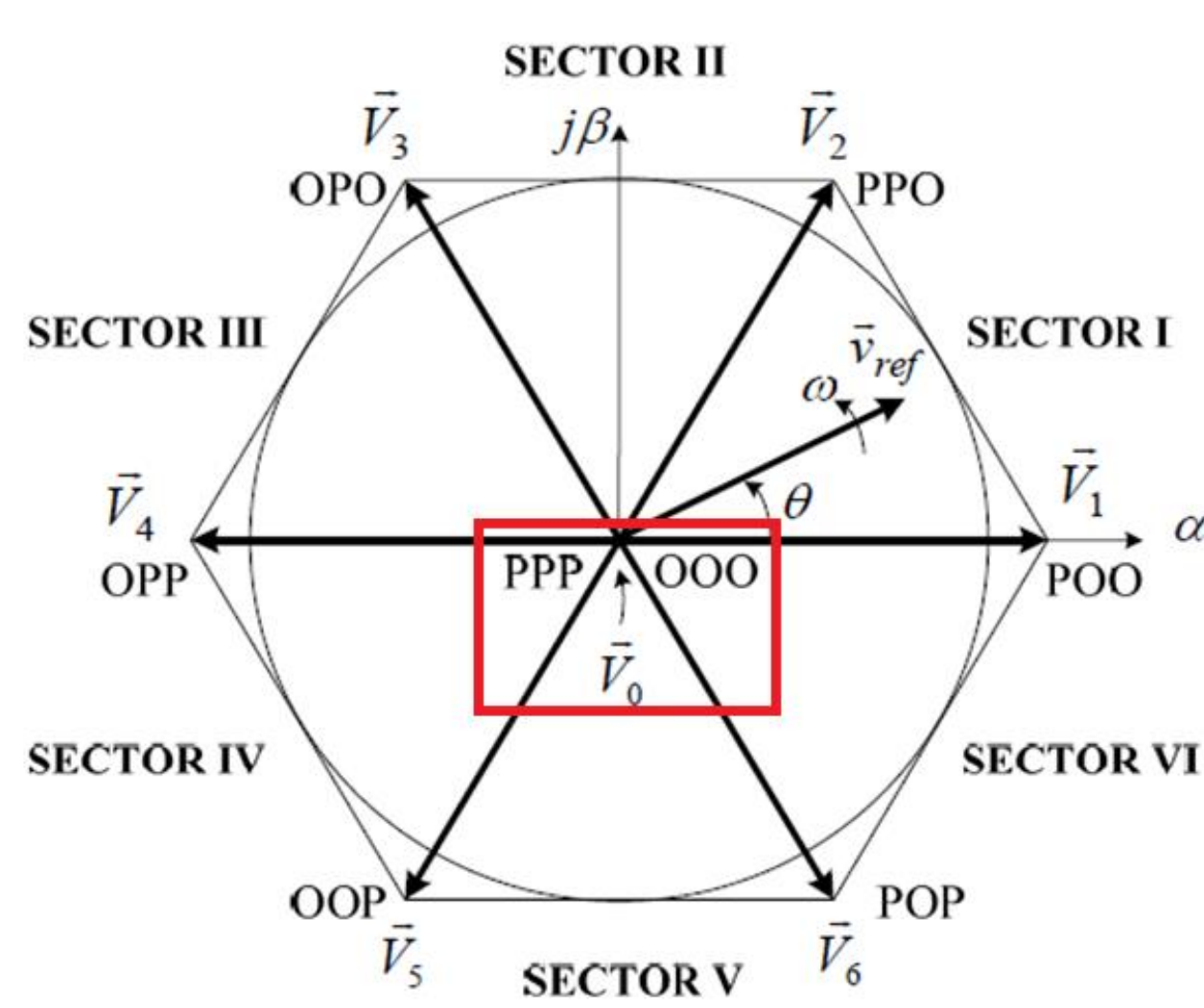Among 8 switching states, [PPP] & [OOO] are 0 states(lies in center) & others are active states.



Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	$\vec{V}_0$	[PPP]	$S_1, S_3, S_5$	$\vec{V}_0 = 0$
		[OOO]	$S_4, S_6, S_2$	
Active Vector	$\vec{V}_1$	[POO]	$S_1, S_6, S_2$	$\vec{V}_1 = \frac{2}{3} V_{dc} e^{j0}$
	$\vec{V}_2$	[PPO]	$S_1, S_3, S_2$	$\vec{V}_2 = \frac{2}{3} V_{dc} e^{j\frac{\pi}{3}}$
	$\vec{V}_3$	[OPO]	$S_4, S_3, S_2$	$\vec{V}_3 = \frac{2}{3} V_{dc} e^{j\frac{2\pi}{3}}$
	$\vec{V}_4$	[OPP]	$S_4, S_3, S_5$	$\vec{V}_4 = \frac{2}{3} V_{dc} e^{j\frac{3\pi}{3}}$
	$\vec{V}_5$	[OOP]	$S_4, S_6, S_5$	$\vec{V}_5 = \frac{2}{3} V_{dc} e^{j\frac{4\pi}{3}}$
	$\vec{V}_6$	[POP]	$S_1, S_6, S_5$	$\vec{V}_6 = \frac{2}{3} V_{dc} e^{j\frac{5\pi}{3}}$

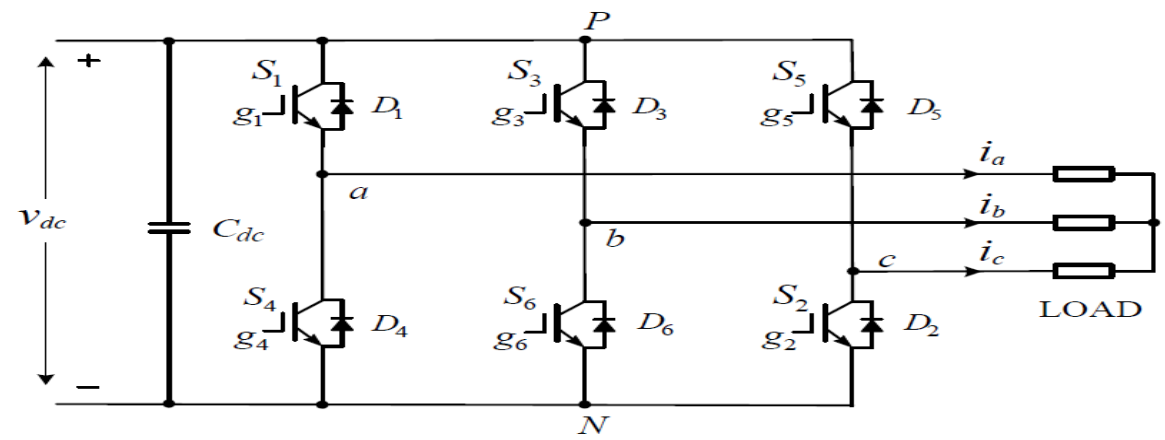


# Space vectors, switching states & on-state switches

Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	$\vec{V}_0$	[PPP]	$S_1, S_3, S_5$	$\vec{V}_0 = 0$
		[OOO]	$S_4, S_6, S_2$	
Active Vector	$\vec{V}_1$	[POO]	$S_1, S_6, S_2$	$\vec{V}_1 = \frac{2}{3}V_{dc} e^{j0}$
	$\vec{V}_2$	[PPO]	$S_1, S_3, S_2$	$\vec{V}_2 = \frac{2}{3}V_{dc} e^{j\frac{\pi}{3}}$
	$\vec{V}_3$	[OPO]	$S_4, S_3, S_2$	$\vec{V}_3 = \frac{2}{3}V_{dc} e^{j\frac{2\pi}{3}}$
	$\vec{V}_4$	[OPP]	$S_4, S_3, S_5$	$\vec{V}_4 = \frac{2}{3}V_{dc} e^{j\frac{3\pi}{3}}$
	$\vec{V}_5$	[OOP]	$S_4, S_6, S_5$	$\vec{V}_5 = \frac{2}{3}V_{dc} e^{j\frac{4\pi}{3}}$
	$\vec{V}_6$	[POP]	$S_1, S_6, S_5$	$\vec{V}_6 = \frac{2}{3}V_{dc} e^{j\frac{5\pi}{3}}$
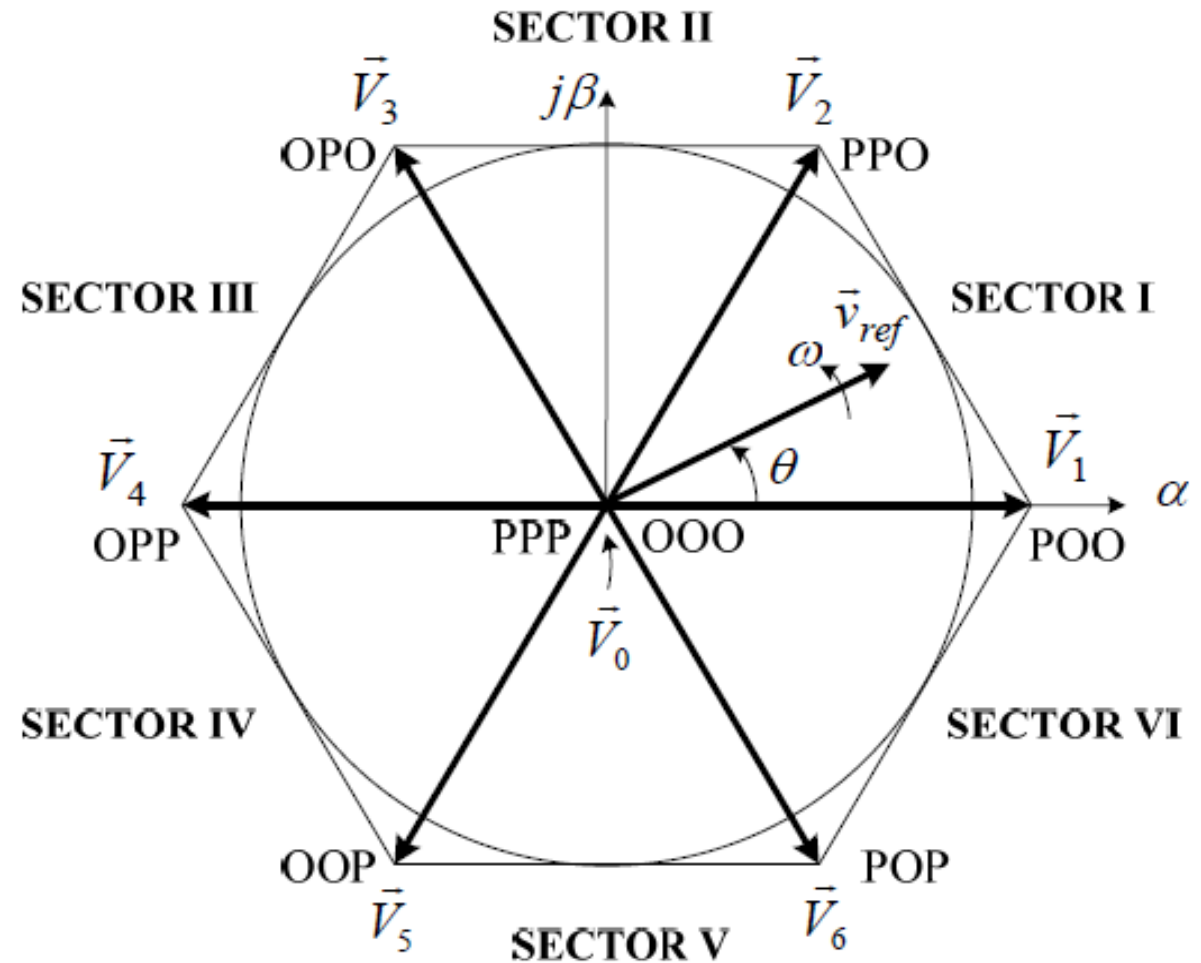
## b) Space Vectors

- Active & 0 switching states can be represented by active & 0 space vectors, respectively.
- A typical space vector diagram for 2-level inverter is shown in Fig., where 6 active vectors  $V_1$  to  $V_6$  form a regular hexagon with 6 equal sectors (I to VI).
- 0 vector  $V_0$  lies on the centre of the hexagon.




To derive relationship between space vectors & switching states, refer to 2-level inverter in Fig.

Assuming that operation of inverter is 3-phase balanced, we have

$$v_a(t) + v_b(t) + v_c(t) = 0$$

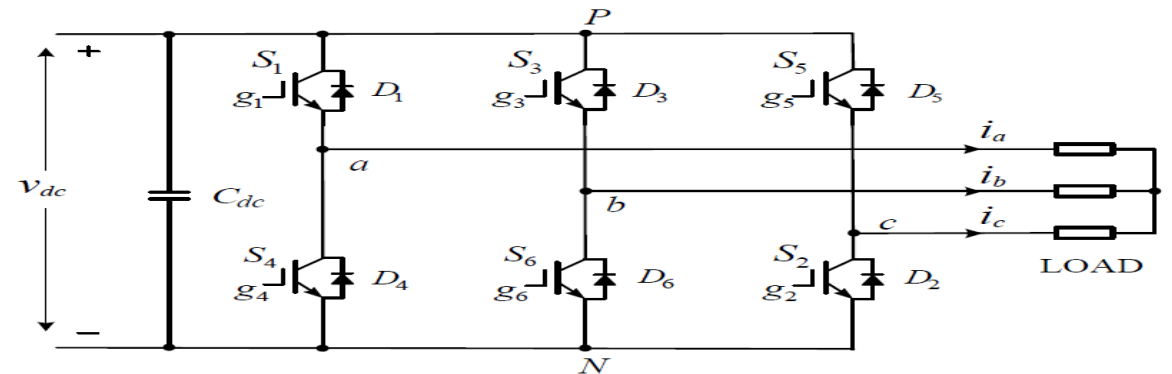where  $v_a$  ,  $v_b$  &  $v_c$  are instantaneous load phase voltages.



From mathematical point of view, one of phase voltages is redundant since given any 2 phase voltages, 3<sup>rd</sup> one can be readily calculated.

$$v_a(t) + v_b(t) + v_c(t) = 0$$

Therefore, it is possible to transform 3-phase variables to 2-phase variables through the *abc/αβ* transformation:

$$\begin{bmatrix} v_\alpha(t) \\ v_\beta(t) \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} v_a(t) \\ v_b(t) \\ v_c(t) \end{bmatrix}$$

A space vector can be generally expressed in terms of 2-phase voltages in  $\alpha$ - $\beta$  frame

$$\vec{v}(t) = v_{\alpha}(t) + j v_{\beta}(t)$$



From

$$\begin{bmatrix} v_{\alpha}(t) \\ v_{\beta}(t) \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} v_a(t) \\ v_b(t) \\ v_c(t) \end{bmatrix}$$

$$V_{\alpha}(t) = \frac{2}{3} \left\{ V_a(t) - \frac{1}{2} V_b(t) - \frac{1}{2} V_c(t) \right\}$$

$$V_{\beta}(t) = \frac{2}{3} \left\{ \frac{\sqrt{3}}{2} V_b(t) - \frac{\sqrt{3}}{2} V_c(t) \right\}$$

Substituting

$$V_{\alpha}(t) = \frac{2}{3} \left\{ V_a(t) - \frac{1}{2} V_b(t) - \frac{1}{2} V_c(t) \right\}$$

$$V_{\beta}(t) = \frac{2}{3} \left\{ \frac{\sqrt{3}}{2} V_b(t) - \frac{\sqrt{3}}{2} V_c(t) \right\}$$

into

$$\vec{v}(t) = V_{\alpha}(t) + jV_{\beta}(t)$$

Try to simplify:

$$V_{\alpha}(t) + jV_{\beta}(t) = \frac{2}{3} \left[ V_a(t) + \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right)V_b(t) + \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right)V_c(t) \right]$$

$$a = \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right)$$

$$V_{\alpha}(t) + jV_{\beta}(t) = \frac{2}{3} \left[ V_a(t) + \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right)V_b(t) + \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right)V_c(t) \right]$$

$$a = \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) = e^{j\frac{2\pi}{3}}$$

$$a^2 = \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) = e^{j\frac{4\pi}{3}}$$

$$\vec{v}(t) = \frac{2}{3} \left[ V_a(t)e^{j0} + V_b(t)e^{j\frac{2\pi}{3}} + V_c(t)e^{j\frac{4\pi}{3}} \right]$$

For active switching state [POO], generated load phase voltages are  $\frac{2}{3}V_{dc} = V_a(t)$   
 $-\frac{1}{3}V_{dc} = V_b(t) = V_c(t)$


Corresponding space vector, denoted as  $\vec{V}_1$  can be obtained by substituting these equations:

$$\vec{v}(t) = \frac{2}{3} \left[ V_a(t)e^{j0} + V_b(t)e^{j\frac{2\pi}{3}} + V_c(t)e^{j\frac{4\pi}{3}} \right]$$

$$\vec{v}(t) = \frac{2}{3} \left[ \frac{2}{3}V_{dc}e^{j0} - \frac{1}{3}V_{dc}e^{j\frac{2\pi}{3}} - \frac{1}{3}V_{dc}e^{j\frac{4\pi}{3}} \right]$$

$$\vec{v}(t) = \frac{2}{3} \left[ \frac{2}{3}V_{dc}e^{j0} - \frac{1}{3}V_{dc}(e^{j\frac{2\pi}{3}} + e^{j\frac{4\pi}{3}}) \right]$$

$$a + a^2 + 1 = 0 \quad a + a^2 = -1$$

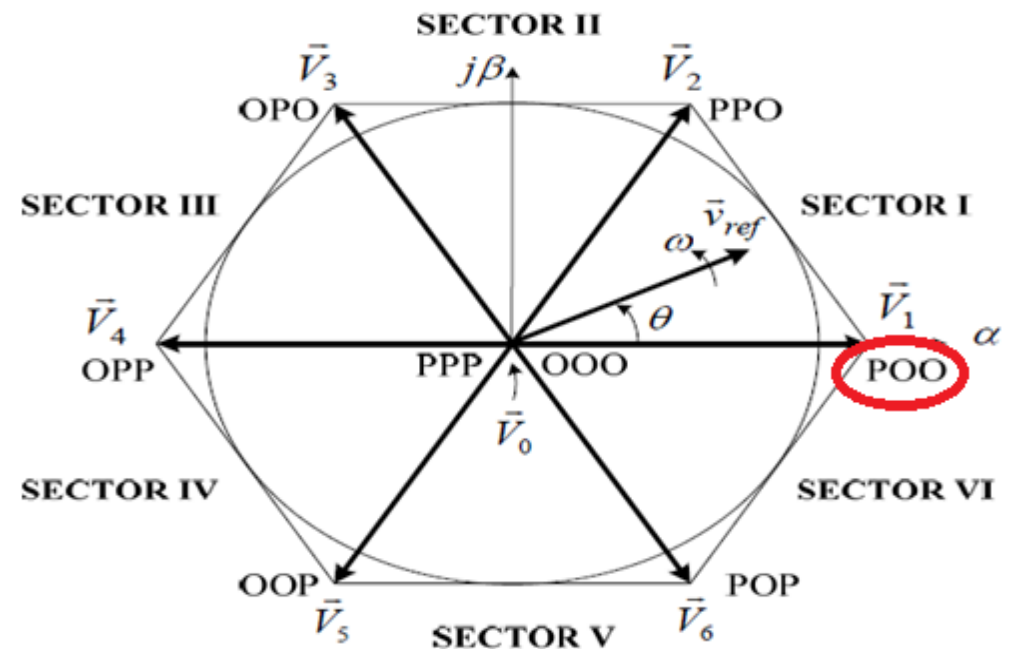

$$\vec{v}(t) = \frac{2}{3} \left[ \frac{2}{3} V_{dc} e^{j0} - \frac{1}{3} V_{dc} (e^{j\frac{2\pi}{3}} + e^{j\frac{4\pi}{3}}) \right] \qquad a + a^2 = -1$$

$$\vec{v}(t) = \frac{2}{3} \left[ \frac{2}{3} V_{dc} e^{j0} + \frac{1}{3} V_{dc} \right]$$

$$\vec{v}_1 = \left[ \frac{2}{3} V_{dc} e^{j0} \right]$$

$$\vec{v}_k = \left[ \frac{2}{3} V_{dc} e^{j(k-1)\frac{\pi}{3}} \right] k = 1, 2, \dots, 6$$

Following the same procedure, all 6 active vectors can be derived

$$\vec{v}_k = \left[ \frac{2}{3} V_{dc} e^{j(k-1)\frac{\pi}{3}} \right] k = 1, 2, \dots, 6$$

$\vec{V}_1 = \frac{2}{3} V_{dc} e^{j0}$
$\vec{V}_2 = \frac{2}{3} V_{dc} e^{j\frac{\pi}{3}}$
$\vec{V}_3 = \frac{2}{3} V_{dc} e^{j\frac{2\pi}{3}}$
$\vec{V}_4 = \frac{2}{3} V_{dc} e^{j\frac{3\pi}{3}}$
$\vec{V}_5 = \frac{2}{3} V_{dc} e^{j\frac{4\pi}{3}}$
$\vec{V}_6 = \frac{2}{3} V_{dc} e^{j\frac{5\pi}{3}}$

# Redundant vector

- 0 vector  $\vec{V}_0$  has 2 switching states [PPP] & [OOO], one of which seems redundant.
- Redundant switching state can be utilized to minimize switching frequency of inverter or perform other useful functions.




Relationship between space vectors & their corresponding switching states is given in Table

Space Vector		Switching State (Three Phases)	On-state Switch	Vector Definition
Zero Vector	$\vec{V}_0$	[PPP]	$S_1, S_3, S_5$	$\vec{V}_0 = 0$
		[OOO]	$S_4, S_6, S_2$	
Active Vector	$\vec{V}_1$	[POO]	$S_1, S_6, S_2$	$\vec{V}_1 = \frac{2}{3}V_{dc} e^{j0}$
	$\vec{V}_2$	[PPO]	$S_1, S_3, S_2$	$\vec{V}_2 = \frac{2}{3}V_{dc} e^{j\frac{\pi}{3}}$
	$\vec{V}_3$	[OPO]	$S_4, S_3, S_2$	$\vec{V}_3 = \frac{2}{3}V_{dc} e^{j\frac{2\pi}{3}}$
	$\vec{V}_4$	[OPP]	$S_4, S_3, S_5$	$\vec{V}_4 = \frac{2}{3}V_{dc} e^{j\frac{3\pi}{3}}$
	$\vec{V}_5$	[OOP]	$S_4, S_6, S_5$	$\vec{V}_5 = \frac{2}{3}V_{dc} e^{j\frac{4\pi}{3}}$
	$\vec{V}_6$	[POP]	$S_1, S_6, S_5$	$\vec{V}_6 = \frac{2}{3}V_{dc} e^{j\frac{5\pi}{3}}$

0 & active vectors do not move in space, & thus are referred to as stationary vectors.


- On the contrary, reference vector  $\vec{v}_{ref}$  rotates in space at an angular velocity  $\omega = 2\pi f$
- where  $f$  is fundamental frequency of inverter output voltage.
- Angular displacement ( $\theta$ ) between  $\vec{v}_{ref}$  &  $\alpha$ -axis of  $\alpha$ - $\beta$  frame can be obtained:
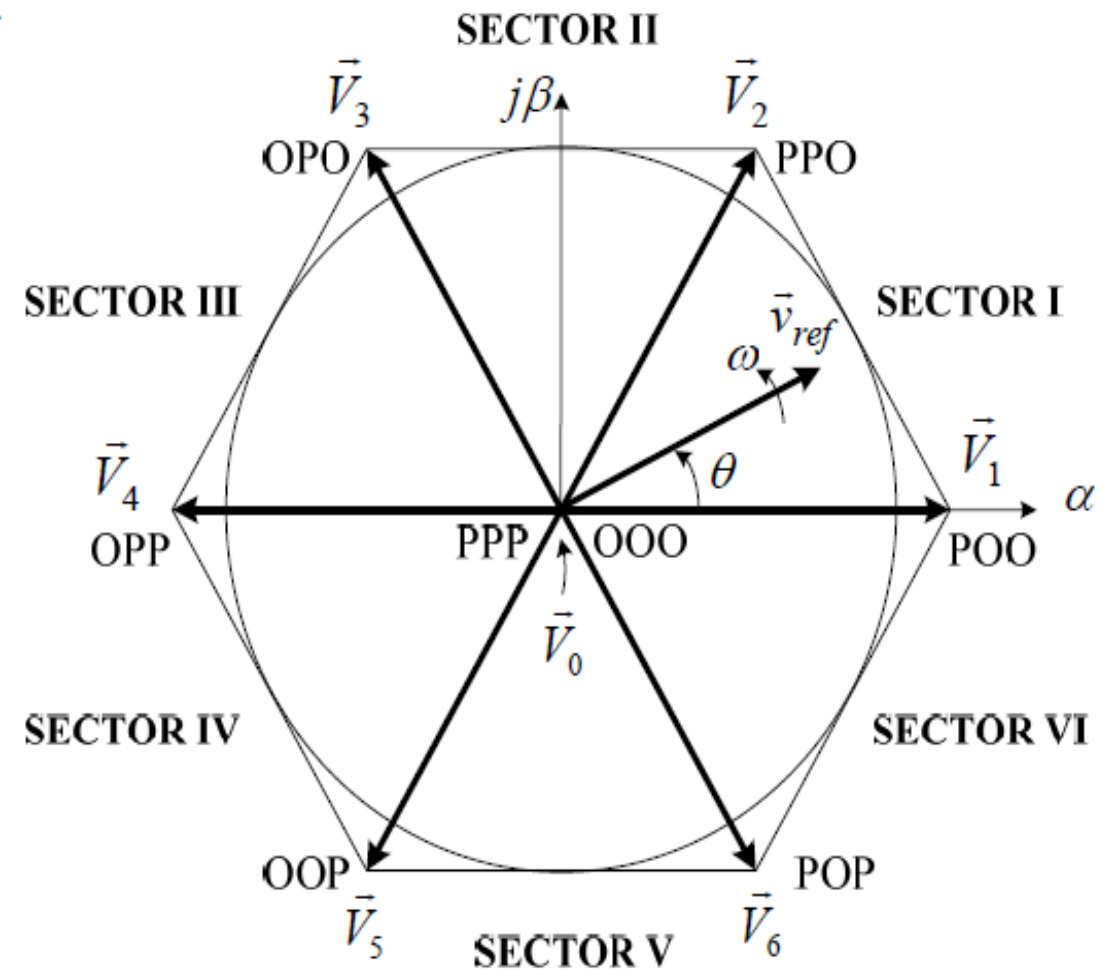
$$\theta(t) = \int_0^t \omega(t) dt + \theta_0$$




For a given magnitude (length) and position,  $\vec{v}_{ref}$  can be synthesized by 3 nearby stationary vectors,

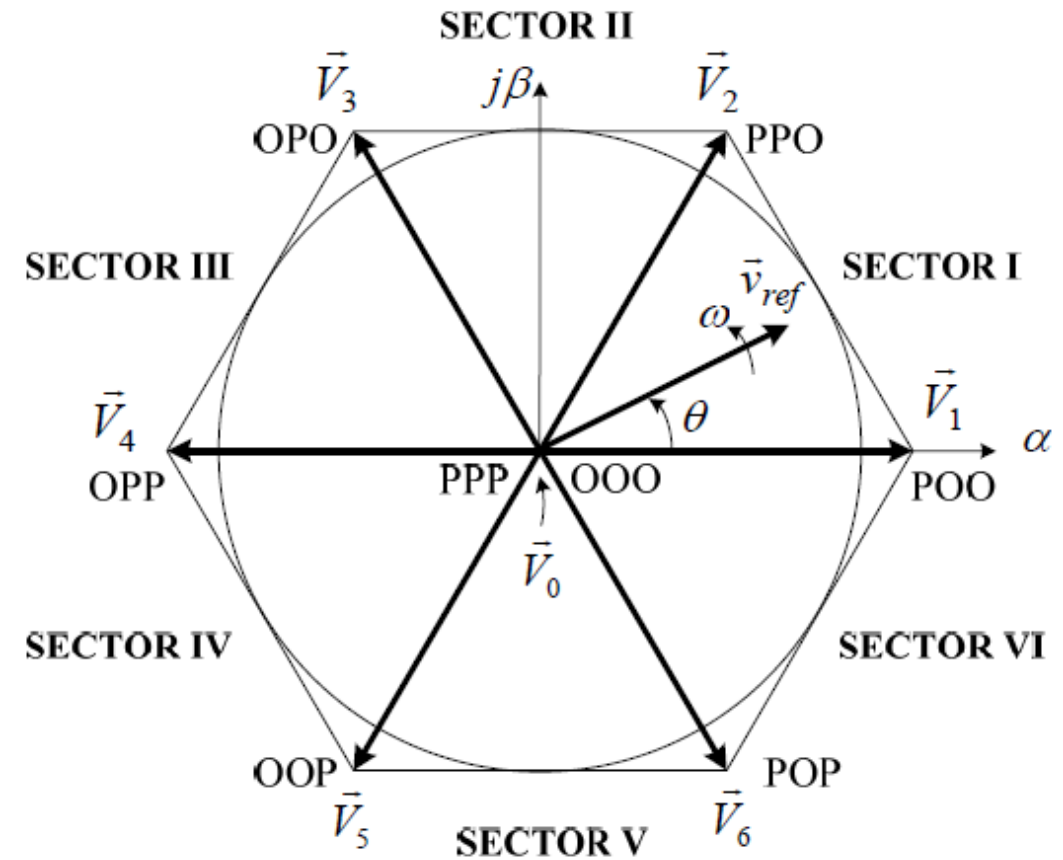- Based on which switching states of inverter can be selected and
- Gate signals for active switches can be generated.




When  $\vec{v}_{ref}$  passes through sectors one by one, different sets of switches will be turned on or off.

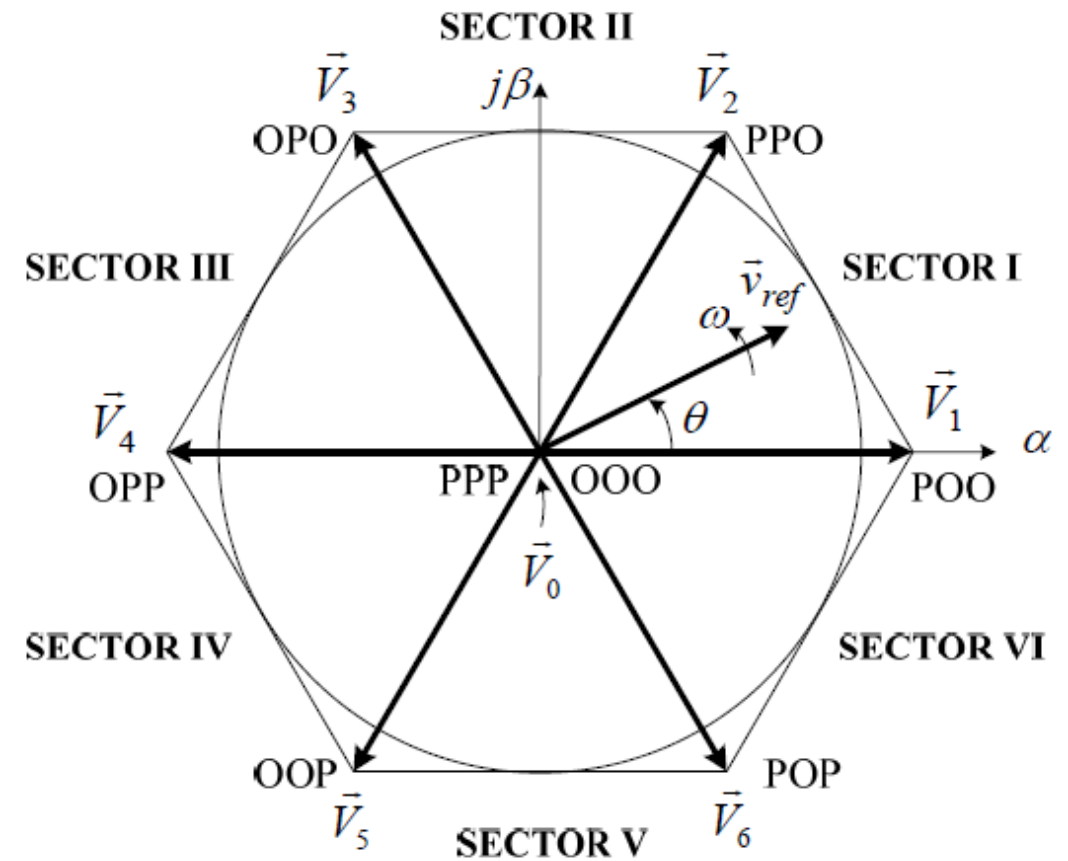- As a result, when  $\vec{v}_{ref}$  rotates 1 revolution in space,
- inverter output voltage varies 1 cycle over time.




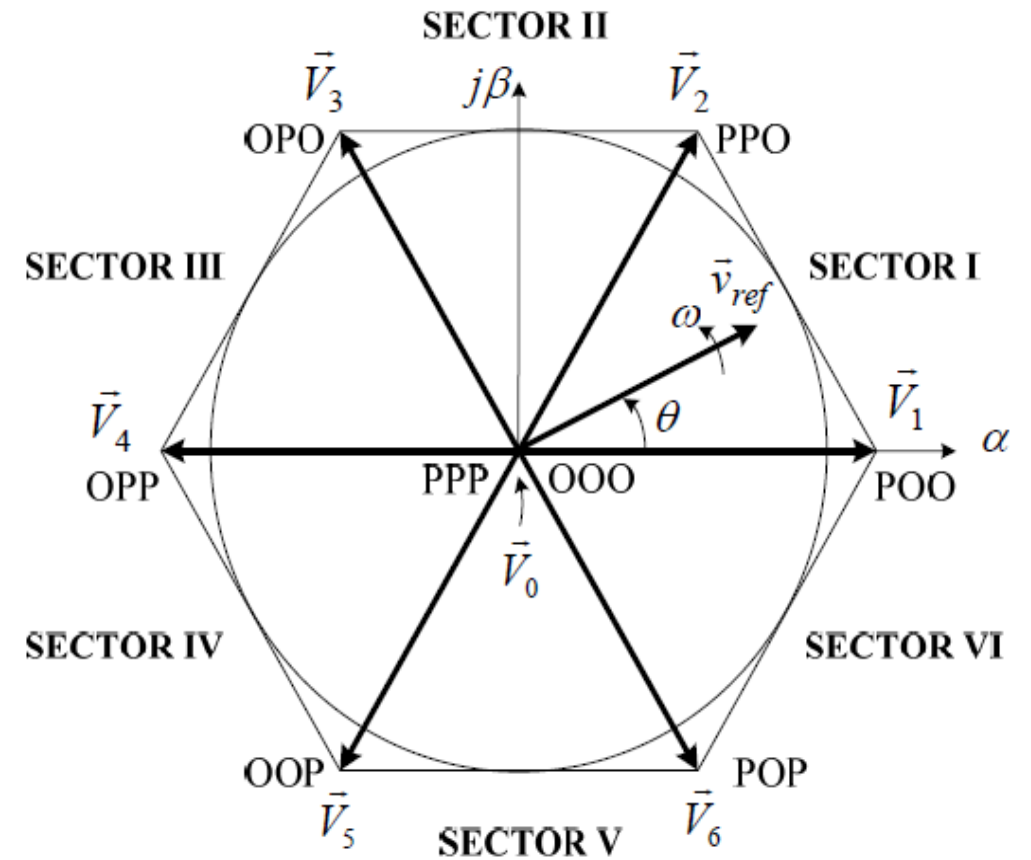
# Inverter output frequency

- Inverter output frequency corresponds to the rotating speed of  $\vec{v}_{ref}$
- while its output voltage can be adjusted by the magnitude of  $\vec{v}_{ref}$



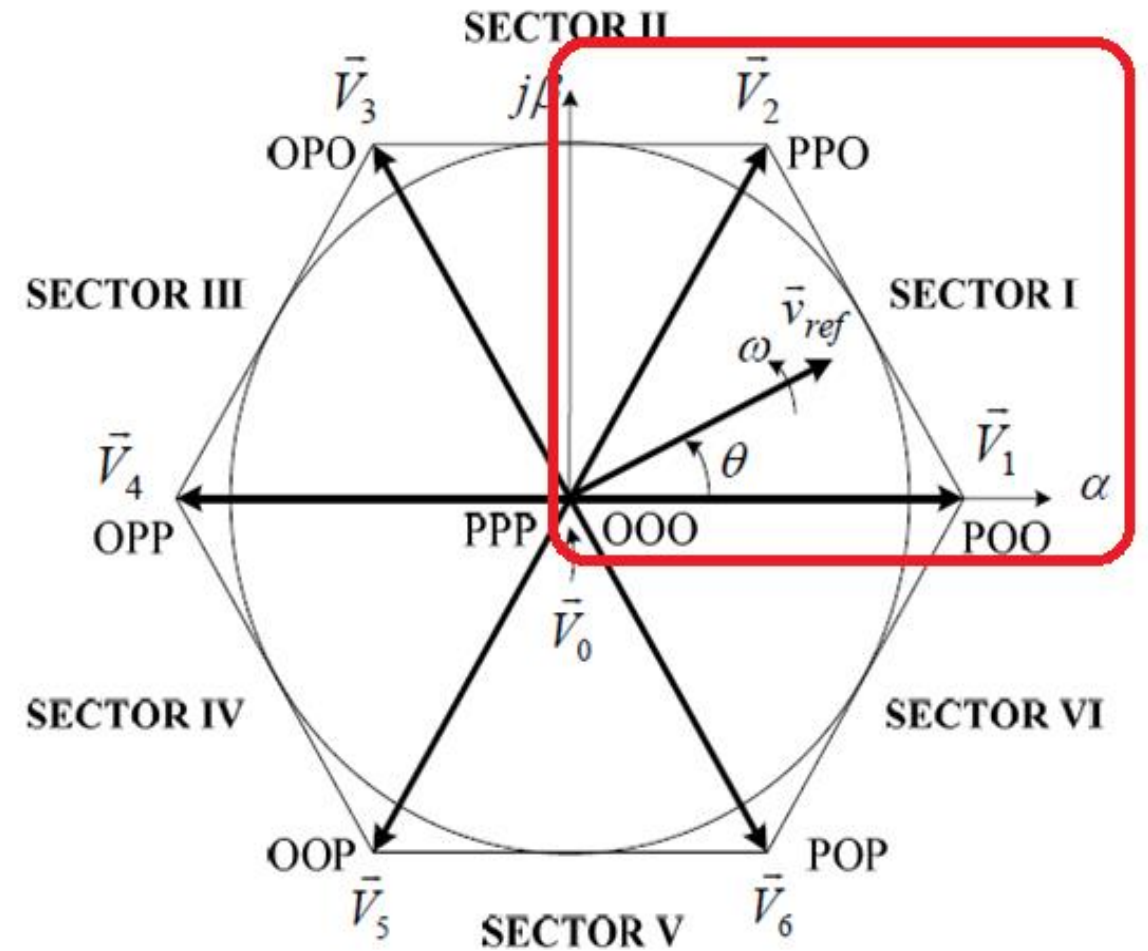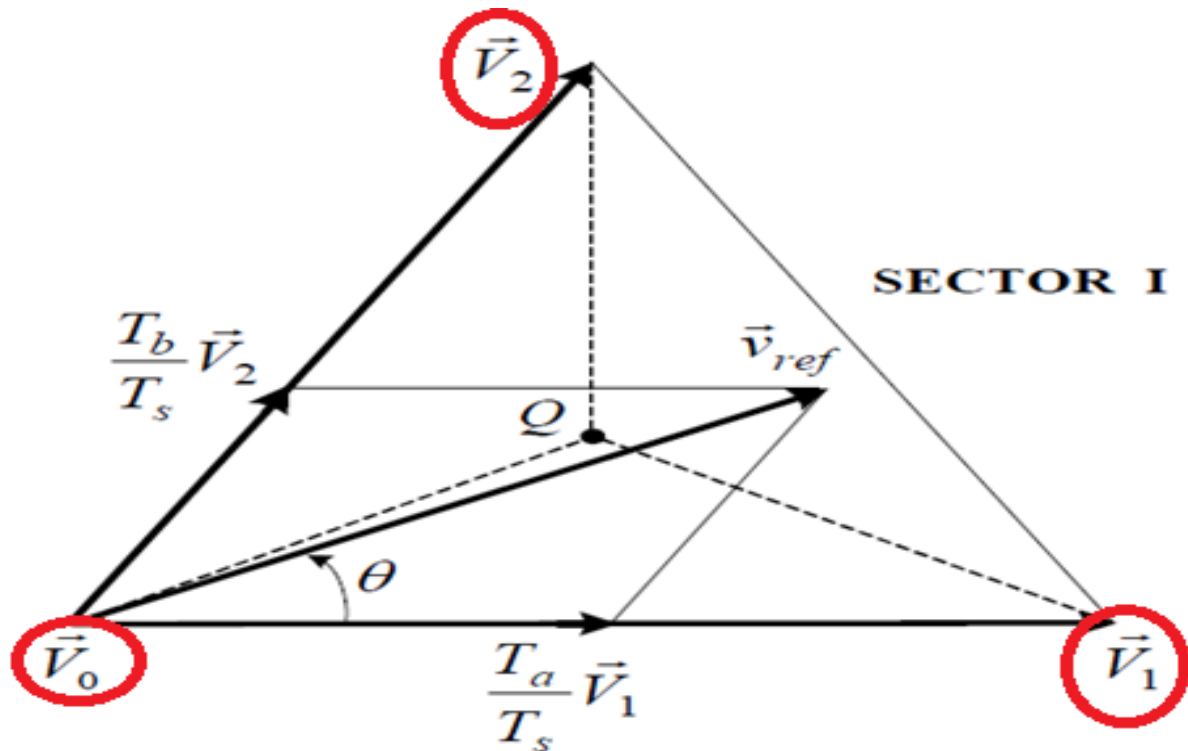
## c) Dwell Time Calculation

- Reference  $\vec{v}_{ref}$  can be synthesized by 3 stationary vectors.



Dwell time for stationary vectors represents:

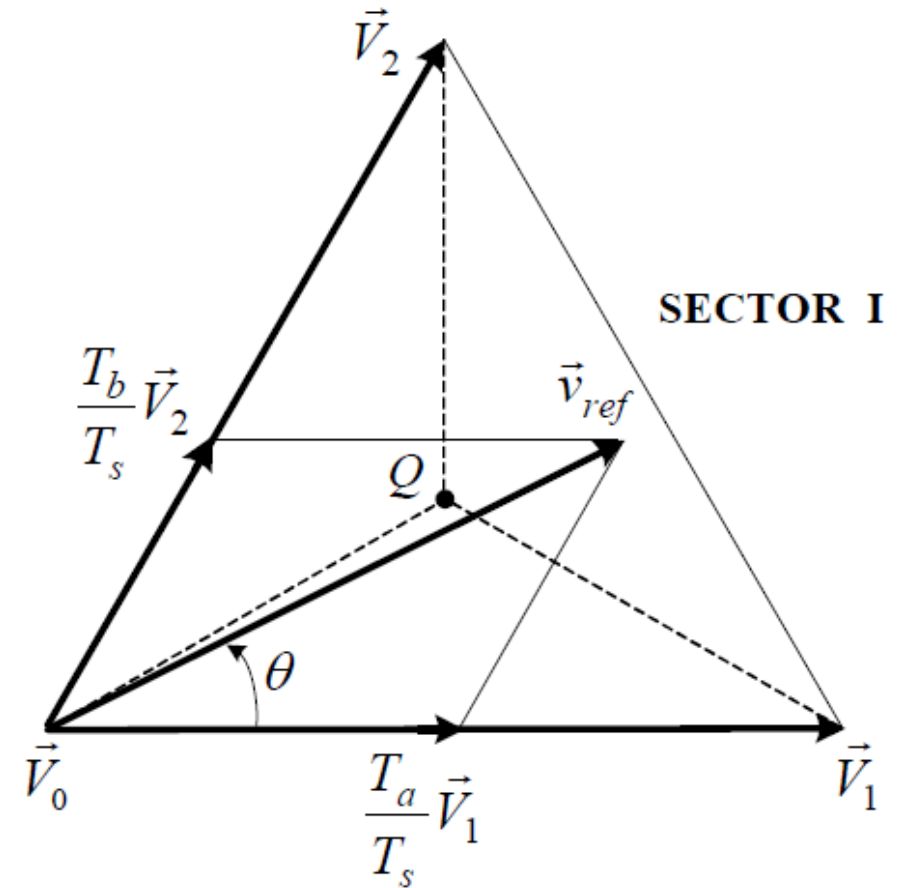
- Duty-cycle time (on-state or off-state time) of chosen switches during a sampling period  $T_s$ .


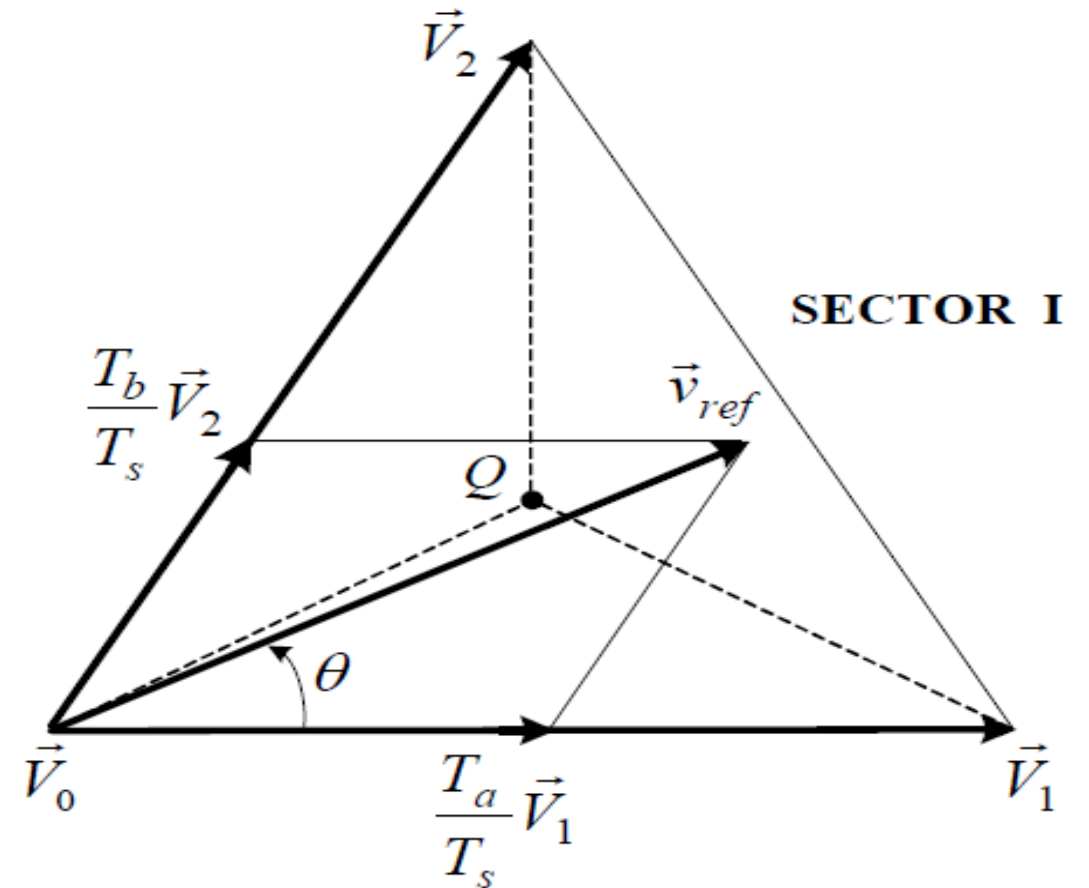
# Dwell time calculation is based on 'voltage-second balancing' principle:

- i.e, product of reference voltage  $\vec{v}_{ref}$  with sampling period  $T_s$  = Sum of voltage multiplied by time interval of chosen space vectors.


$$\begin{cases} \vec{v}_{ref} T_s = \vec{V}_1 T_a + \vec{V}_2 T_b + \vec{V}_0 T_0 \\ T_s = T_a + T_b + T_0 \end{cases}$$





Assumption: Sampling period  $T_s$  is sufficiently small, reference vector  $\vec{v}_{ref}$  can be considered constant during  $T_s$ .

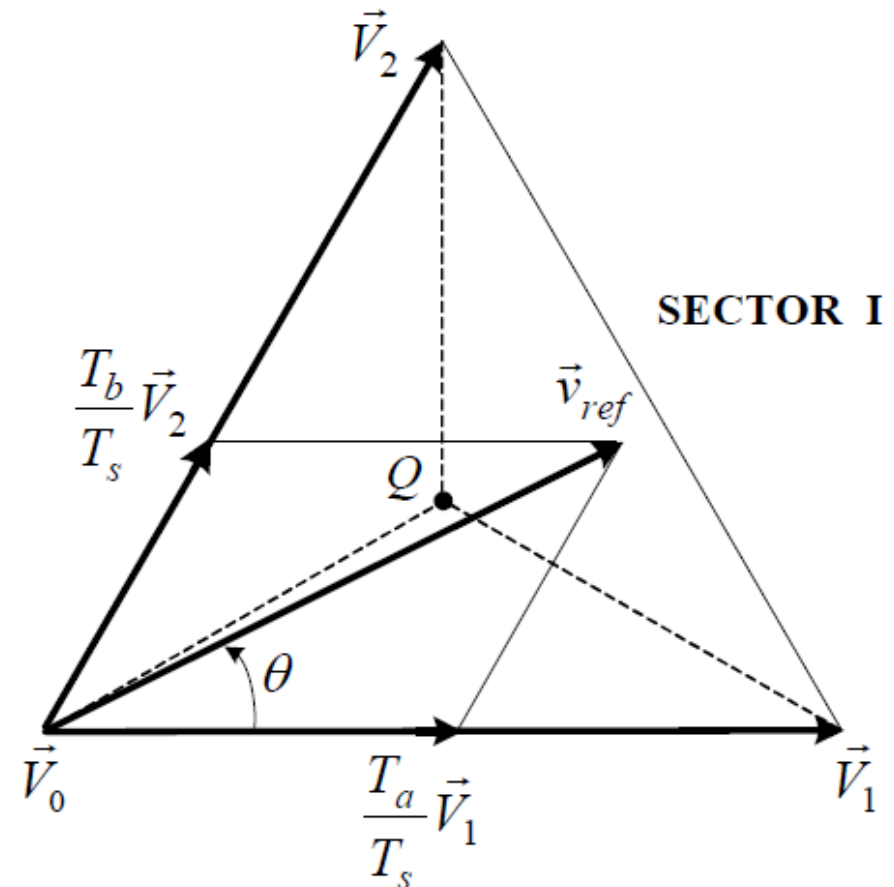- $\vec{v}_{ref}$  can be approximated by 2 adjacent active vectors & one 0 vector.
- e.g,  $\vec{v}_{ref}$  when falls into sector I as shown in Fig, it can be synthesized by  $\vec{V}_1$ ,  $\vec{V}_2$  and  $\vec{V}_0$



Volt-second balancing equation is:


$$\begin{cases} \vec{v}_{ref} T_s = \vec{V}_1 T_a + \vec{V}_2 T_b + \vec{V}_0 T_0 \\ T_s = T_a + T_b + T_0 \end{cases}$$

where  $T_a$ ,  $T_b$  and  $T_0$  are dwell times for vectors

$\vec{V}_1$ ,  $\vec{V}_2$  and  $\vec{V}_0$ , can be obtained by


$$\vec{v}_k = \left[ \frac{2}{3} V_{dc} e^{j(k-1)\frac{\pi}{3}} \right] k = 1, 2, \dots, 6$$
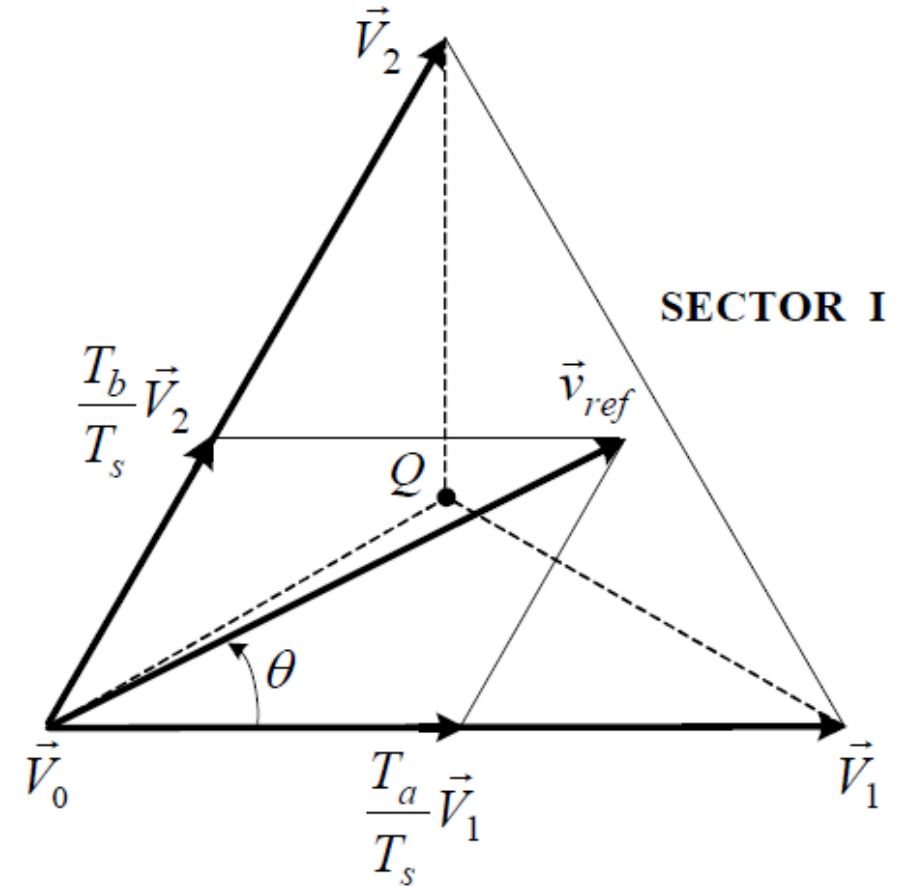
$$\vec{V}_1 = \frac{2}{3} V_{dc}, \quad \vec{V}_2 = \frac{2}{3} V_{dc} e^{j\frac{\pi}{3}} \quad \text{and} \quad \vec{V}_0 = 0$$



$v_{ref}$  represents length of reference vector

$$\vec{v}_{ref} = v_{ref} e^{j\theta}$$

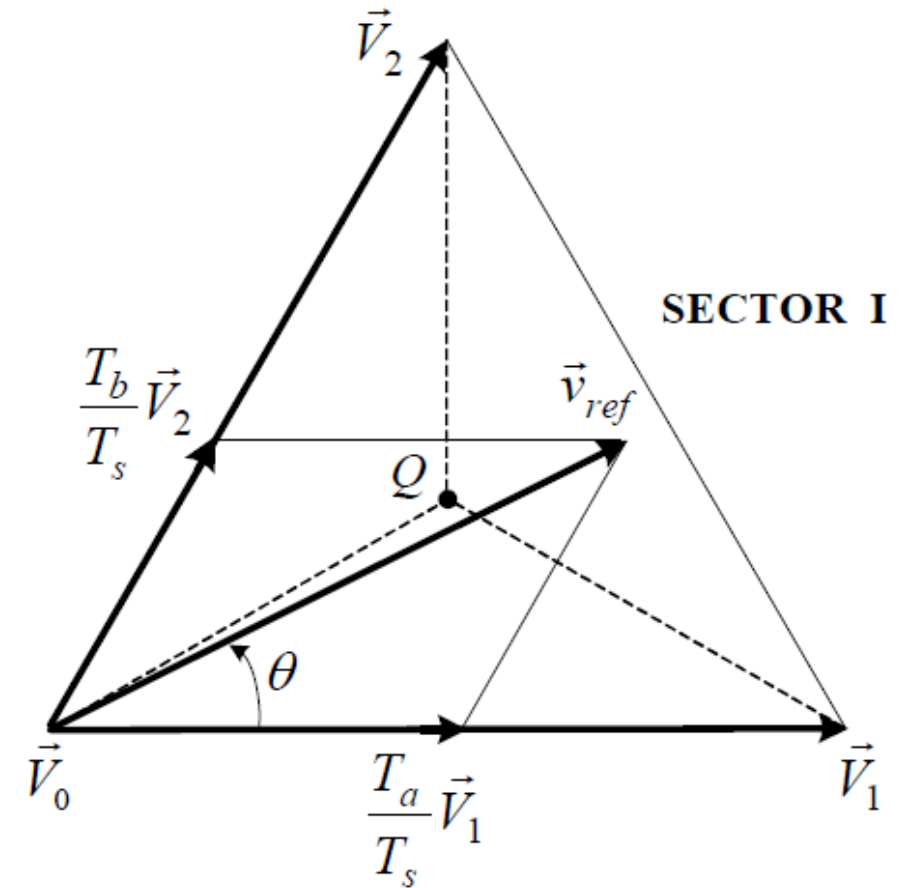

Substituting  $\vec{v}_{ref} = v_{ref} e^{j\theta}$ ,  $\vec{V}_1 = \frac{2}{3}V_{dc}$ ,  $\vec{V}_2 = \frac{2}{3}V_{dc} e^{j\frac{\pi}{3}}$  and  $\vec{V}_0 = 0$

into 
$$\begin{cases} \vec{v}_{ref} T_s = \vec{V}_1 T_a + \vec{V}_2 T_b + \vec{V}_0 T_0 \\ T_s = T_a + T_b + T_0 \end{cases}$$

& then splitting resultant equation into real ( $\alpha$ -axis) & imaginary ( $\beta$ -axis) components in  $\alpha$ - $\beta$  frame, we have

$$\begin{cases} \text{Re: } v_{ref} (\cos \theta) T_s = \frac{2}{3} V_{dc} T_a + \frac{1}{3} V_{dc} T_b \\ \text{Im: } v_{ref} (\sin \theta) T_s = \frac{1}{\sqrt{3}} V_{dc} T_b \end{cases}$$

Solving 
$$\begin{cases} \text{Re:} & v_{ref}(\cos \theta) T_s = \frac{2}{3} V_{dc} T_a + \frac{1}{3} V_{dc} T_b \\ \text{Im:} & v_{ref}(\sin \theta) T_s = \frac{1}{\sqrt{3}} V_{dc} T_b \end{cases}$$

together with  $T_s = T_a + T_b + T_0$  yields

$$\begin{cases} T_a = \frac{\sqrt{3} T_s v_{ref}}{V_{dc}} \sin\left(\frac{\pi}{3} - \theta\right) \\ T_b = \frac{\sqrt{3} T_s v_{ref}}{V_{dc}} \sin \theta \\ T_0 = T_s - T_a - T_b \end{cases} \quad \text{for } 0 \leq \theta < \pi/3$$


To visualize relationship between location of  $\vec{v}_{ref}$  and dwell times, let us examine some special cases.

If  $\vec{v}_{ref}$  lies exactly in middle between


$\vec{V}_1$  and  $\vec{V}_2$  (i.e.,  $\theta = \pi / 6$ ),

- Dwell time  $T_a$  of  $\vec{V}_1$  will be equal to dwell time  $T_b$  of  $\vec{V}_2$
- i.e  $T_a = T_b$
- Because:
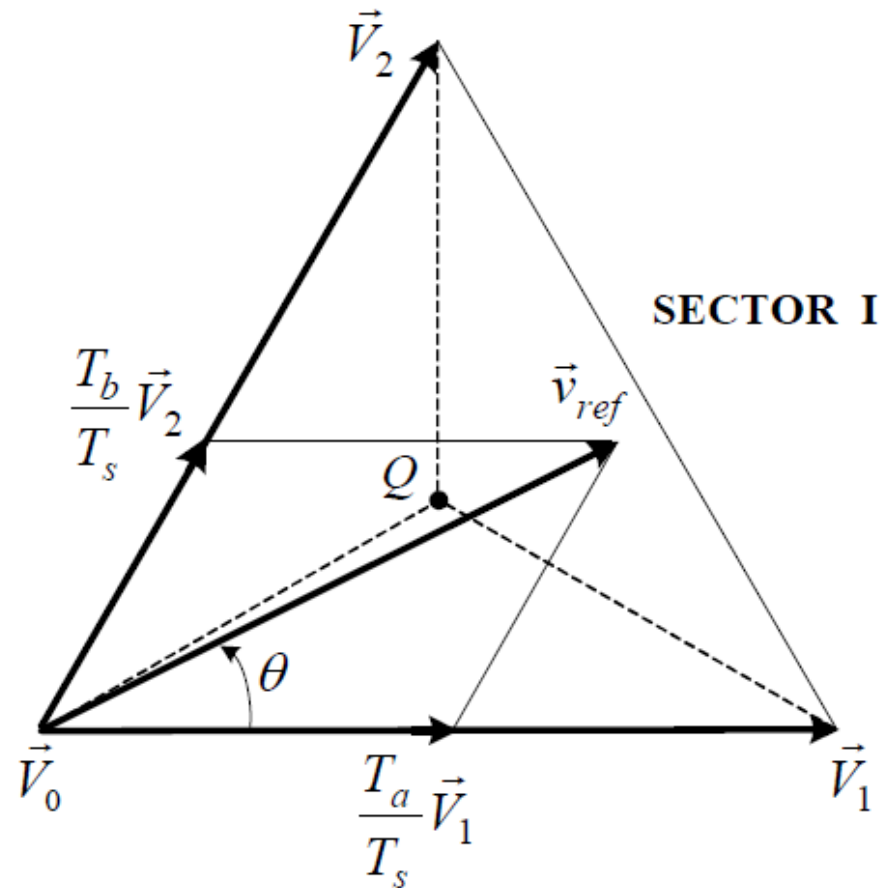
$$\frac{T_b}{T_s} \vec{V}_2 = \frac{T_a}{T_s} \vec{V}_1$$




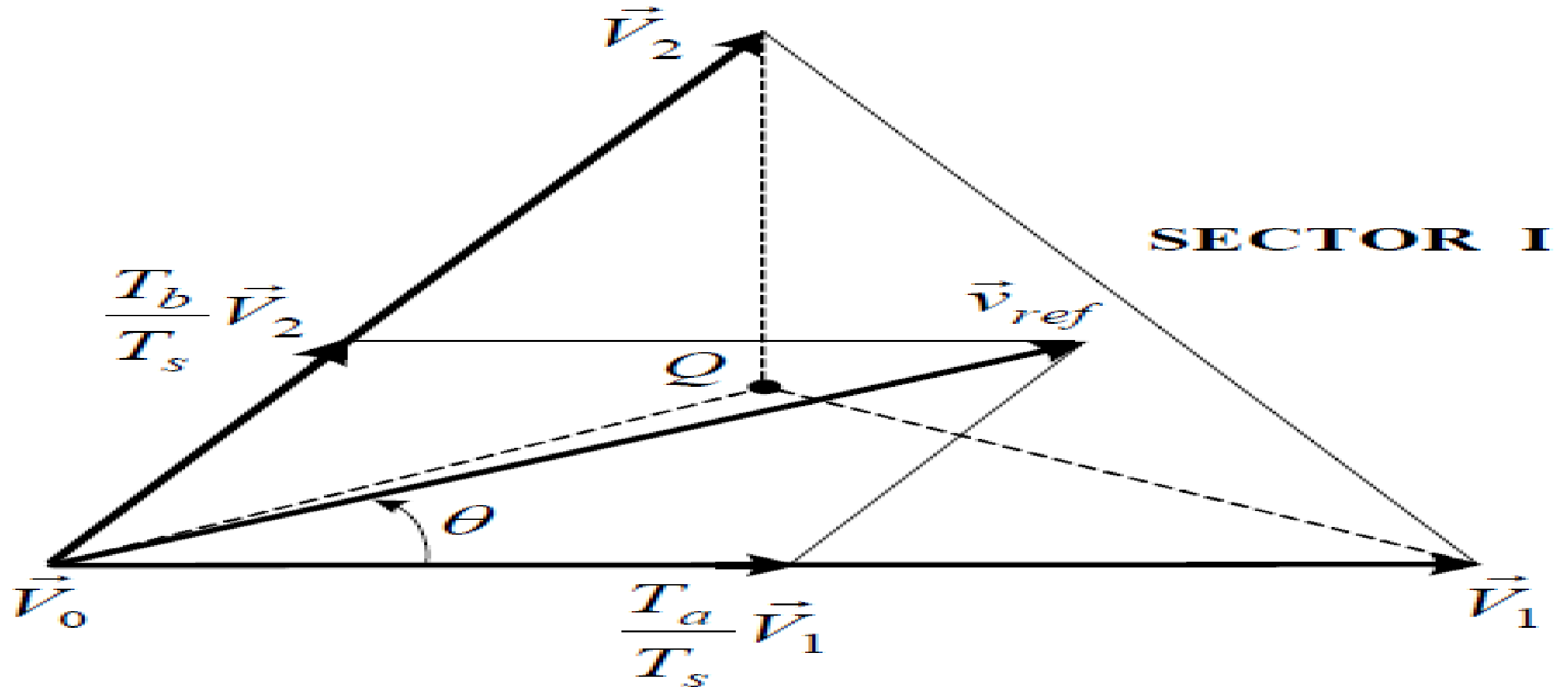When  $\vec{v}_{ref}$  is closer to  $\vec{V}_2$ ,  $T_b > T_a$






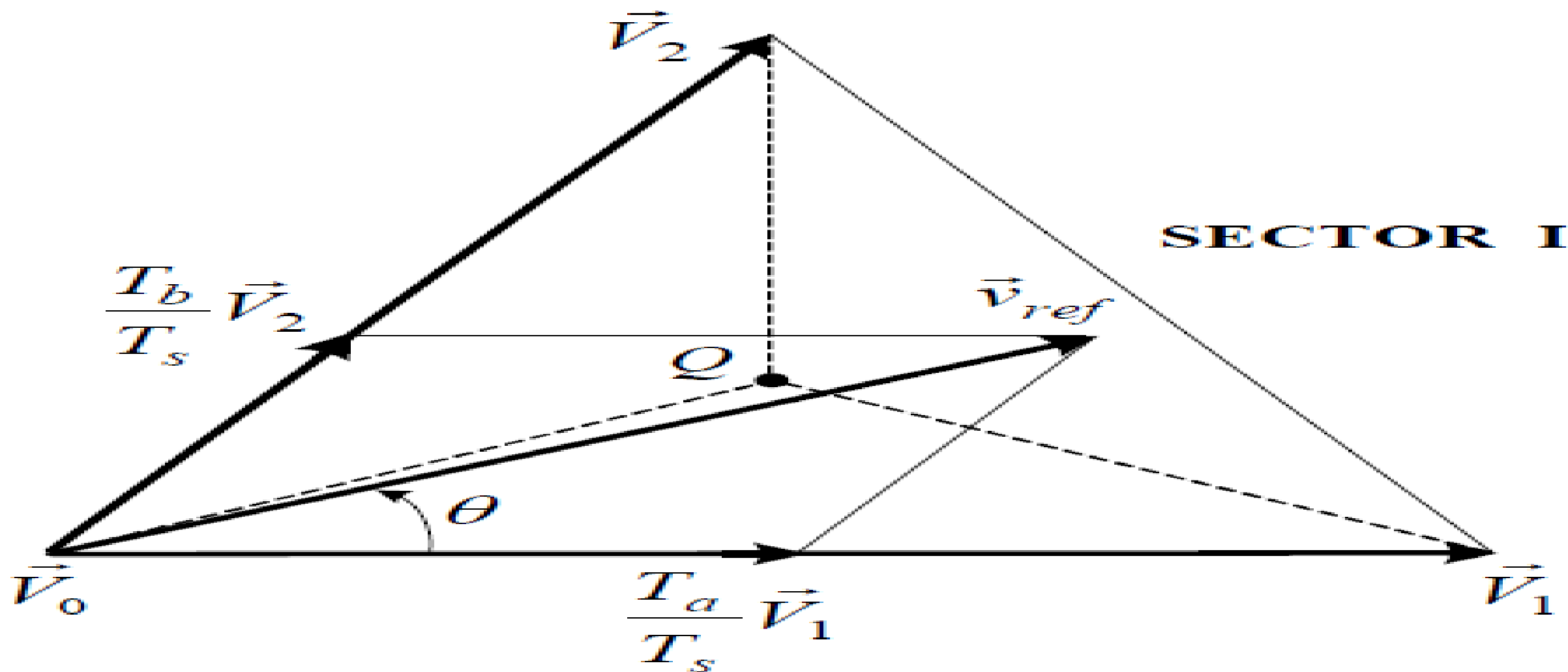If  $\vec{v}_{ref}$  is coincident with  $\vec{V}_2$ ,  $T_a=0$




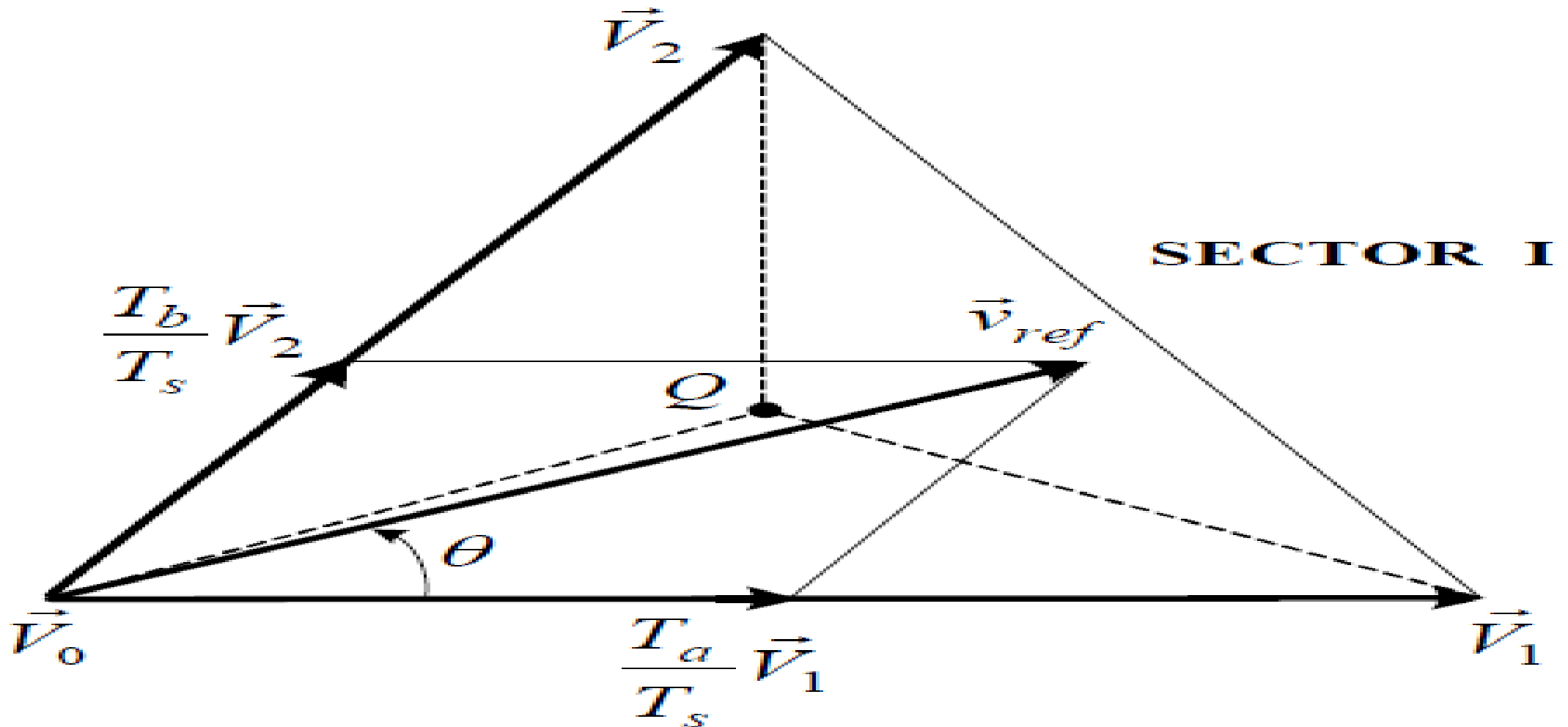With head of  $\vec{v}_{ref}$  located right on central point  $Q$ ,  
 $T_a = T_b = T_0$



Relationship between  $\vec{v}_{ref}$  location & dwell times is summarized in Table

$\vec{v}_{ref}$ Location	$\theta = 0$	$0 < \theta < \frac{\pi}{6}$	$\theta = \frac{\pi}{6}$	$\frac{\pi}{6} < \theta < \frac{\pi}{3}$	$\theta = \frac{\pi}{3}$
Dwell Times	$T_a > 0$ $T_b = 0$	$T_a > T_b$	$T_a = T_b$	$T_a < T_b$	$T_a = 0$ $T_b > 0$


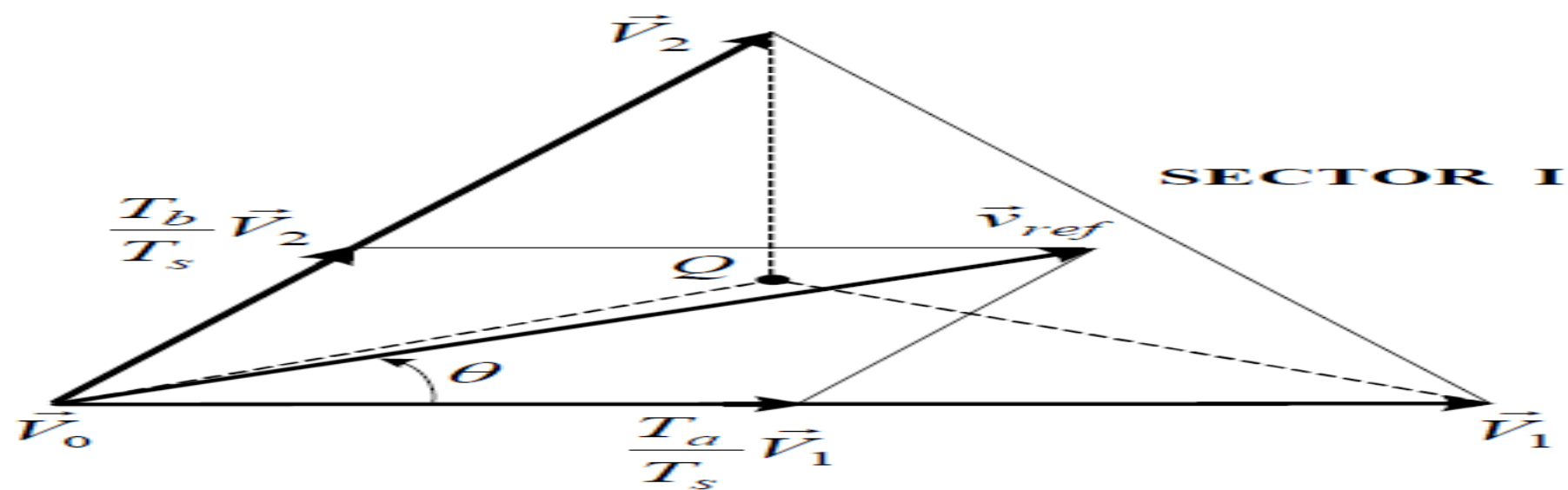


Although equation

$$\begin{cases} T_a = \frac{\sqrt{3} T_s v_{ref}}{V_{dc}} \sin(\frac{\pi}{3} - \theta) \\ T_b = \frac{\sqrt{3} T_s v_{ref}}{V_{dc}} \sin \theta \\ T_o = T_s - T_a - T_b \end{cases}$$

for  $0 \leq \theta < \pi/3$

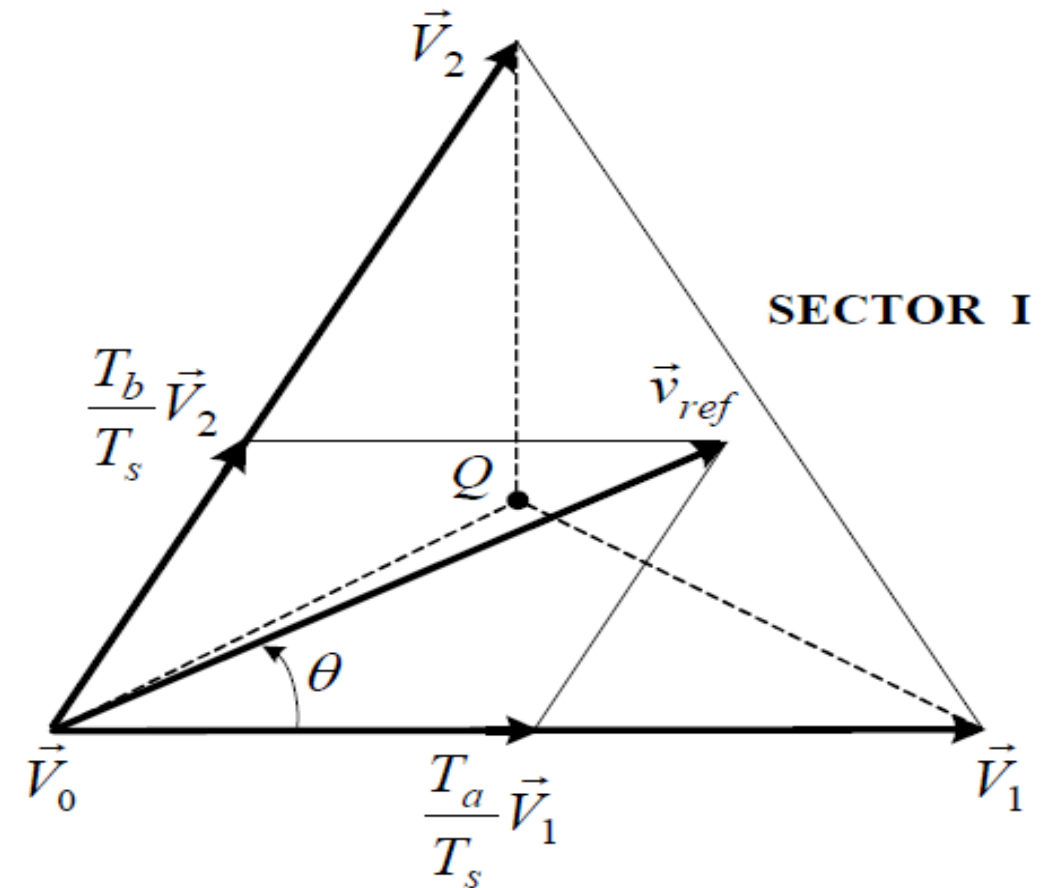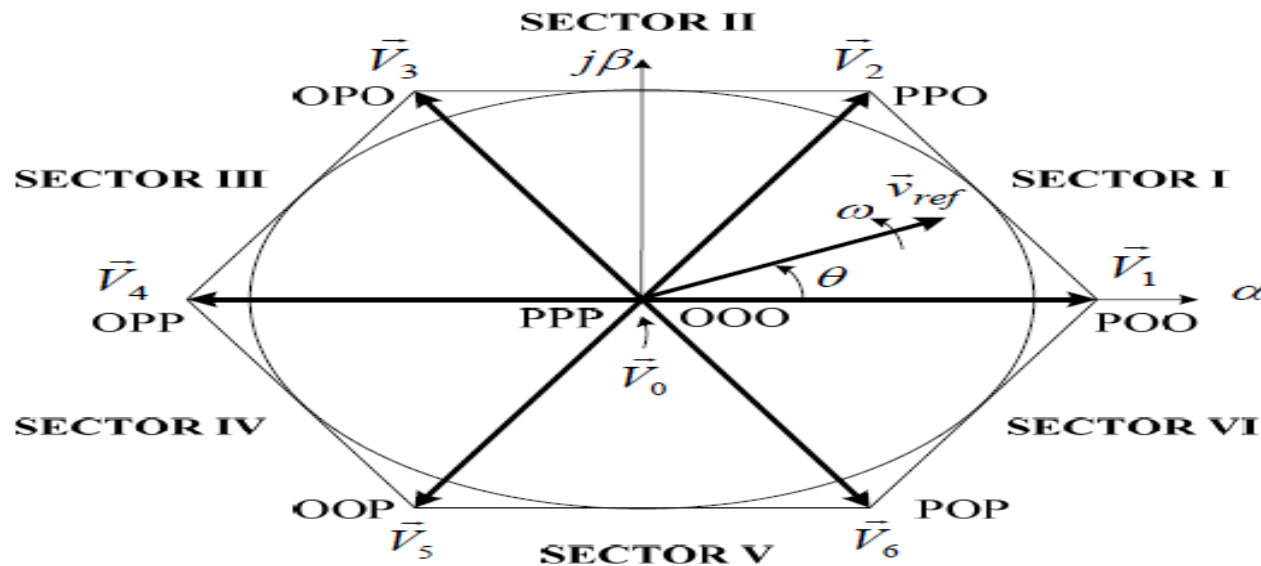- is derived when  $\vec{v}_{ref}$  is in sector I,
- it can also be used when  $\vec{v}_{ref}$  is in other sectors?



Answer: Yes


Although equation

$$\begin{cases} T_a = \frac{\sqrt{3} T_s v_{ref}}{V_{dc}} \sin(\frac{\pi}{3} - \theta) \\ T_b = \frac{\sqrt{3} T_s v_{ref}}{V_{dc}} \sin \theta \\ T_0 = T_s - T_a - T_b \end{cases} \quad \text{for } 0 \leq \theta < \pi/3$$

- is derived when  $\vec{v}_{ref}$  is in sector I, it can also be used when  $\vec{v}_{ref}$  is in other sectors provided that a multiple of  $\pi/3$  is subtracted from actual angular displacement  $\theta$  such that modified angle  $\theta'$  falls into range between 0 &  $\pi/3$  for use in equation, i.e,

$$\theta' = \theta - (k-1)\pi/3 \quad \text{for } 0 \leq \theta' < \pi/3$$

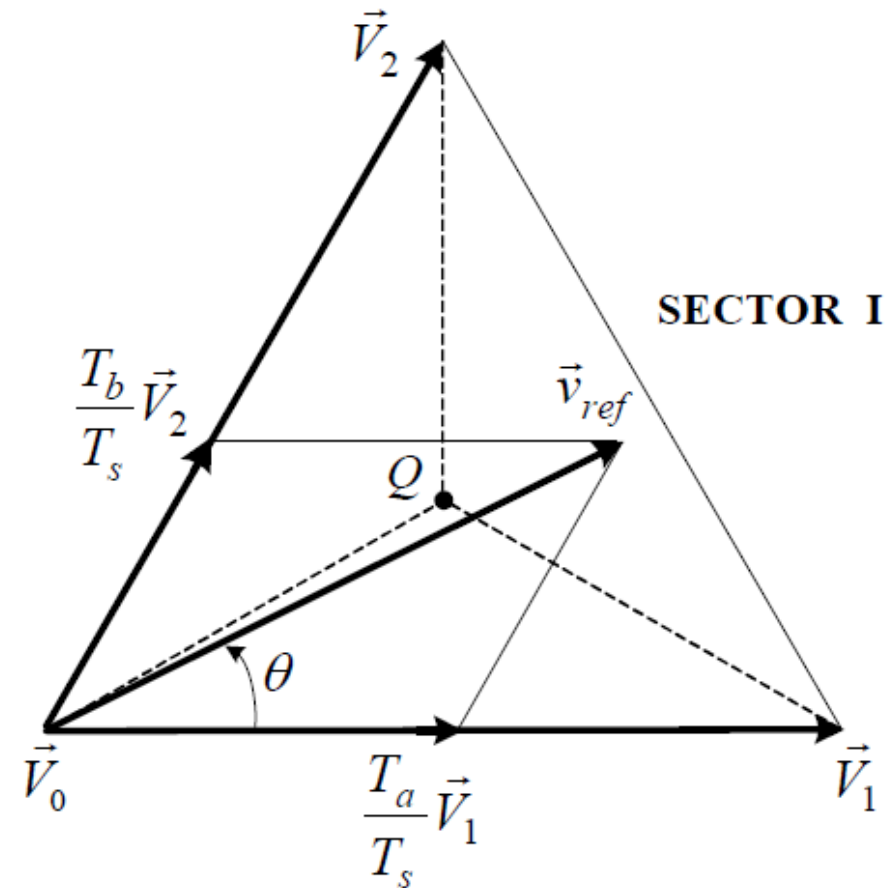- where  $k = 1, 2, \dots, 6$  for sectors I, II, ..., VI, respectively.



## d) Modulation Index

- Equation 
$$\begin{cases} T_a = \frac{\sqrt{3} T_s v_{ref}}{V_{dc}} \sin(\frac{\pi}{3} - \theta) \\ T_b = \frac{\sqrt{3} T_s v_{ref}}{V_{dc}} \sin \theta \\ T_0 = T_s - T_a - T_b \end{cases} \quad \begin{cases} T_a = T_s m_a \sin(\frac{\pi}{3} - \theta) \\ T_b = T_s m_a \sin \theta \\ T_0 = T_s - T_a - T_b \end{cases}$$
- can also be expressed in terms of modulation index  $m_a = \frac{\sqrt{3} v_{ref}}{V_{dc}}$

Length of reference vector  $\vec{v}_{ref}$  represents peak value of fundamental-frequency component in inverter output phase voltage, i.e.,  $v_{ref} = \hat{V}_{a1} = \sqrt{2} V_{a1}$

where  $V_{a1}$  is rms value of fundamental component in inverter output phase (phase-a) voltage.

## Relationship between $m_a$ & $V_{a1}$

Substituting  $v_{ref} = \hat{V}_{a1} = \sqrt{2}V_{a1}$  into  $m_a = \frac{\sqrt{3} v_{ref}}{V_{dc}}$

$$m_a = \frac{\sqrt{3} v_{ref}}{V_{dc}} = \frac{\sqrt{6} V_{a1}}{V_{dc}}$$

For a given dc voltage  $V_{dc}$ , inverter output voltage  $V_{a1}$  is proportional to modulation index  $m_a$ .


$$V_{a1} \propto m_a$$



Maximum length of reference vector,  $v_{ref,max}$ , corresponds to radius of largest circle that can be inscribed within hexagon as shown in Fig.

- Since hexagon is formed by 6 active vectors having a length of  $2V_{dc}/3$ ,  $v_{ref,max}$ , can be found from
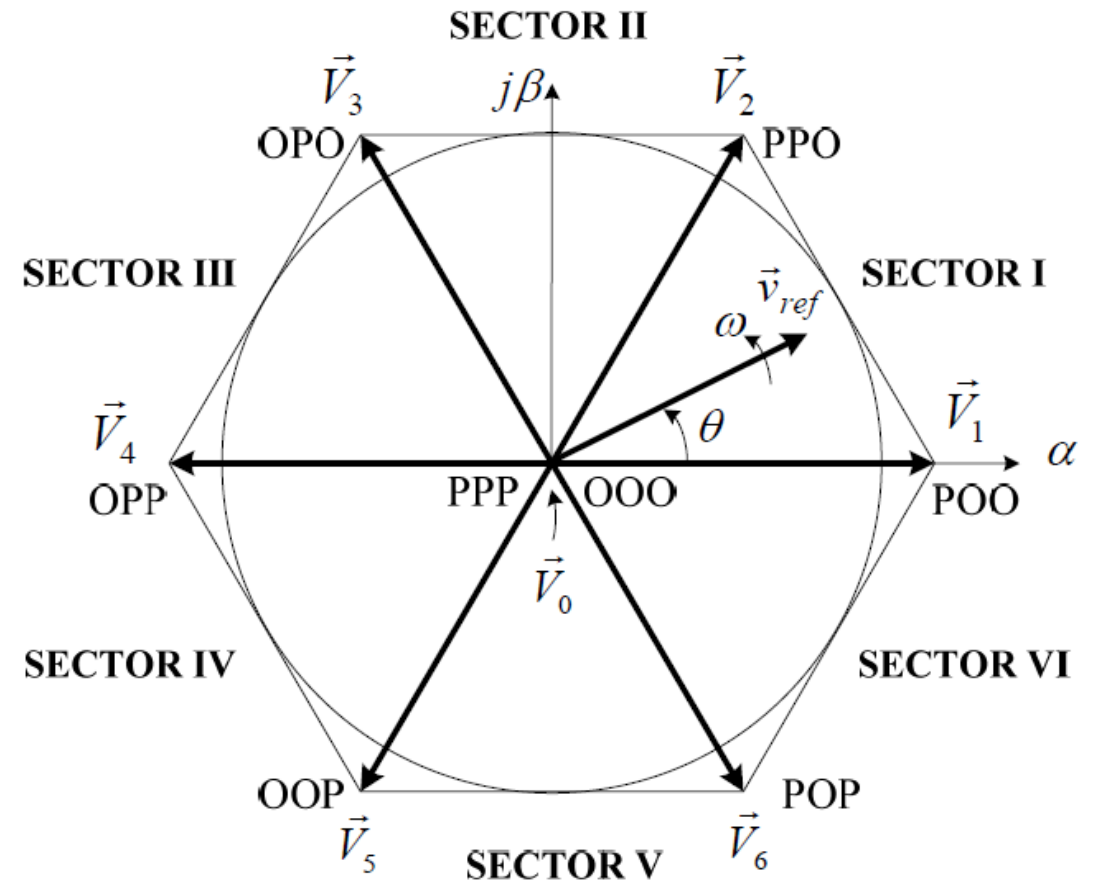
$$v_{ref,max} = \frac{2}{3}V_{dc} \times \frac{\sqrt{3}}{2} = \frac{V_{dc}}{\sqrt{3}}$$



Substituting  $v_{ref, \max} = \frac{V_{dc}}{\sqrt{3}}$  into  $m_a = \frac{\sqrt{3} v_{ref}}{V_{dc}}$

- Gives the maximum modulation index  $m_{a, \max} = 1$

from which modulation index for SVM scheme is in range of


$$0 \leq m_a \leq 1$$

## e) Switching Sequence

- With space vectors selected & their dwell times calculated,
- next step is to **arrange switching sequence**.
- In general, switching sequence design for a given  $\vec{v}_{ref}$  is not unique,
- but it should satisfy following 2 requirements for minimization of device switching frequency:


1<sup>st</sup> requirement for minimization of device switching frequency

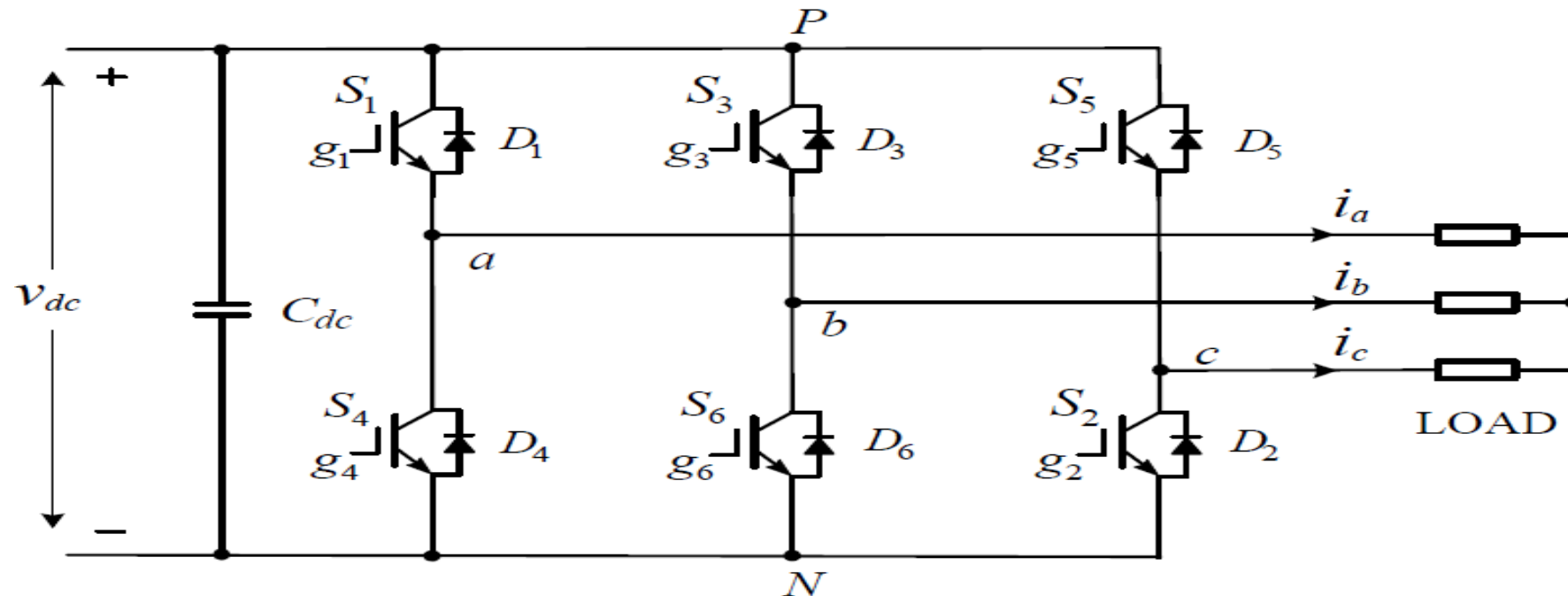a) Transition from one switching state to next involves only 2 switches in same inverter leg, one being switched on & other switched off





## 2<sup>nd</sup> requirement for minimization of device switching frequency

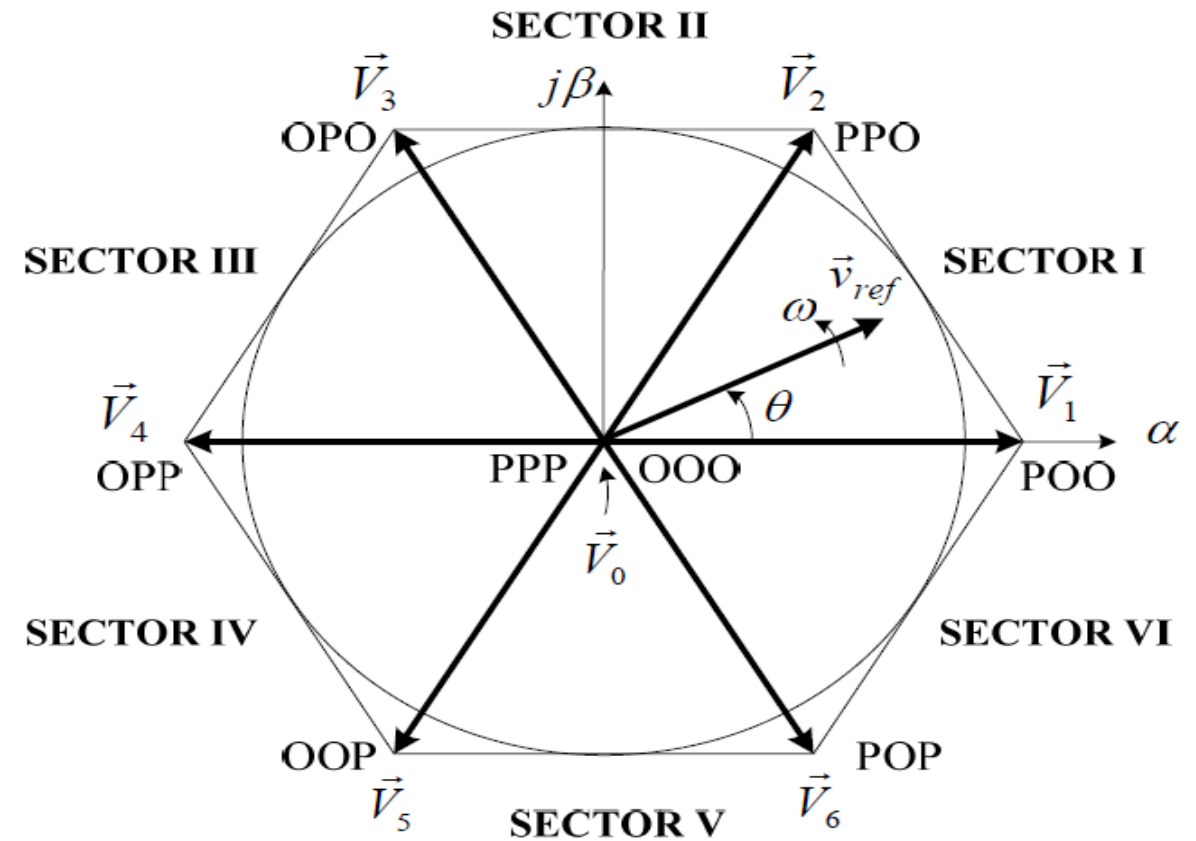
b) Transition for  $\vec{v}_{ref}$  moving from 1 sector in space vector diagram to next requires no or minimum number of switchings.



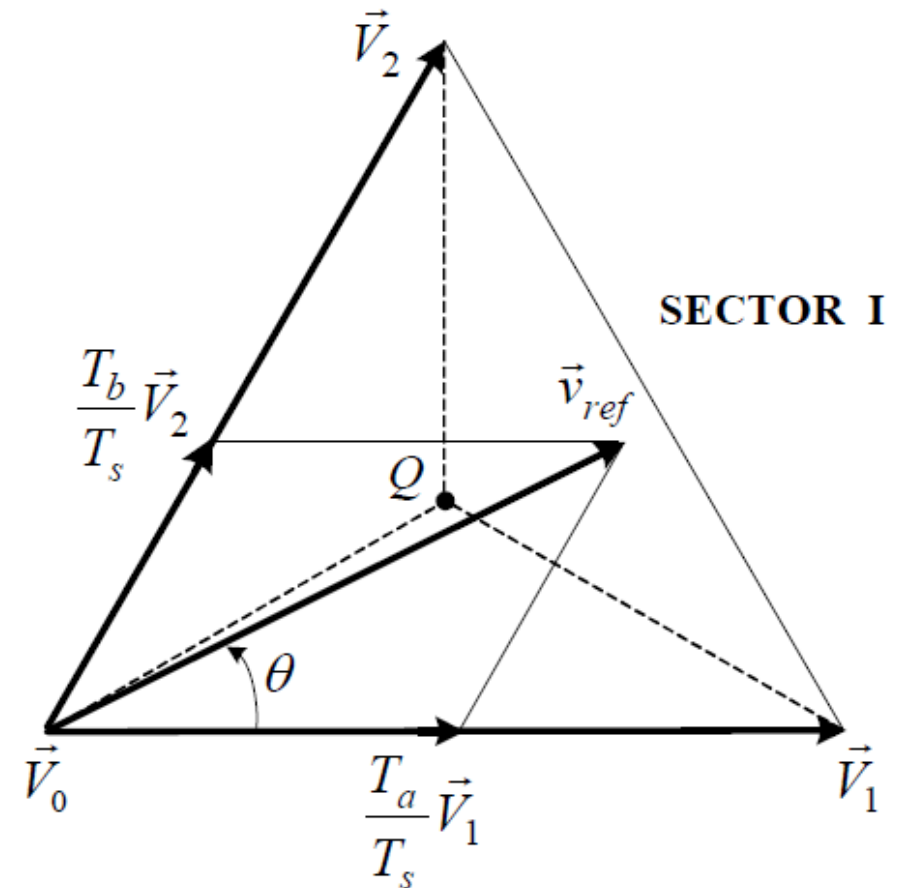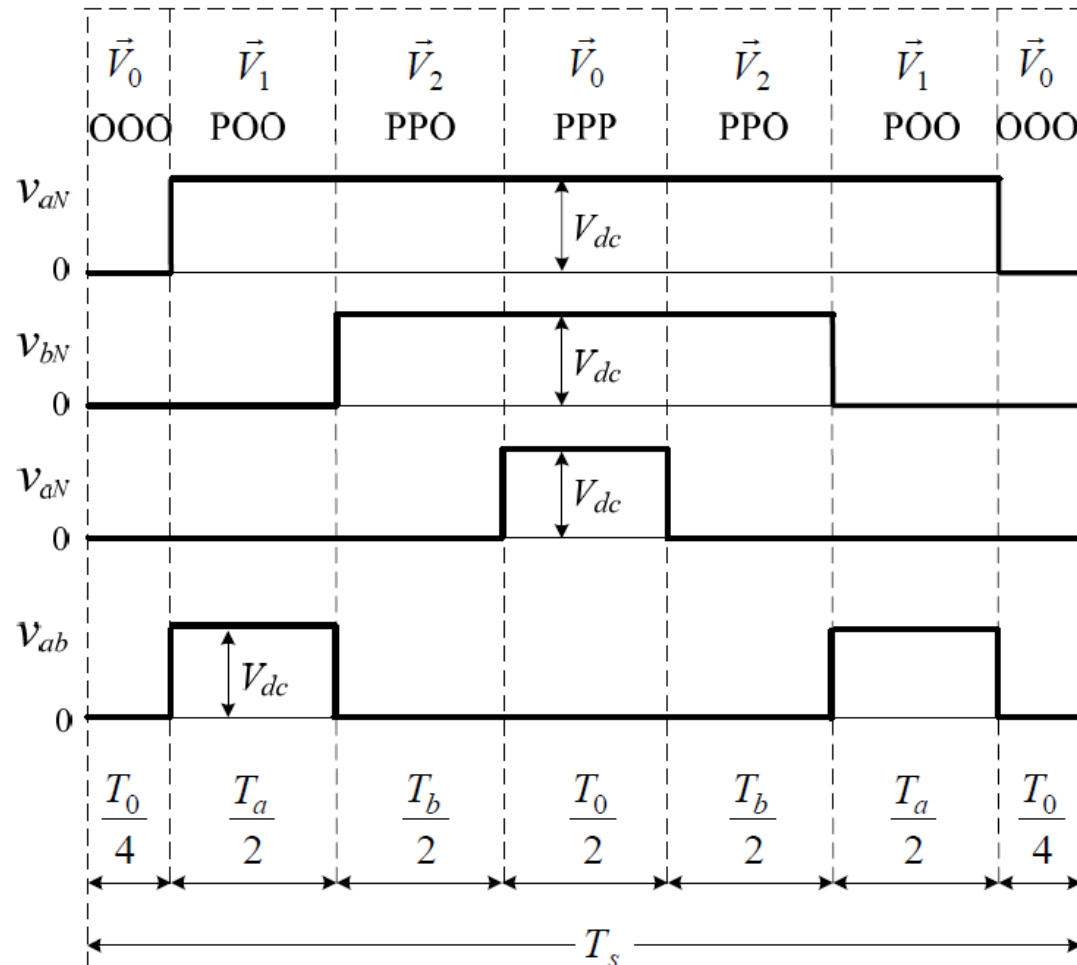Seven-segment switching sequence & inverter output voltage waveforms for  $\vec{v}_{ref}$  in sector I, where  $\vec{v}_{ref}$  is synthesized by  $\vec{V}_1$ ,  $\vec{V}_2$  and  $\vec{V}_0$




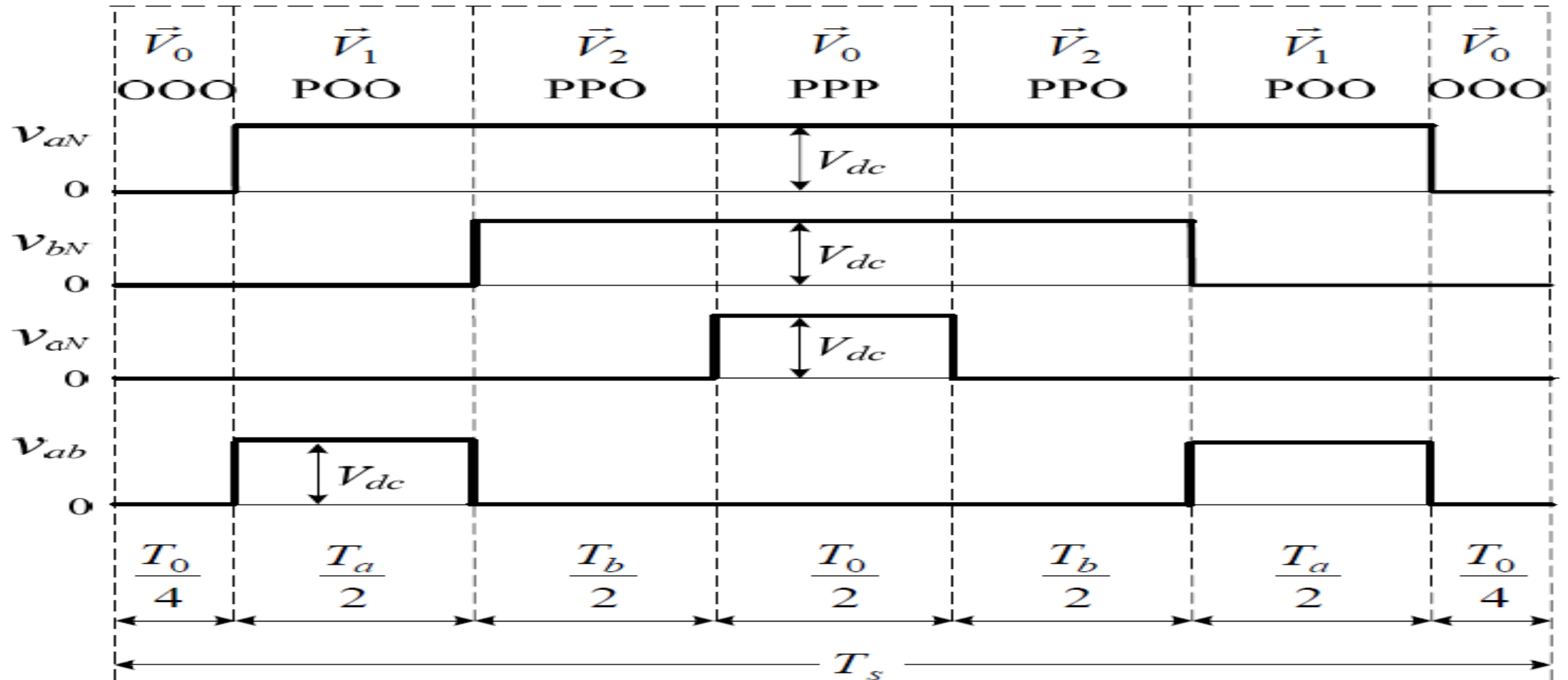Sampling period  $T_s$  is divided into 7 segments for selected vectors.



It can be observed that:


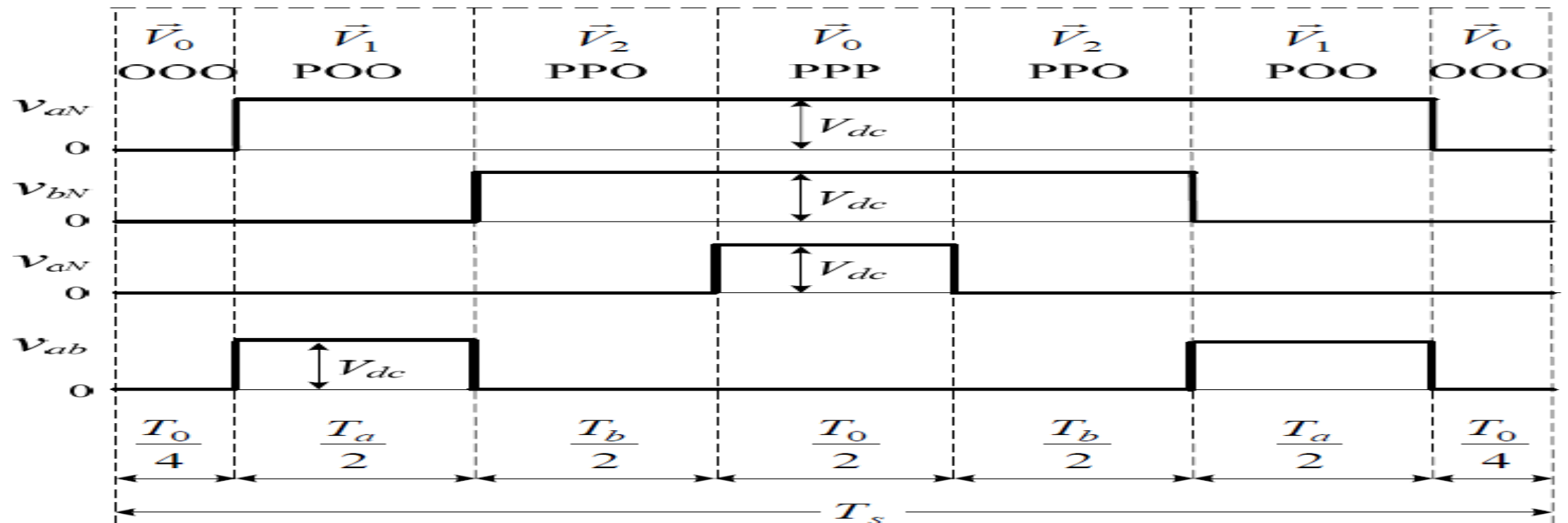
- Dwell times for 7 segments add up to the sampling period  
 $(T_s = T_a + T_b + T_0)$





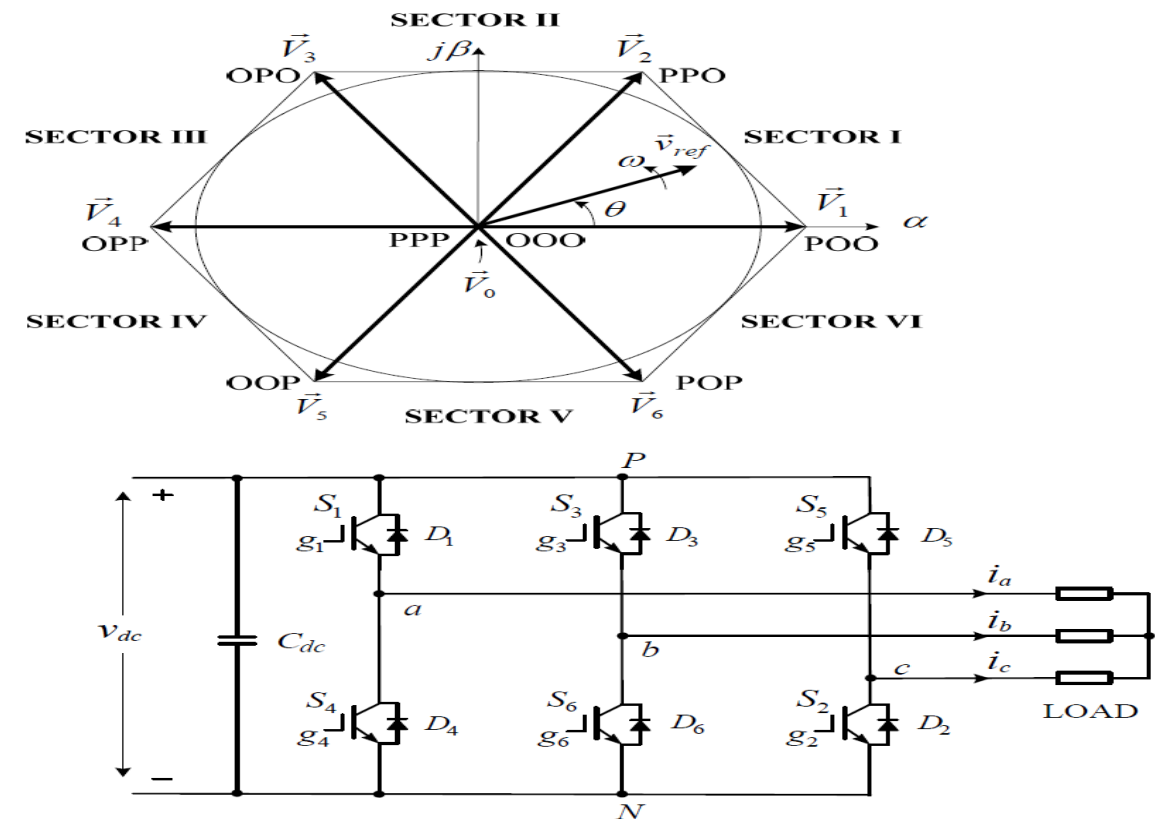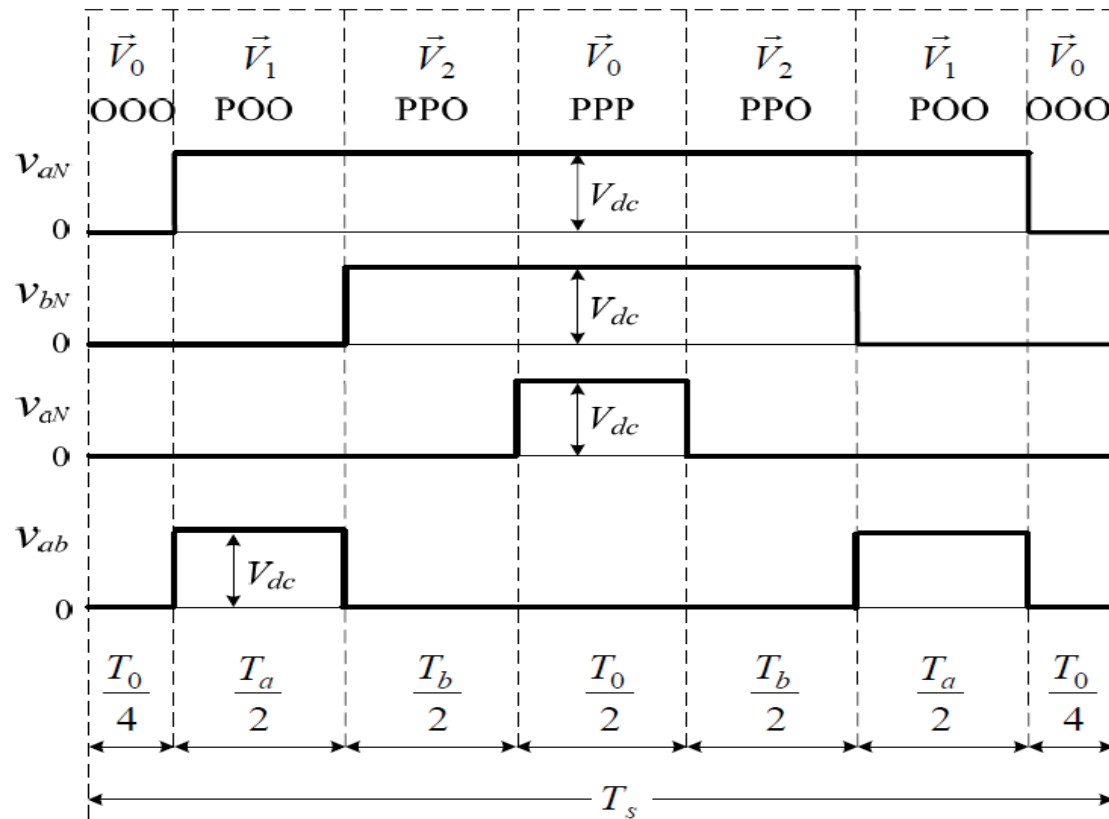
# Design requirement a) is satisfied.


- For instance, transition from [000] to [POO] is accomplished by turning  $S_1$  on &  $S_4$  off, which involves only 2 switches;



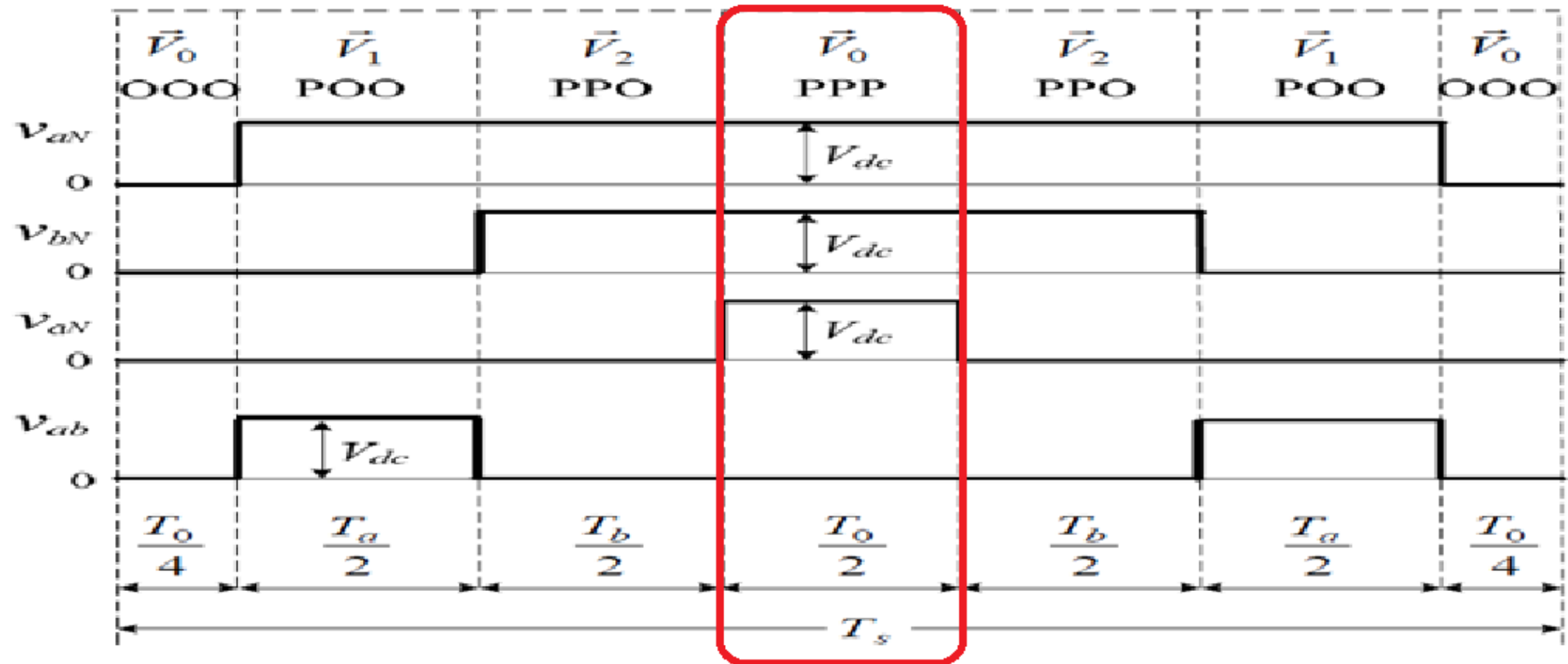For  $T_0/2$  segment in centre of sampling period, switching state [PPP] is selected



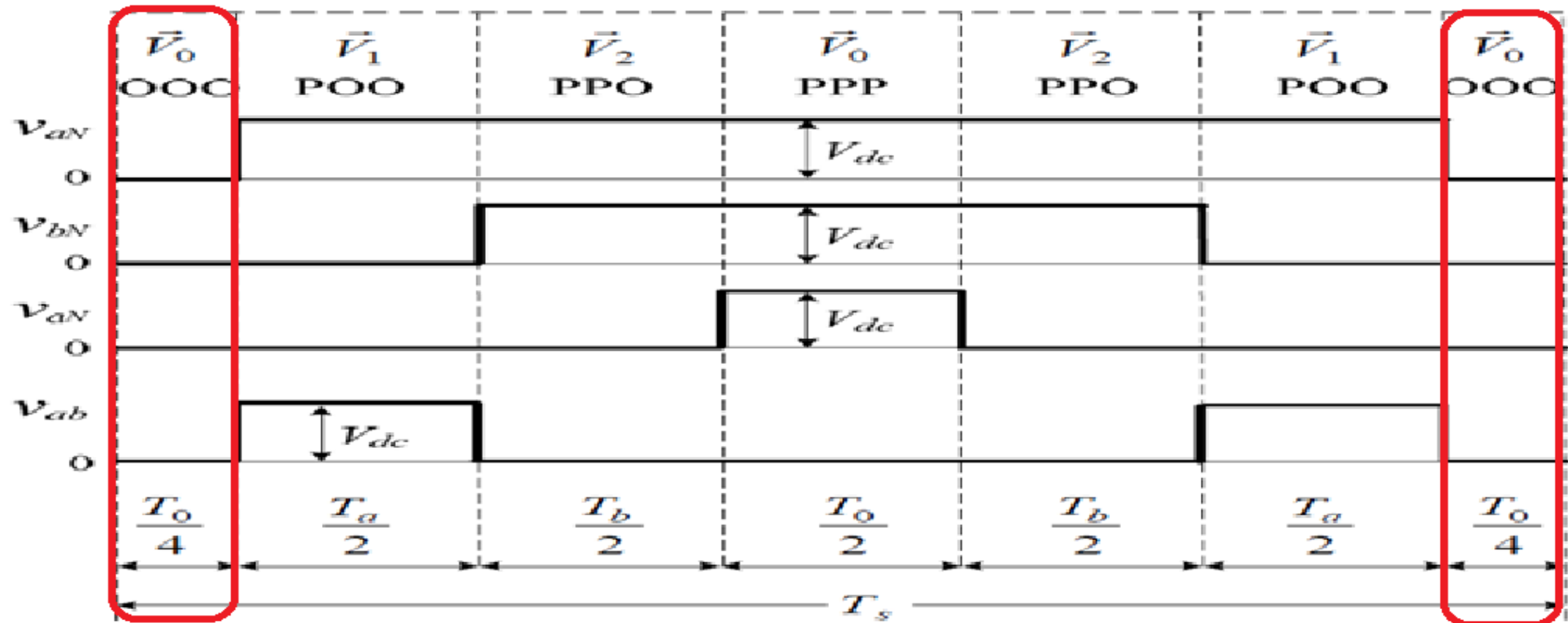
For  $T_0 / 4$  segments on both sides, state [000] is used






# Case Study 4-3 Two-level Voltage Source Inverter with Space Vector Modulation


- In this case study, procedure for computer simulation & real-time digital implementation of SVM scheme is introduced.
- Simulation for 2-level voltage source inverter in performance, & harmonic performance of SVM scheme is analysed.
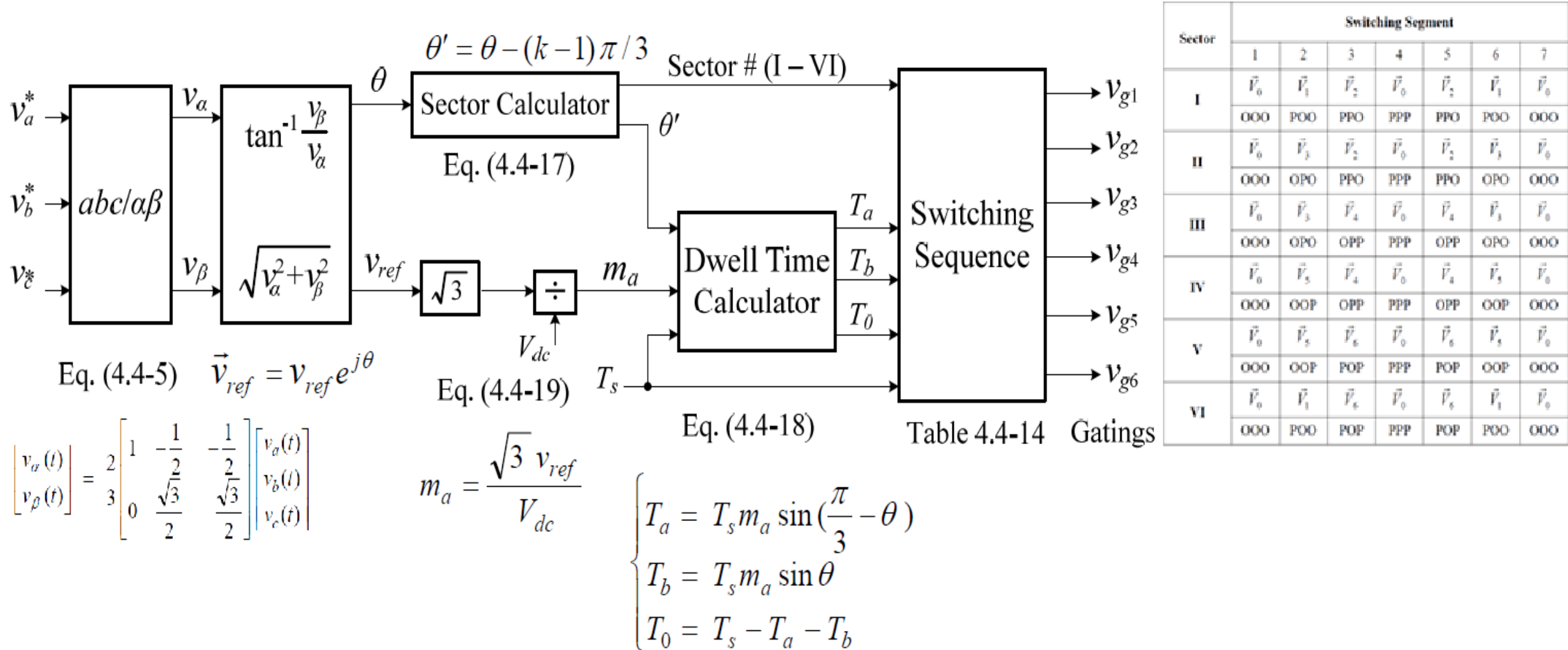
# Block diagram for computer simulation & real-time digital implementation of SVM algorithm.




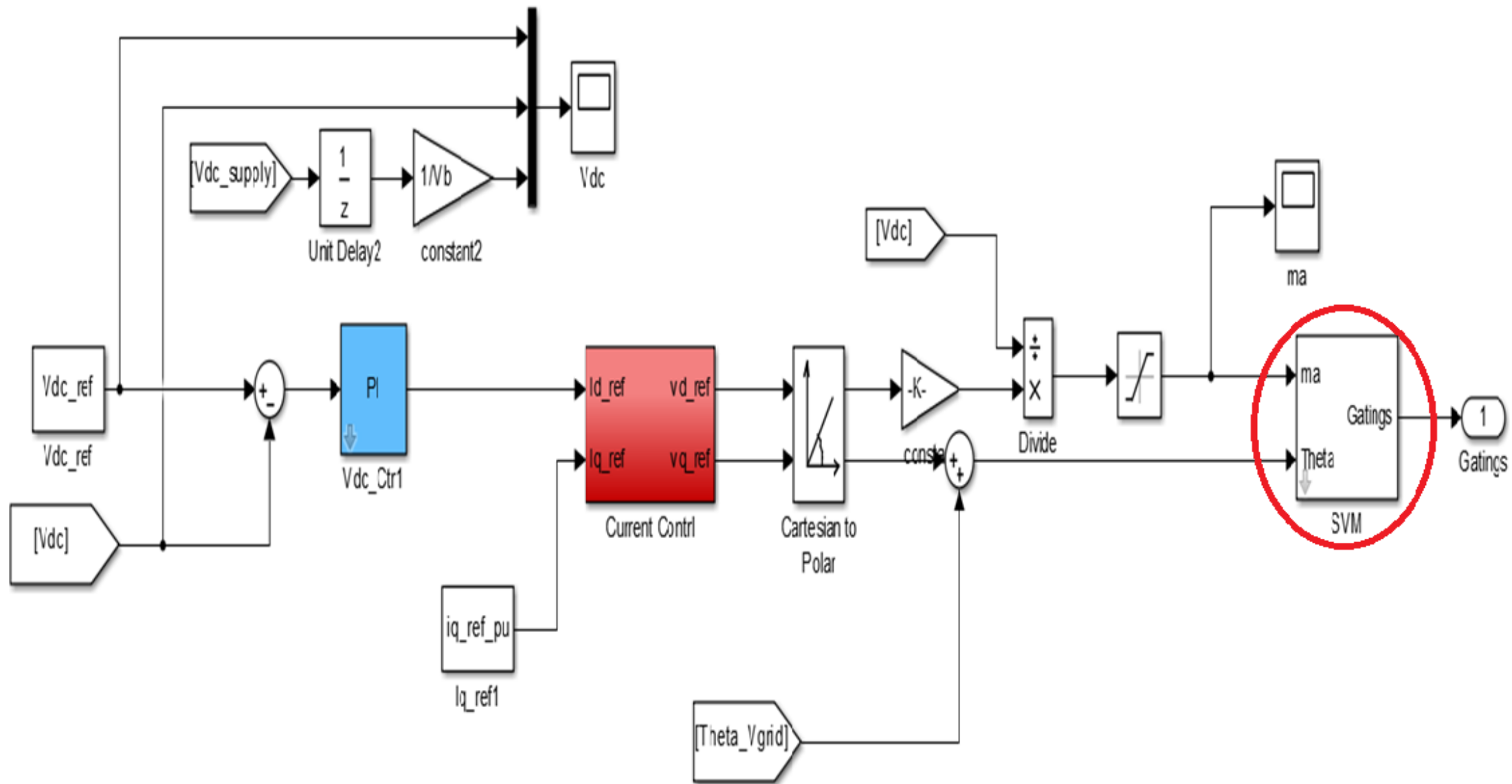

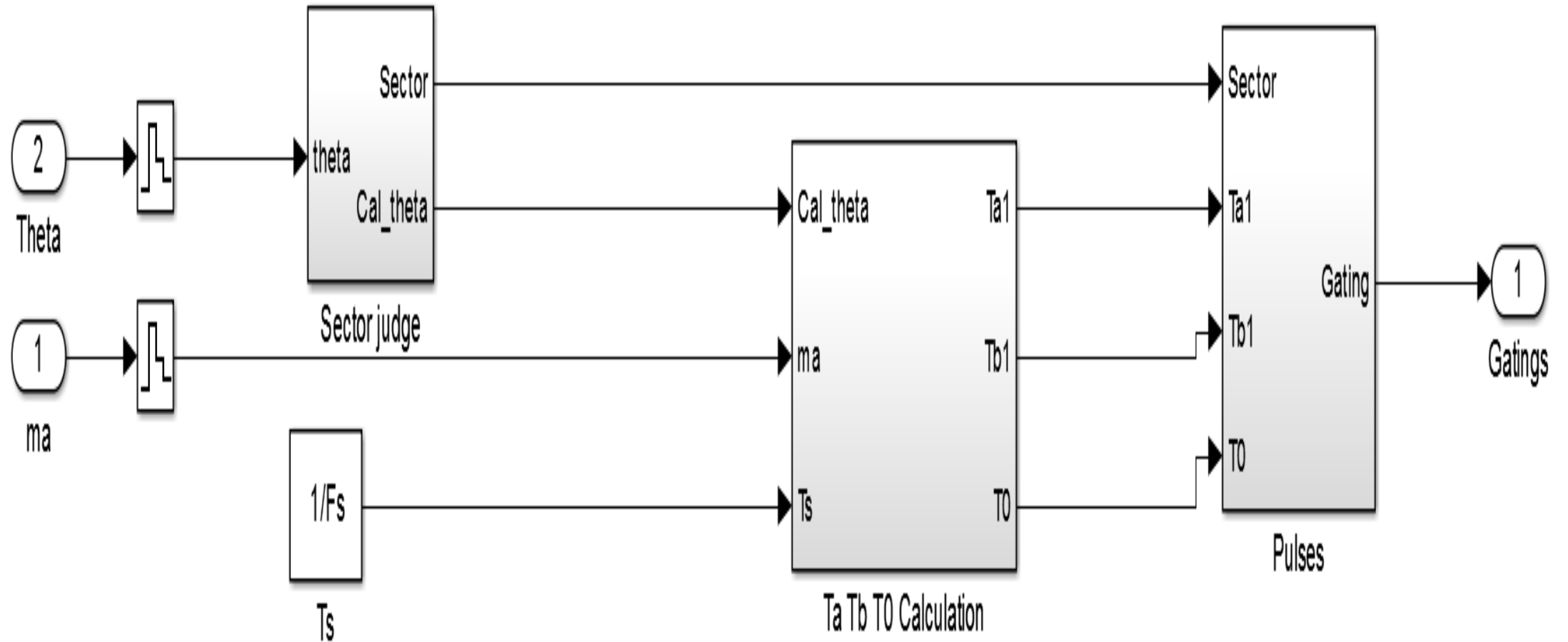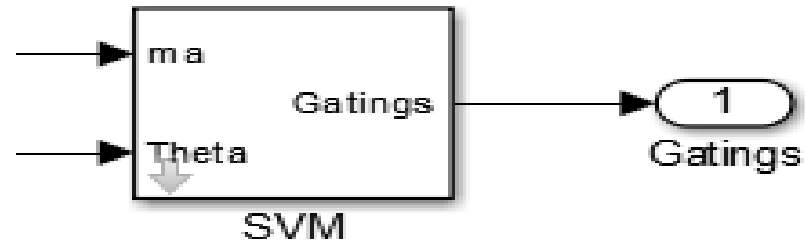


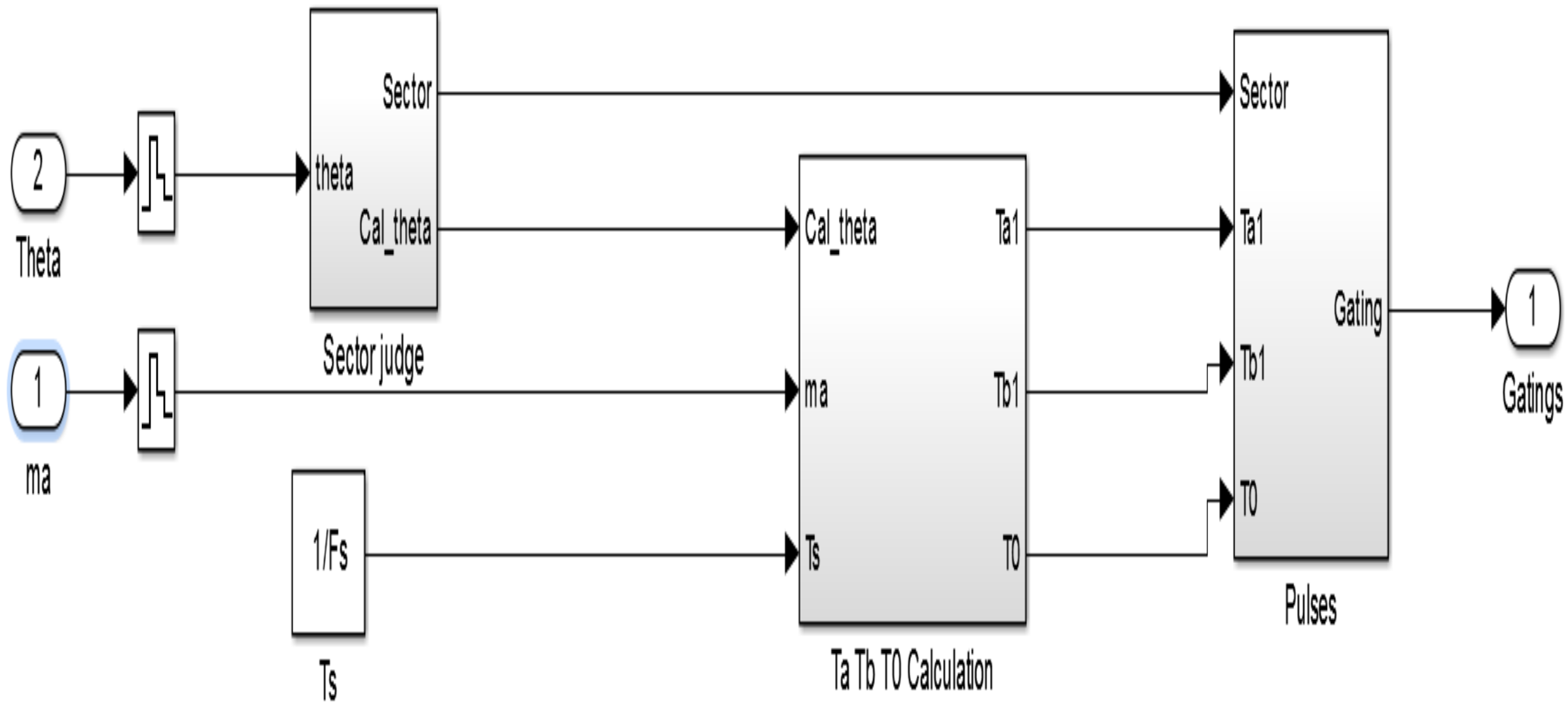



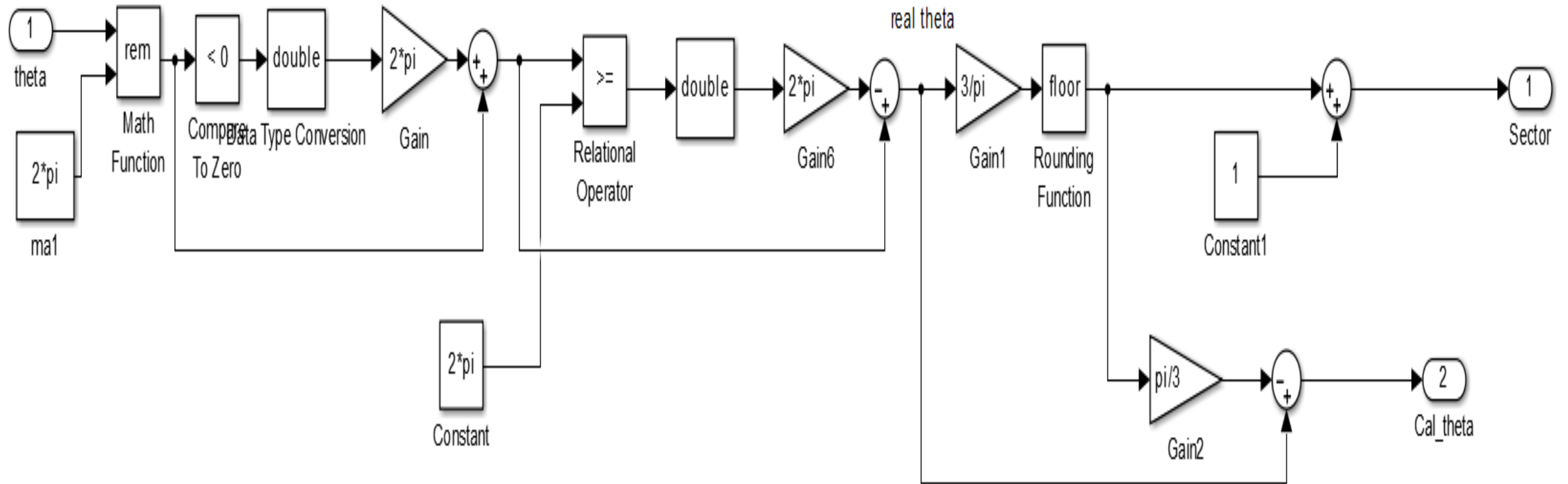

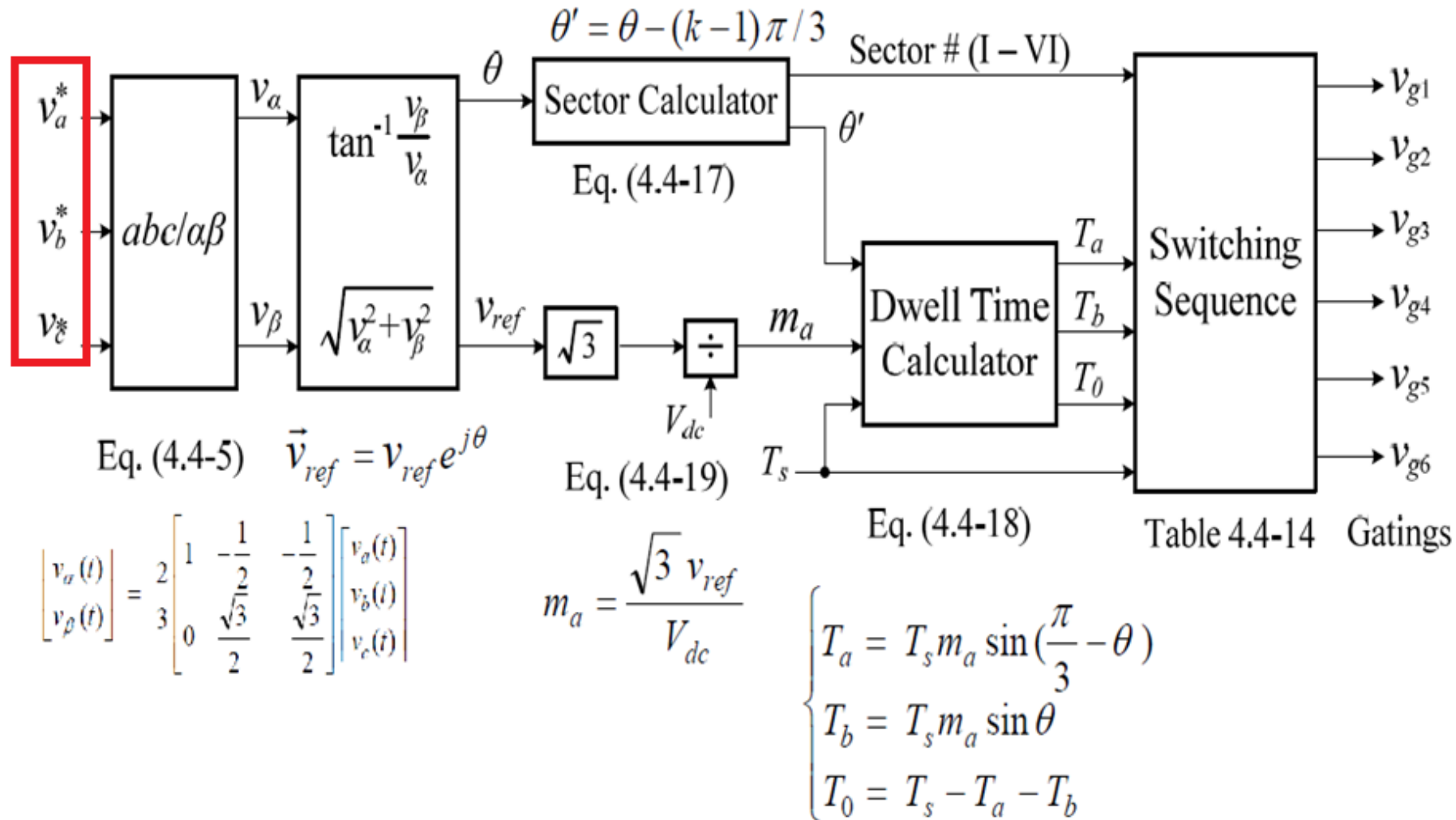Input variables,  $v_a^*$ ,  $v_b^*$  &  $v_c^*$  are 3-phase reference voltages, which are also required output phase voltages of inverter




Sector	Switching Segment						
	1	2	3	4	5	6	7
I	$\vec{V}_0$	$\vec{V}_1$	$\vec{V}_2$	$\vec{V}_0$	$\vec{V}_2$	$\vec{V}_1$	$\vec{V}_0$
	OOO	POO	PPO	PPP	PPO	POO	OOO
II	$\vec{V}_0$	$\vec{V}_3$	$\vec{V}_2$	$\vec{V}_0$	$\vec{V}_2$	$\vec{V}_3$	$\vec{V}_0$
	OOO	OPO	PPO	PPP	PPO	OPO	OOO
III	$\vec{V}_0$	$\vec{V}_3$	$\vec{V}_4$	$\vec{V}_0$	$\vec{V}_4$	$\vec{V}_3$	$\vec{V}_0$
	OOO	OPO	OPP	PPP	OPP	OPO	OOO
IV	$\vec{V}_0$	$\vec{V}_5$	$\vec{V}_4$	$\vec{V}_0$	$\vec{V}_4$	$\vec{V}_5$	$\vec{V}_0$
	OOO	OOP	OPP	PPP	OPP	OOP	OOO
V	$\vec{V}_0$	$\vec{V}_5$	$\vec{V}_6$	$\vec{V}_0$	$\vec{V}_6$	$\vec{V}_5$	$\vec{V}_0$
	OOO	OOP	POP	PPP	POP	OOP	OOO
VI	$\vec{V}_0$	$\vec{V}_1$	$\vec{V}_6$	$\vec{V}_0$	$\vec{V}_6$	$\vec{V}_1$	$\vec{V}_0$
	OOO	POO	POP	PPP	POP	POO	OOO

Reference voltages  $v_a^*$ ,  $v_b^*$  &  $v_c^*$  are normally generated by controller in a wind energy conversion system.

- Through  $abc/\alpha\beta$  transformation, 3-phase reference voltages in  $abc$  stationary frame are transformed into 2-phase variables,  $v_\alpha$  &  $v_\beta$ , in  $\alpha$ - $\beta$  stationary frame,
- from which reference vector for SVM scheme is established:

$$\vec{v}_{ref} = v_{ref} e^{j\theta}$$

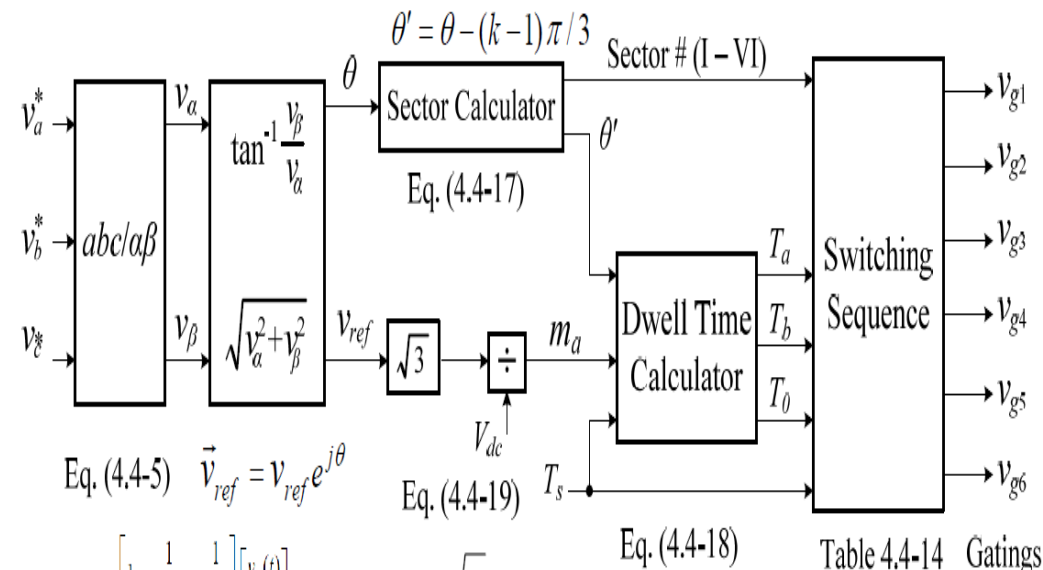

Sector	Switching Segment						
	1	2	3	4	5	6	7
I	$\vec{V}_0$	$\vec{V}_1$	$\vec{V}_2$	$\vec{V}_0$	$\vec{V}_2$	$\vec{V}_1$	$\vec{V}_0$
	OOO	POO	PPO	PPP	PPO	POO	OOO
II	$\vec{V}_0$	$\vec{V}_2$	$\vec{V}_3$	$\vec{V}_0$	$\vec{V}_3$	$\vec{V}_2$	$\vec{V}_0$
	OOO	OPO	PPO	PPP	PPO	OPO	OOO
III	$\vec{V}_0$	$\vec{V}_3$	$\vec{V}_4$	$\vec{V}_0$	$\vec{V}_4$	$\vec{V}_3$	$\vec{V}_0$
	OOO	OPO	OPP	PPP	OPP	OPO	OOO
IV	$\vec{V}_0$	$\vec{V}_4$	$\vec{V}_5$	$\vec{V}_0$	$\vec{V}_5$	$\vec{V}_4$	$\vec{V}_0$
	OOO	OOP	OPP	PPP	OOP	OOP	OOO
V	$\vec{V}_0$	$\vec{V}_5$	$\vec{V}_6$	$\vec{V}_0$	$\vec{V}_6$	$\vec{V}_5$	$\vec{V}_0$
	OOO	OOP	POP	PPP	POP	OOP	OOO
VI	$\vec{V}_0$	$\vec{V}_1$	$\vec{V}_6$	$\vec{V}_0$	$\vec{V}_6$	$\vec{V}_1$	$\vec{V}_0$
	OOO	POO	POP	PPP	POP	POO	OOO

$$\begin{bmatrix} v_\alpha(t) \\ v_\beta(t) \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & \frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} v_a(t) \\ v_b(t) \\ v_c(t) \end{bmatrix}$$


$$m_a = \frac{\sqrt{3} v_{ref}}{V_{dc}}$$

$$\begin{cases} v_{ref} = \sqrt{(v_\alpha)^2 + (v_\beta)^2} \\ \theta = \tan^{-1} \frac{v_\beta}{v_\alpha} \end{cases}$$


$$\begin{cases} T_a = T_s m_a \sin\left(\frac{\pi}{3} - \theta\right) \\ T_b = T_s m_a \sin \theta \\ T_0 = T_s - T_a - T_b \end{cases}$$

With reference vector in place, modulation index  $m_a$  and sector number can be calculated by (4.4-19) and (4.4-17),

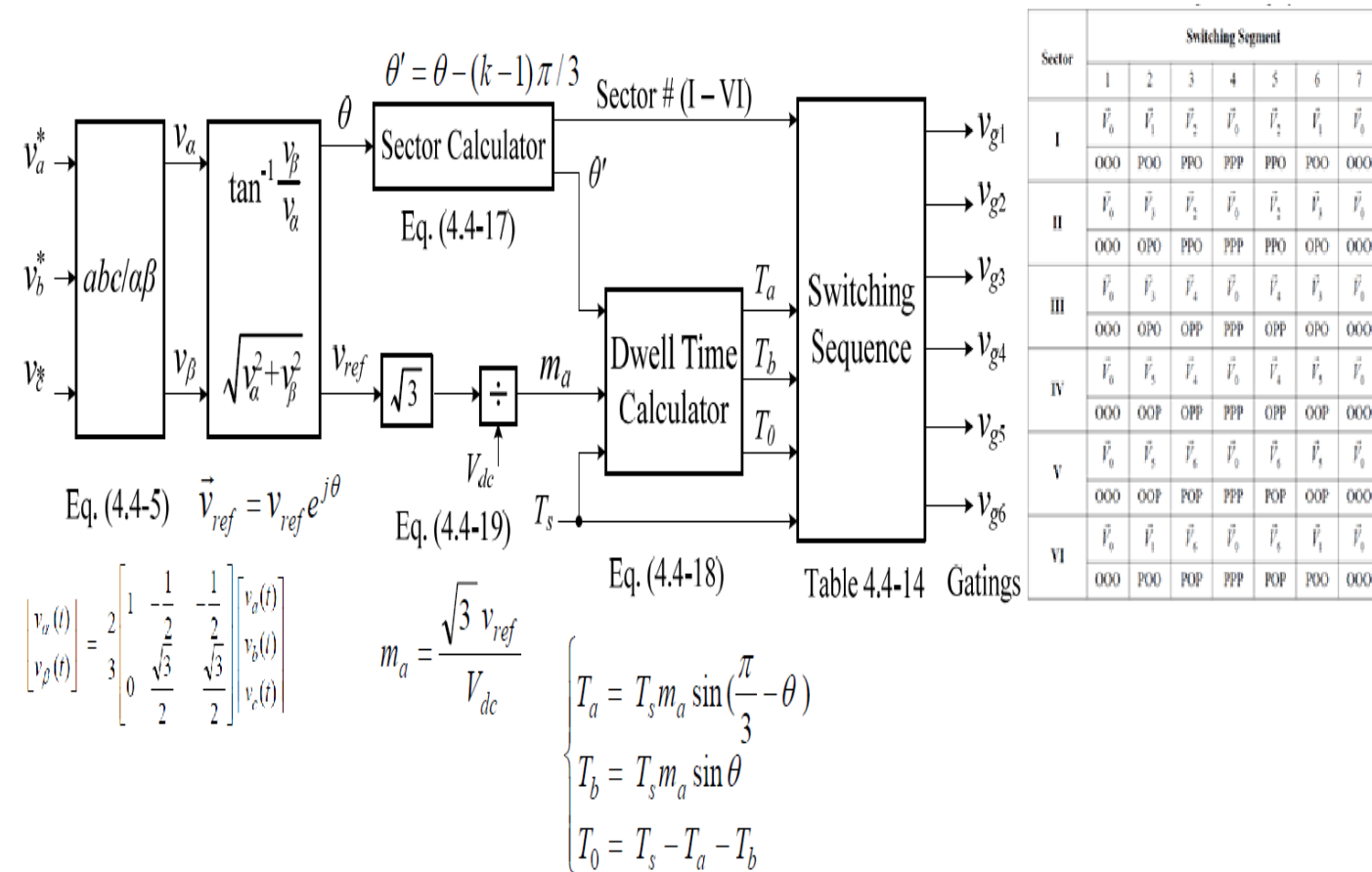- Dwell times can be determined by (4.4-18), and switching sequence can be designed according to Table 4.4-4.
- Finally, gate signals for 6 switches in inverter can be generated.
- With SVM scheme, fundamental frequency and magnitude of inverter output voltages  $v_a$ ,  $v_b$ , and  $v_c$  are equal to those of 3-phase reference voltage  $v_a^*$ ,  $v_b^*$ , and  $v_c^*$



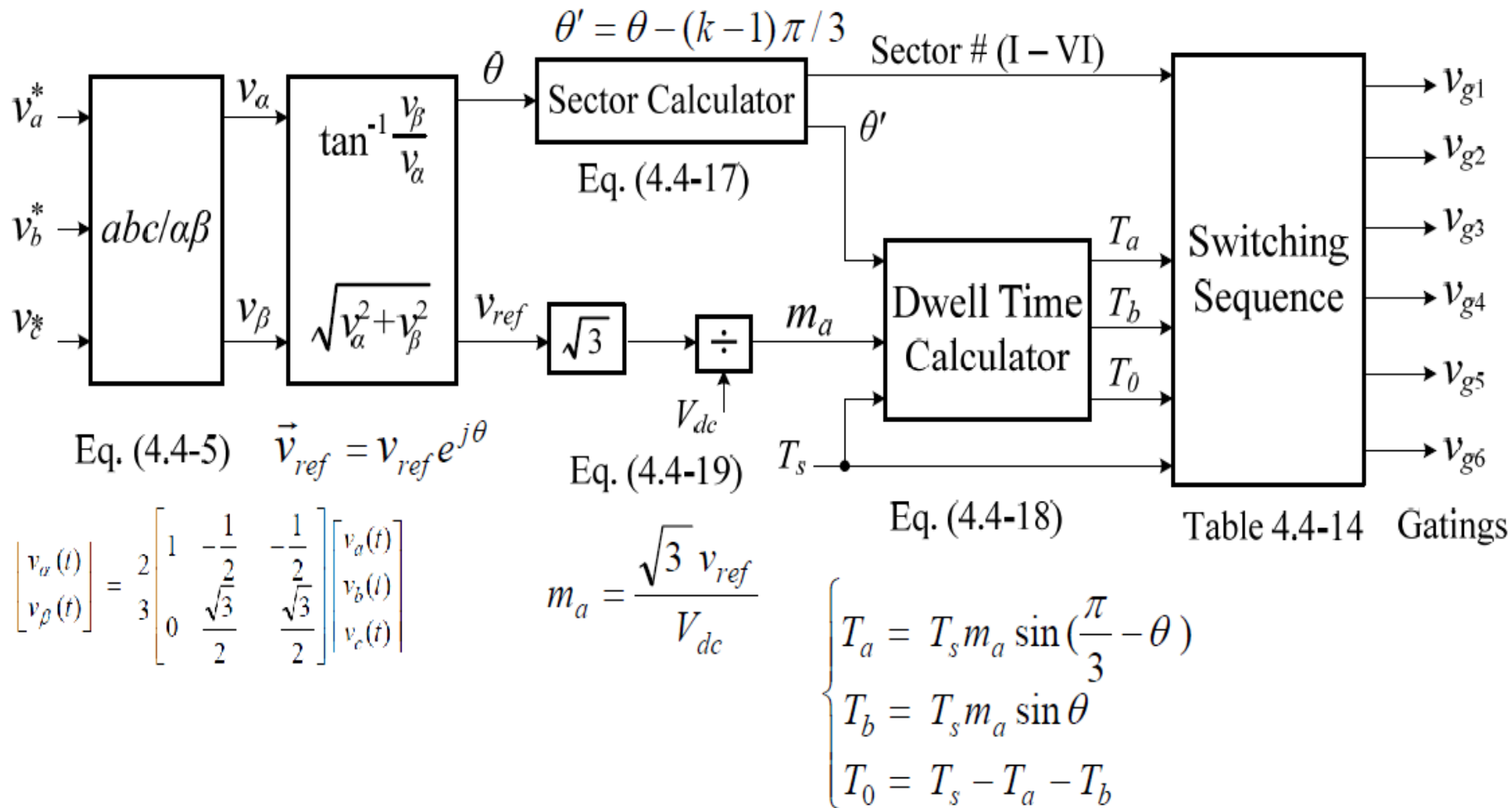As result, inverter output voltage is fully controllable by its references



Sector	Switching Segment						
	1	2	3	4	5	6	7
I	$\bar{V}_0$	$\bar{V}_1$	$\bar{V}_2$	$\bar{V}_0$	$\bar{V}_2$	$\bar{V}_1$	$\bar{V}_0$
	OOO	POO	PPO	PPP	PPO	POO	OOO
II	$\bar{V}_0$	$\bar{V}_3$	$\bar{V}_2$	$\bar{V}_0$	$\bar{V}_2$	$\bar{V}_3$	$\bar{V}_0$
	OOO	OPO	PPO	PPP	PPO	OPO	OOO
III	$\bar{V}_0$	$\bar{V}_3$	$\bar{V}_4$	$\bar{V}_0$	$\bar{V}_4$	$\bar{V}_3$	$\bar{V}_0$
	OOO	OPO	OPP	PPP	OPP	OPO	OOO
IV	$\bar{V}_0$	$\bar{V}_3$	$\bar{V}_4$	$\bar{V}_0$	$\bar{V}_4$	$\bar{V}_5$	$\bar{V}_0$
	OOO	OOP	OPP	PPP	OPP	OOP	OOO
V	$\bar{V}_0$	$\bar{V}_5$	$\bar{V}_6$	$\bar{V}_0$	$\bar{V}_6$	$\bar{V}_5$	$\bar{V}_0$
	OOO	OOP	POP	PPP	POP	OOP	OOO
VI	$\bar{V}_0$	$\bar{V}_1$	$\bar{V}_6$	$\bar{V}_0$	$\bar{V}_6$	$\bar{V}_1$	$\bar{V}_0$
	OOO	POO	POP	PPP	POP	POO	OOO