

# Power converters

## *AC/DC Converters*

*Dr. Tahir Izhar*  
*UET-Lahore*


1

## Single Phase Converters


- The basic rectifier principles are understood from the operation of single phase circuits.
- The emphasis will be on physical understanding not on the detailed analysis.
- First consider a simple half wave rectifier circuit with resistive load.

2

## Half-Wave Rectifier

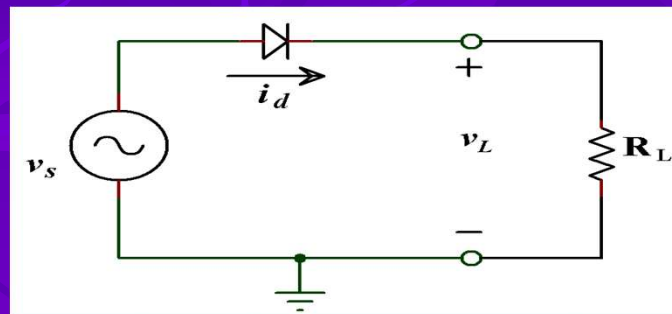

**Resistive Load**

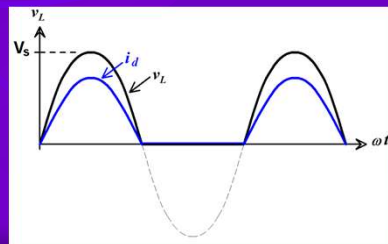

3


## Half-Wave Rectifier

**Resistive Load**


- The load voltage is nearly same as the source voltage during positive half cycle.
- The current is also sinusoidal during positive half cycle.
- During negative half cycle, the diode is reverse biased the load current is zero, source current is zero and the load voltage is also zero.

4

## Half wave Rectifier

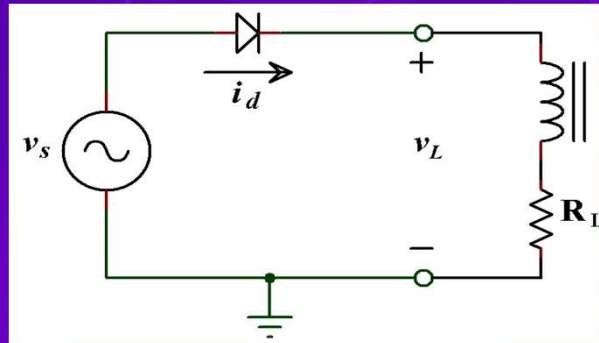

**Inductive Load**

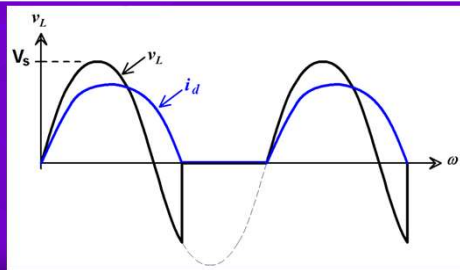

5

## Half wave Rectifier

**Inductive Load**



- For inductive load, the current will keep on flowing even if the source voltage is negative.
- This is due to the stored energy in the inductor.
- When the source voltage reverses its polarity, the inductor becomes a source and the polarity of this source is so that it will keep the current flowing in the same direction.
- When the stored energy is released the diode current will be reduced to zero and the diode is reverse biased.
- During a part of the negative cycle, the load voltage will follow the source voltage.

6

# Half wave Rectifier
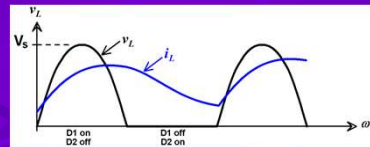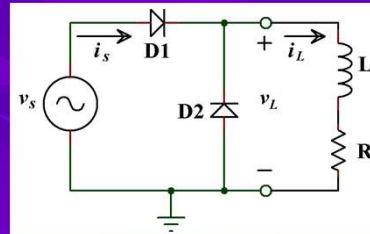
## Inductive Load with Freewheeling Diode



- The addition of diode  $D_2$  permits the load current to be continuous and prevents  $v_L$  from going negative.
- When  $D_1$  is off,  $D_2$  allows the energy in the circuit to maintain continuity by providing a path through which the inductor current can free wheel.
- Diode  $D_2$  is known as free-wheel diode, by-pass, fly-back, catch diode or commutation diode.



7

# Half wave Rectifier
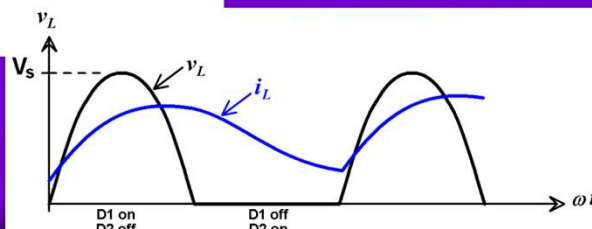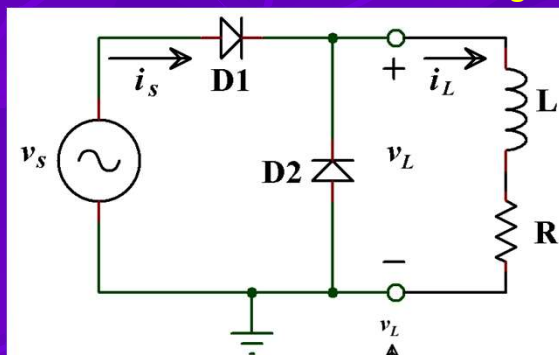
## Inductive Load with Freewheeling Diode



# Half wave Rectifier

## Inductive Load with Freewheeling Diode


- The addition of diode  $D_2$  permits the load current to be continuous and prevents  $v_L$  from going negative.
- When  $D_1$  is off,  $D_2$  allows the energy in the circuit to maintain continuity by providing a path through which the inductor current can free wheel.
- Diode  $D_2$  is known as free-wheel diode, by-pass, fly-back, catch diode or commutation diode.

9



# Half wave Rectifier
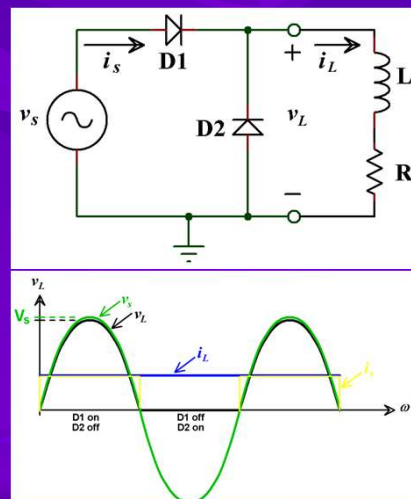
## Highly Inductive Load with Freewheeling Diode

- If we assume that the inductor is very large approaching infinity, the load current will become constant without any fluctuations.
- The Green line shows  $v_s$ , Black is the load voltage, blue is the load current and yellow is the source current.
- It can be observed that the source current is unidirectional step waveform.



## 1-Φ Bridge Rectifier

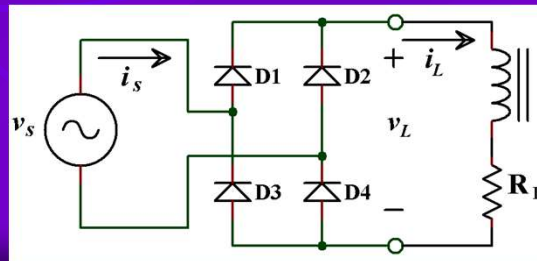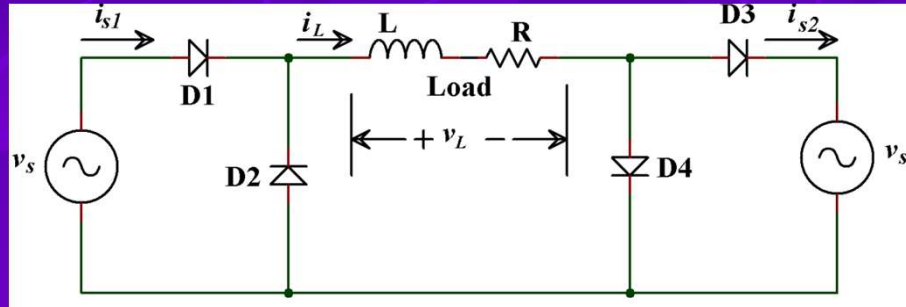



11

## 1-Φ Bridge Rectifier

- AC source current contain no DC component.
- For same AC source voltage, the full wave rectifier produces an average output voltage twice that of the half-wave circuit with free-wheeling diode.
- The half-wave rectifier with free wheeling diode serves as the basic building block for the bridge circuit and in this context the circuit is sometimes called a half-bridge.

12

## 1-Φ Bridge Rectifier

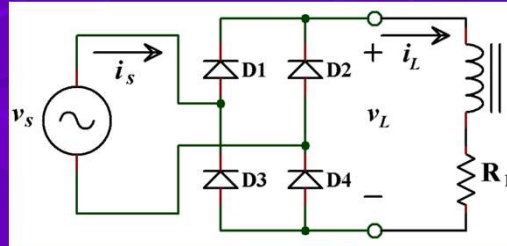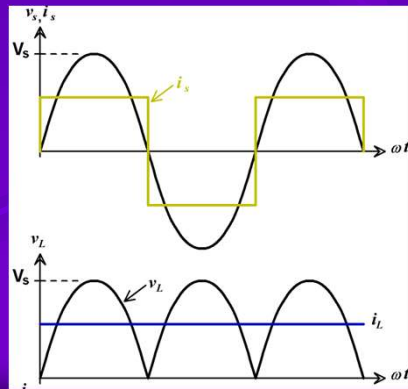

13

## 1-Φ Bridge Rectifier

- The source currents  $i_{s1}$  and  $i_{s2}$  contain DC components, however, the total source current for the full-bridge circuit does not contain any DC components.
- The reason is that the source current in the bridge is sum of the two source currents, which have DC components of equal magnitude but of opposite polarity.
- As the load is highly inductive, the load current  $i_L$  is constant.

14

## 1-Φ Bridge Rectifier

- During positive half cycle,  $i_L$  is supplied by D1 and D4, therefore,  $i_s = i_L$ .
- During negative half cycle,  $i_L$  is supplied by D2 and D3, therefore,  $i_s = -i_L$ .
- Therefore the source current will have a square wave shape with zero DC component.

15

## Analysis of 1-Φ Converter

### Power Transfer From Mains

Consider that a Single Phase Bridge rectifier is connected to the mains supply and it draws a non-sinusoidal current from the mains.

The average or mean output Voltage is

$$V_{mean} = \frac{1}{\pi} \int_0^{\pi} V_s \sin \omega t d\omega t \quad (1)$$

$$V_{mean} = \frac{2V_s}{\pi} \quad (2)$$

The average load current is

$$I_L = \frac{V_{mean}}{R} = \frac{2V_s}{\pi R} \quad (3)$$

16



# Analysis of 1-Φ Converter

## Power Transfer From Mains

The average load Power is

$$P_{av} = V_{mean} I_L \quad (4)$$

$$= \frac{2V_s}{\pi} \frac{2V_s}{\pi R} = \frac{4V_s^2}{\pi^2 R} \quad (5)$$

Since  $V_s = \sqrt{2}V_{rms}$

$$P_{av} = \frac{8V_{rms}^2}{\pi^2 R} \quad (6)$$

17

# Analysis of 1-Φ Converter

## Power Transfer From Mains

Since the AC current is a simple square wave, it has the well known spectrum of odd harmonics with amplitude inversely proportional to the order.

$$I_n = \frac{4I_L}{n\pi} \quad (7)$$

For n=1,3,5...

18

# Analysis of 1-Φ Converter

We also know that in case of non-sinusoidal mains current, only the fundamental component of current contributes towards average power.

$$P_{av} = V_{mean} I_{1rms} \quad (8)$$

Peak value of fundamental current is

$$I_1 = \frac{4I_L}{\pi} = \frac{4 \times 2 \times V_s}{\pi \times \pi \times R} = \frac{8V}{\pi^2 R} = \frac{8V_{rms} \times \sqrt{2}}{\pi^2 R}$$

$$I_{1rms} = \frac{I_1}{\sqrt{2}} = \frac{8V_{rms}}{\pi^2 R} \quad (9)$$

Therefore

$$P_{av} = \frac{8V_{rms}^2}{\pi^2 R} \quad (10)$$

Note that the results obtained in equations (6) and (10) is same

19