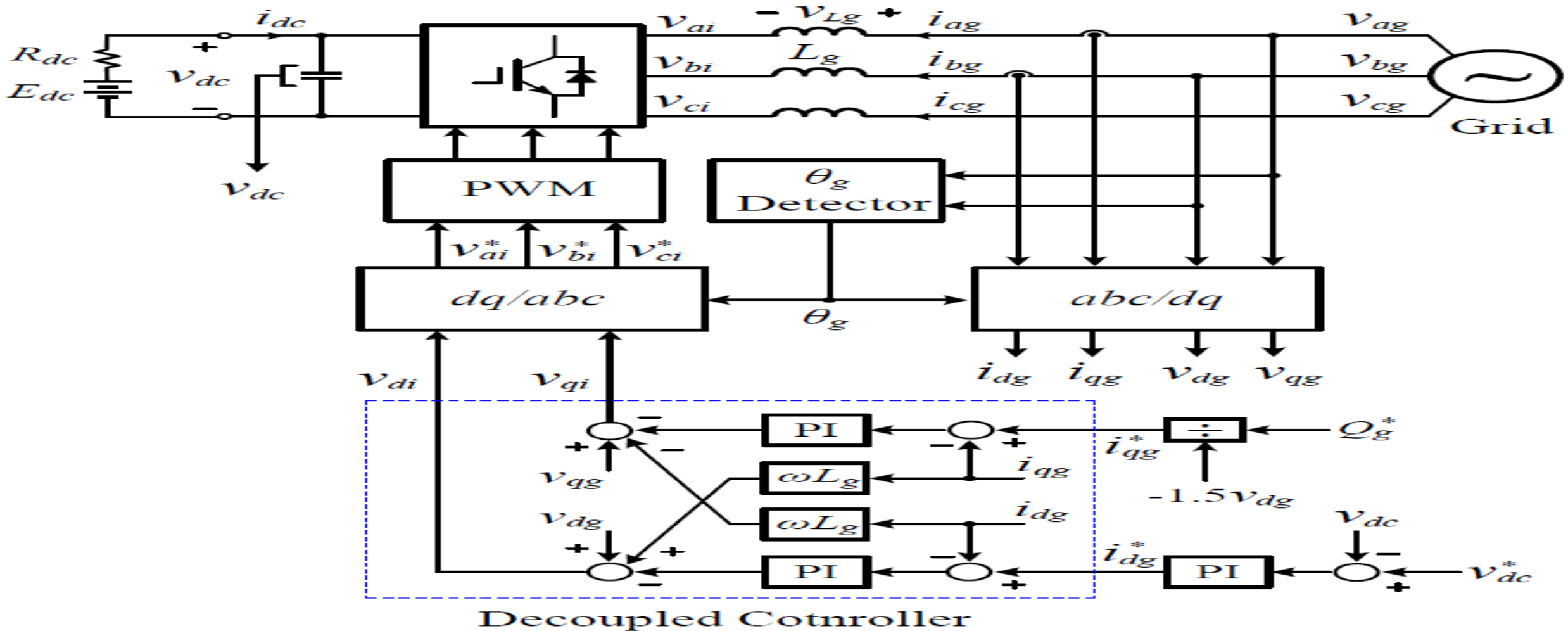


Lecture#


Numericals

- Topic: Control of Grid-Connected Converters

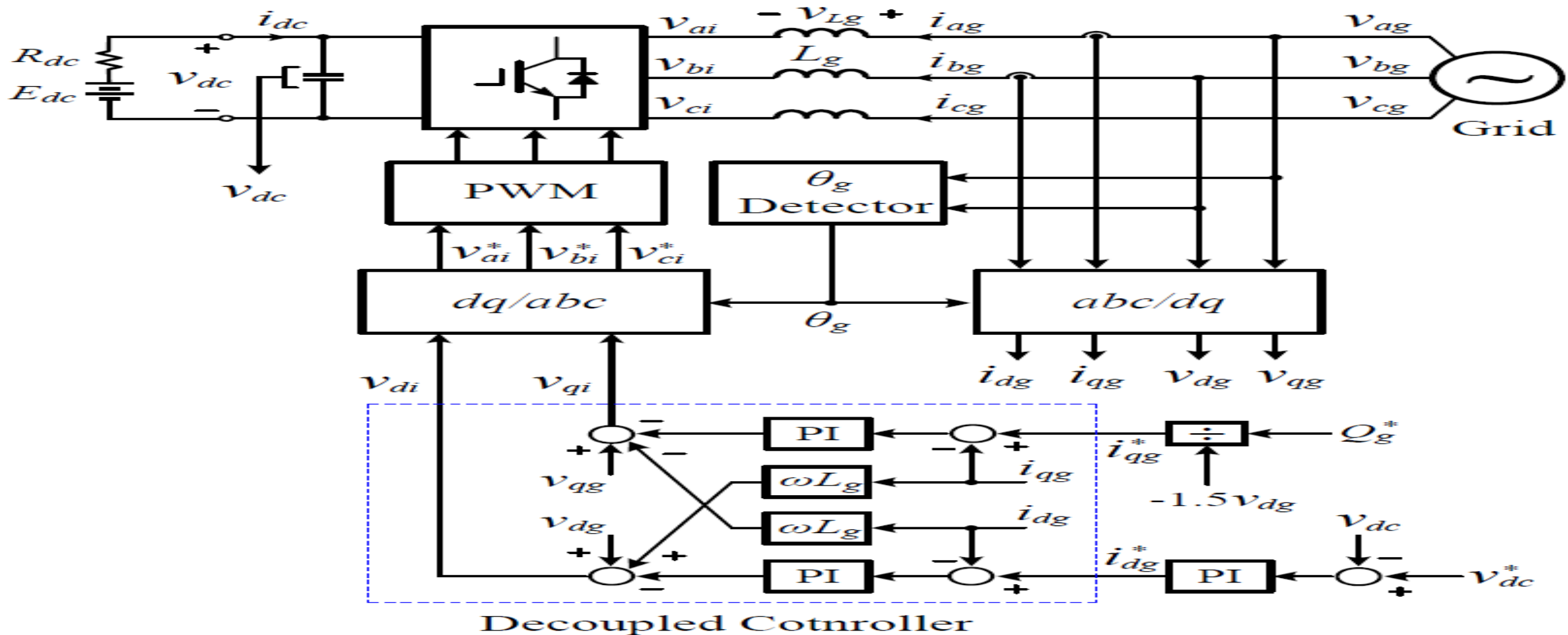
4-17 (Solved Problem.PP.272) Consider a grid-connected 2-level voltage source inverter with voltage oriented control (VOC) shown in Fig.




Inverter is connected to grid of 690V/50Hz & delivers 2.3MW to grid with unity power factor operation. Here $V_{abi1}=690\text{v}$ is rms value of fundamental-frequency component of inverter line to line voltage.



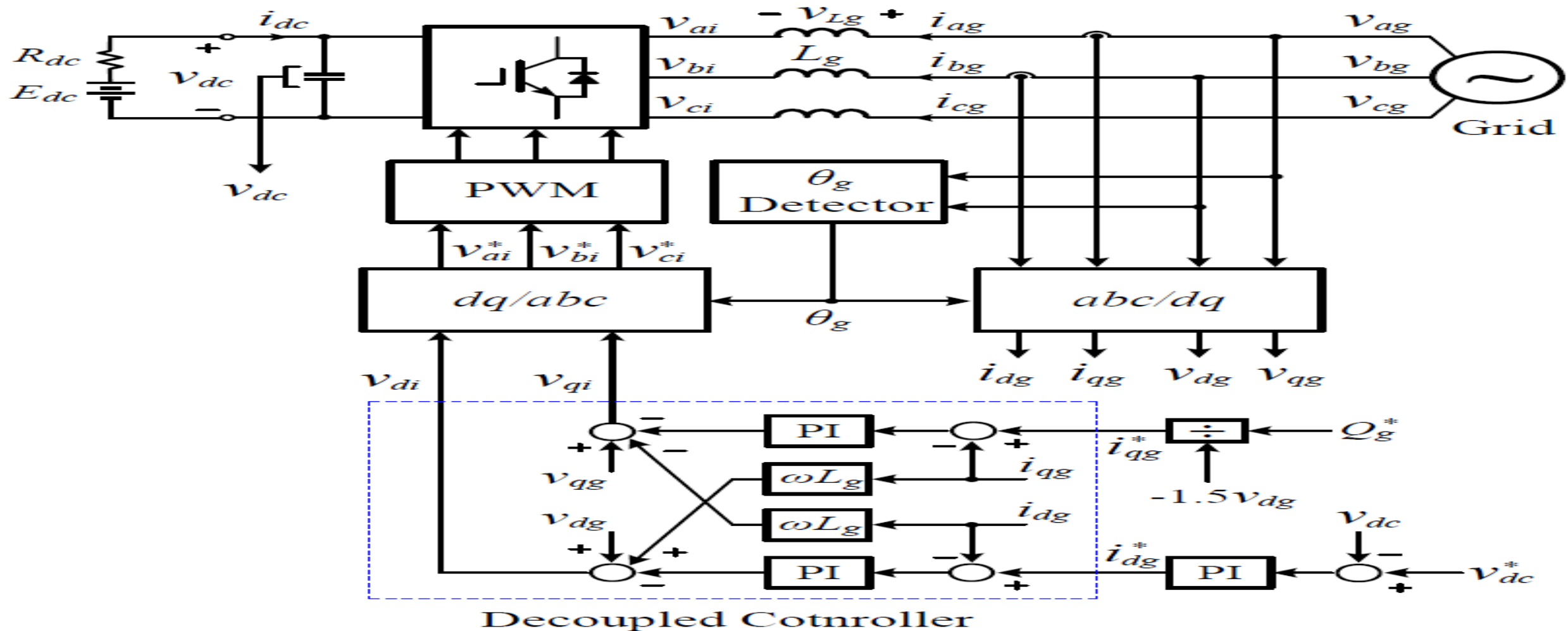Inverter is modulated by SVM scheme with modulation index of 0.8 & operates under steady state conditions. Line inductance L_g is 0.1098 mH.



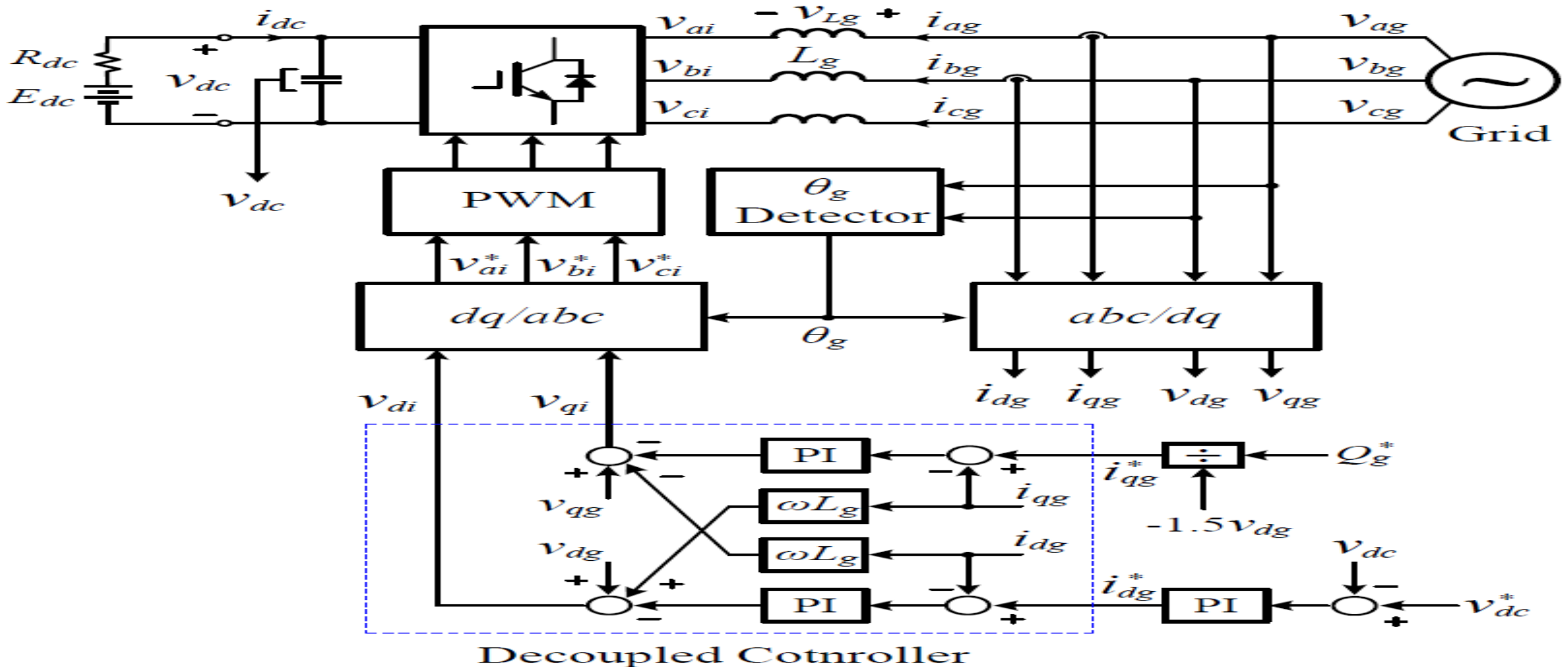- To simplify analysis, all harmonics produced by inverter are neglected. When grid voltage vector angle ϑ_g is -45° .



Determine following:

- a) instantaneous 3-phase grid voltages & currents,
- b) grid voltage angle,
- c) dq -axis grid voltages & currents,
- d) active & reactive powers delivered to grid (using dq -axis grid voltages & currents),
- e) dc-link voltage & current, and
- f) dq -axis & 3-phase reference voltages for PWM modulator.


a) Grid voltage, current and frequency:

$$v_g = \frac{690}{\sqrt{3}} \times \sqrt{2} = 563.38 \text{ V (peak)}$$

$$P_g = \frac{3}{2} v_g i_g$$

$$i_g = \frac{2P_g}{3v_g} = \frac{2 \times 2.3 \times 10^6}{3 \times 563.38} = 2721.6 \text{ A (peak)}$$

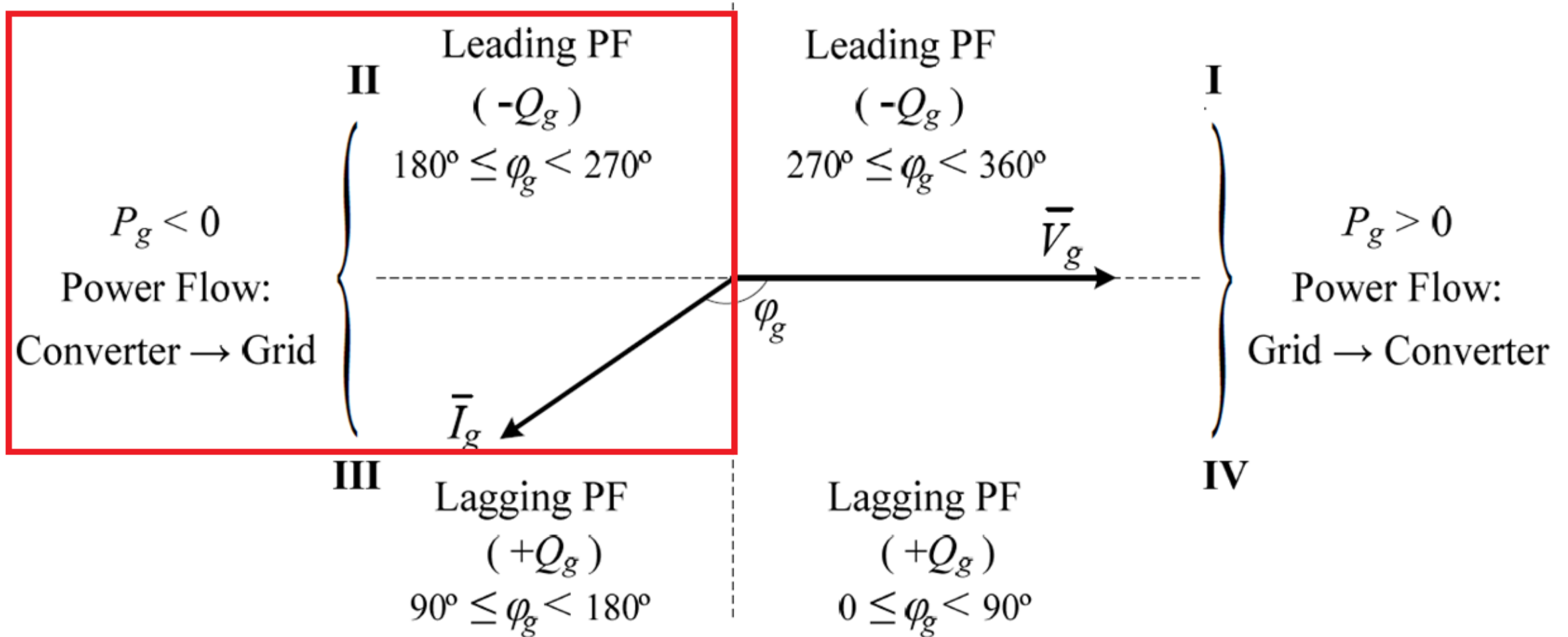
As inverter delivers 2.3MW to grid with unity power factor operation so $\varphi_g = 180^\circ = \pi \text{ rad}$ (generating mode)



$$\omega_g = 2\pi \times 50 = 314.16 \text{ rad/sec} .$$

$$\text{At } \theta_g = -45^\circ, \omega_g t = \theta_g = -\pi / 4 \text{ rad}$$
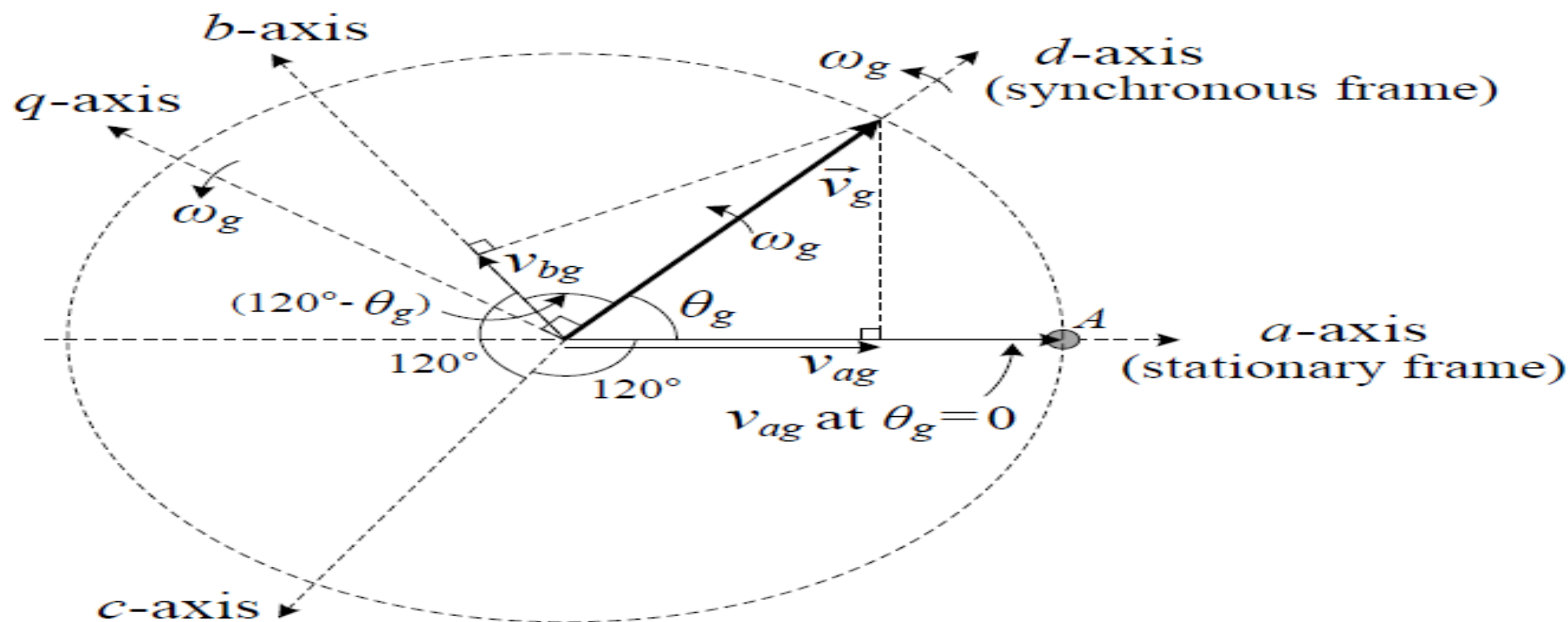
$$\begin{cases} v_{ag} = v_g \cos \theta_g = v_g \cos \omega_g t \\ v_{bg} = v_g \cos(\theta_g - 120^\circ) = v_g \cos(\omega_g t - 120^\circ) \\ v_{cg} = v_g \cos(\theta_g + 120^\circ) = v_g \cos(\omega_g t + 120^\circ) \end{cases}$$



Instantaneous 3-phase grid voltages:

$$\begin{cases} v_{ag} = v_g \cos \omega_g t = 563.38 \times \cos(-\pi / 4) = 398.37 \text{ V (peak)} \\ v_{bg} = v_g \cos(\omega_g t - 2\pi / 3) = 563.38 \times \cos(-\pi / 4 - 2\pi / 3) = -544.19 \text{ V (peak)} \\ v_{cg} = v_g \cos(\omega_g t + 2\pi / 3) = 563.38 \times \cos(-\pi / 4 + 2\pi / 3) = 145.81 \text{ V (peak)} \end{cases}$$

Instantaneous 3-phase grid currents:

$$\begin{cases} i_{ag} = i_g \cos(\omega_g t - \varphi_g) = 2721.6 \times \cos(-\pi / 4 - \pi) = -1924.5 \text{ A (peak)} \\ i_{bg} = i_g \cos(\omega_g t - \varphi_g - 2\pi / 3) = 2721.6 \times \cos(-\pi / 4 - \pi - 2\pi / 3) = 2628.9 \text{ A (peak)} \\ i_{cg} = i_g \cos(\omega_g t - \varphi_g + 2\pi / 3) = 2721.6 \times \cos(-\pi / 4 - \pi + 2\pi / 3) = -704.42 \text{ A (peak)} \end{cases}$$

b) The α - β components of 3-phase grid voltages:

$$\begin{bmatrix} v_{\alpha} \\ v_{\beta} \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -1/2 & -1/2 \\ 0 & \sqrt{3}/2 & -\sqrt{3}/2 \end{bmatrix} \begin{bmatrix} v_{ag} \\ v_{bg} \\ v_{cg} \end{bmatrix}$$

from which

$$v_{\alpha} = v_{ag} = 398.37 \text{ V (peak)}$$


$$v_{\beta} = \frac{\sqrt{3}}{3} (v_{ag} + 2v_{bg}) = \frac{\sqrt{3}}{3} (398.37 + 2 \times -544.19) = -398.37 \text{ V (peak)}$$

Verify the grid voltage vector angle:

$$\theta_g = \tan^{-1} \frac{v_{\beta}}{v_{\alpha}} = \tan^{-1} \frac{-398.37}{398.37} = -\pi / 4 \text{ rad}$$

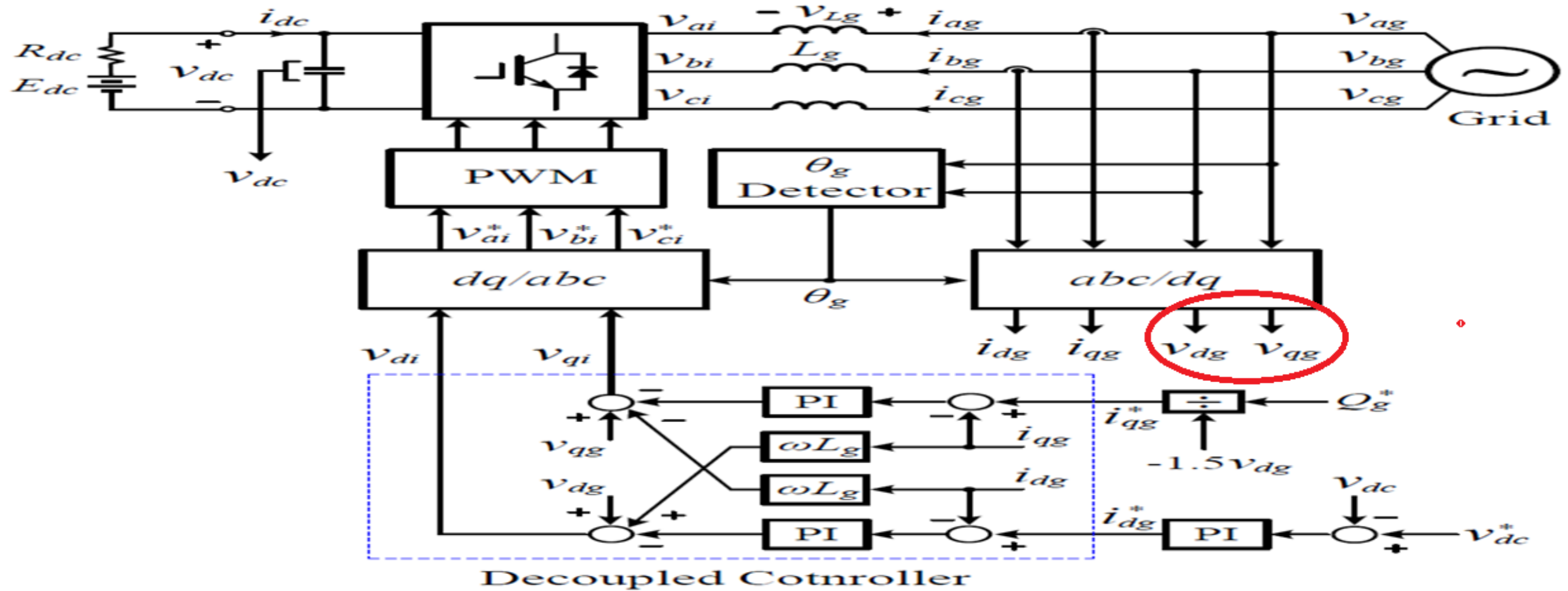c) The dq/abc transformation with voltage oriented control is given by

$$\begin{bmatrix} V_{dg} \\ V_{qg} \end{bmatrix} = \frac{2}{3} \begin{bmatrix} \cos \theta_g & \cos(\theta_g - 2\pi/3) & \cos(\theta_g - 4\pi/3) \\ -\sin \theta_g & -\sin(\theta_g - 2\pi/3) & -\sin(\theta_g - 4\pi/3) \end{bmatrix} \cdot \begin{bmatrix} V_{ag} \\ V_{bg} \\ V_{cg} \end{bmatrix}$$



from which, dq -axis grid voltages can be calculated by

$$\begin{aligned}v_{dg} &= \frac{2}{3} \left(v_{ag} \cos \theta_g + v_{bg} \cos(\theta_g - 2\pi/3) + v_{cg} \cos(\theta_g - 4\pi/3) \right) \\&= \frac{2}{3} \left(398.37 \times \cos(-\pi/4) - 544.19 \times \cos(-\pi/4 - 2\pi/3) + 145.81 \times \cos(-\pi/4 - 4\pi/3) \right) \\&= 563.38 \text{ V (peak)}\end{aligned}$$

$$\begin{aligned}v_{qg} &= -\frac{2}{3} \left(v_{ag} \sin \theta_g + v_{bg} \sin(\theta_g - 2\pi/3) + v_{cg} \sin(\theta_g - 4\pi/3) \right) \\&= -\frac{2}{3} \left(398.37 \times \sin(-\pi/4) - 544.19 \times \sin(-\pi/4 - 2\pi/3) + 145.81 \times \sin(-\pi/4 - 4\pi/3) \right) \\&= 0 \text{ V}\end{aligned}$$

The dq -axis grid currents can be found in a similar way,

$$\begin{aligned} i_{dg} = i_{dg}^* &= \frac{2}{3} (i_{ag} \cos \theta_g + i_{bg} \cos(\theta_g - 2\pi/3) + i_{cg} \cos(\theta_g - 4\pi/3)) \\ &= \frac{2}{3} (-1924.5 \times \cos(-\pi/4) - 2628.9 \times \cos(-\pi/4 - 2\pi/3) - 704.42 \times \cos(-\pi/4 - 4\pi/3)) \\ &= -2721.65 \text{ A (peak)} \end{aligned}$$

$$\begin{aligned} i_{qg} = i_{qg}^* &= -\frac{2}{3} (i_{ag} \sin \theta_g + i_{bg} \sin(\theta_g - 2\pi/3) + i_{cg} \sin(\theta_g - 4\pi/3)) \\ &= -\frac{2}{3} (-1924.5 \times \sin(-\pi/4) - 2628.9 \times \sin(-\pi/4 - 2\pi/3) - 704.42 \times \sin(-\pi/4 - 4\pi/3)) \\ &= 0 \text{ A (peak)} \end{aligned}$$

d) Active & reactive powers delivered to grid:

$$\begin{cases} P_g = \frac{3}{2}(v_{dg}i_{dg} + v_{qg}i_{qg}) = \frac{3}{2}(563.38 \times -2721.6 + 0) = -2300 \times 10^3 \text{ W } (-1.0 \text{ pu}) \\ Q_g = \frac{3}{2}(v_{qg}i_{dg} - v_{dg}i_{qg}) = -\frac{3}{2}(0 - 0) = 0 \text{ VAR} \end{cases}$$

e) The dc-link voltage and current: with modulation index m_a is 0.8, leaving 20% margin for adjustments.

$$V_{dc} = \frac{\sqrt{2}V_{abi1}}{m_a} = \frac{\sqrt{2} \times 690}{0.8} = 1220 \text{ V}$$

$V_{abi1}=690\text{v}$ is rms value of fundamental-frequency component of inverter line to line voltage

Dc-link current:

$$I_{dc} = \frac{P_g}{V_{dc}} = \frac{-2300 \times 10^3}{1220} = -1885.6 \text{ A}$$

f) the dq -axis reference voltages for the PWM modulator:

$$\begin{cases} v_{di} = -(k_1 + k_2 / S)(i_{dg}^* - i_{dg}) + \omega_g L_g i_{qg} + v_{dg} \\ v_{qi} = -(k_1 + k_2 / S)(i_{qg}^* - i_{qg}) - \omega_g L_g i_{dg} + v_{qg} \end{cases}$$

In steady-state $i_{dg}^* = i_{dg}$ and $i_{qg}^* = i_{qg}$, thus

$$\begin{cases} v_{di} = \omega_g L_g i_{qg} + v_{dg} = 0 + 563.38 = 563.38 \text{ V (peak)} \\ v_{qi} = -\omega_g L_g i_{dg} + v_{qg} = -314.16 \times 0.1098 \times 10^{-3} \times -2721.65 + 0 = 93.88 \text{ V (peak)} \end{cases}$$

Note: Though the q -axis grid voltage v_{qg} is zero, its reference v_{qi} is not zero because of the $-\omega_g L_g i_{dg}$ term used in the decoupled controller.

3-phase reference voltages for PWM modulator can be obtained by dq/abc transformation:

$$\begin{bmatrix} x_{ai} \\ x_{bi} \\ x_{ci} \end{bmatrix} = \begin{bmatrix} \cos \theta_g & -\sin \theta_g \\ \cos(\theta_g - 2\pi/3) & -\sin(\theta_g - 2\pi/3) \\ \cos(\theta_g - 4\pi/3) & -\sin(\theta_g - 4\pi/3) \end{bmatrix} \cdot \begin{bmatrix} x_{di} \\ x_{qi} \end{bmatrix}$$

from which

$$\begin{aligned} v_{ai}^* &= v_{di} \cos \theta_g - v_{qi} \sin \theta_g \\ &= 563.38 \times \cos(-\pi/4) - 93.88 \times \sin(-\pi/4) = 464.76 \text{ V (peak)} \end{aligned}$$

$$\begin{aligned} v_{bi}^* &= v_{di} \cos(\theta_g - 2\pi/3) - v_{qi} \sin(\theta_g - 2\pi/3) \\ &= 563.38 \times \cos(-\pi/4 - 2\pi/3) - 93.88 \times \sin(-\pi/4 - 2\pi/3) = -519.89 \text{ V (peak)} \end{aligned}$$

$$\begin{aligned} v_{ci}^* &= v_{di} \cos(\theta_g - 4\pi/3) - v_{qi} \sin(\theta_g - 4\pi/3) \\ &= 563.38 \times \cos(-\pi/4 - 4\pi/3) - 93.88 \times \sin(-\pi/4 - 4\pi/3) = 55.13 \text{ V (peak)} \end{aligned}$$

Cross Check:

$$P_g = 3V_g I_g \cos \varphi_g = 3 \times \frac{690}{\sqrt{3}} \times 1924.5 \times \cos(180^\circ) = -2300 \times 10^3 \text{ W}$$

$$Q_g = 3V_g I_g \sin \varphi_g = 3 \times \frac{690}{\sqrt{3}} \times 1924.5 \times \sin(180^\circ) = 0 \text{ VAR}$$

Answers:

a) $i_g = 1360.8 \text{ A}$, $\varphi_g = 154.16^\circ$ (2.691 rad), $v_{ag} = -563.38 \text{ V}$

$$v_{bg} = 281.69 \text{ V}, \quad v_{cg} = 281.69 \text{ V}, \quad i_{ag} = -1224.7 \text{ A}, \quad i_{bg} = -98.67 \text{ A}, \quad i_{cg} = -1126.1 \text{ A}$$

b) $v_\alpha = -563.38 \text{ V}$, $v_\beta = 0 \text{ V}$, $\theta_g = -180^\circ$ ($-\pi$ rad)

c) $v_{dg} = 563.38 \text{ V}$, $v_{qg} = 0 \text{ V}$, $i_{dg} = -1224.7 \text{ A}$, $i_{qg} = -593.171 \text{ A}$

d) $P_g = -1035 \times 10^3 \text{ W}$ (-0.45 pu), $Q_g = 501.27 \times 10^3 \text{ VAR}$ (0.2179 pu)

e) $V_{dc} = 1220 \text{ V}$, $I_{dc} = -848.53 \text{ A}$


f) $v_{di} = 542.92 \text{ V}$, $v_{qi} = 42.25 \text{ V}$, $v_{ai}^* = -542.92 \text{ V}$, $v_{bi}^* = 234.87 \text{ V}$, $v_{ci}^* = 308.05 \text{ V}$

4-18 Repeat Problem 4-17 if the grid-side power factor is 0.8 leading. Perform calculations when grid voltage vector angle $\vartheta_g = 90^\circ$.

As inverter delivers 2.3MW to grid with 0.8 leading power factor operation so $\cos(216.87) = -0.8$

$$\varphi_g = 216.87^\circ \text{ (3.785 rad)}$$

(generating mode)

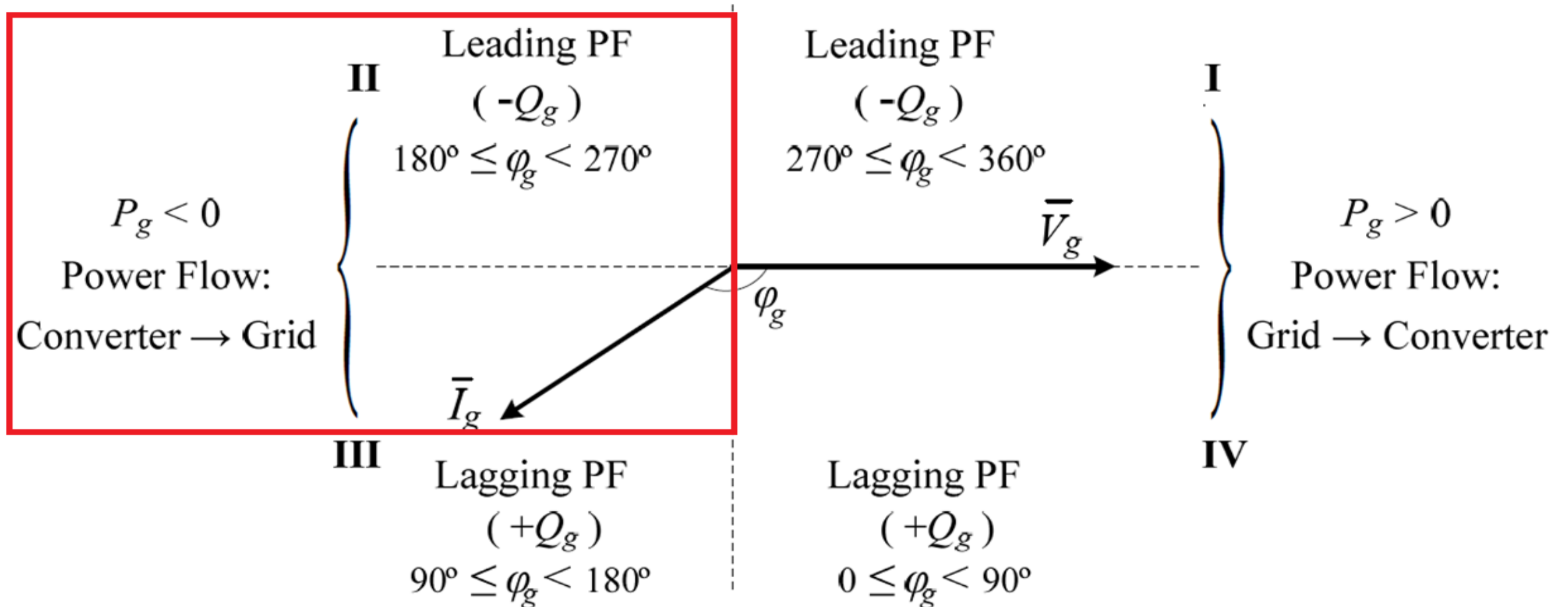

a) Grid voltage, current and frequency:

$$v_g = \frac{690}{\sqrt{3}} \times \sqrt{2} = 563.38 \text{ V (peak)}$$

$$P_g = \frac{3}{2} v_g i_g$$

$$i_g = \frac{2P_g}{3v_g} = \frac{2 \times 2.3 \times 10^6}{3 \times 563.38} = 2721.6 \text{ A (peak)}$$

$$\omega_g = 2\pi \times 50 = 314.16 \text{ rad/sec}$$

At $\omega_g t = \theta_g = 90^\circ \quad (\pi / 2 \text{ rad})$

Instantaneous 3-phase grid voltages:

$$\begin{cases} v_{ag} = v_g \cos \omega_g t \\ v_{bg} = v_g \cos(\omega_g t - 2\pi / 3) \\ v_{cg} = v_g \cos(\omega_g t + 2\pi / 3) \end{cases}$$

$$\omega_g t = \theta_g = 90^\circ \quad (\pi / 2 \text{ rad})$$

$$v_g = 563.38 \text{ V (peak)}$$

$$\begin{cases} i_{ag} = i_g \cos(\omega_g t - \varphi_g) \\ i_{bg} = i_g \cos(\omega_g t - \varphi_g - 2\pi / 3) \\ i_{cg} = i_g \cos(\omega_g t - \varphi_g + 2\pi / 3) \end{cases}$$

$$i_{ag} = -1633 \text{ A}, \quad i_{bg} = -1069.1 \text{ A}, \quad i_{cg} = 2702.1 \text{ A}$$

Answers:

a) $\varphi_g = 216.87^\circ$ (3.785 rad), $v_{ag} = 0$ V, $v_{bg} = 487.9$ V, $v_{cg} = -487.9$ V

$$i_{ag} = -1633 \text{ A}, \quad i_{bg} = -1069.1 \text{ A}, \quad i_{cg} = 2702.1 \text{ A}$$

b) $v_\alpha = 0$ V, $v_\beta = 562.38$ V, $\theta_g = 90^\circ$ ($\pi / 2$ rad)

c) $v_{dg} = 563.38$ V, $v_{qg} = 0$ V, $i_{dg} = -2177.3$ A, $i_{qg} = 1633$ A

d) $P_g = -1840 \times 10^3$ W (-0.8 pu), $Q_g = -1380 \times 10^3$ VAR (-0.6 pu)

e) $V_{dc} = 1220$ V, $I_{dc} = -1508.5$ A


f) $v_{di} = 619.71$ V, $v_{qi} = 75.11$ V, $v_{ai}^* = -75.11$ V, $v_{bi}^* = 574.24$ V, $v_{ci}^* = -499.13$ V

4-19 Repeat Problem 4-17 if grid-side power factor is 0.9 lagging & inverter delivers 50% of rated power to grid. Perform calculations when grid voltage vector angle $\vartheta_g = 180^\circ$.

As inverter delivers 2.3MW to grid with 0.9 lagging power factor operation so $\cos(154.16) = -0.9$

$$\varphi_g = 154.16^\circ \quad (2.691 \text{ rad})$$

(generating mode)

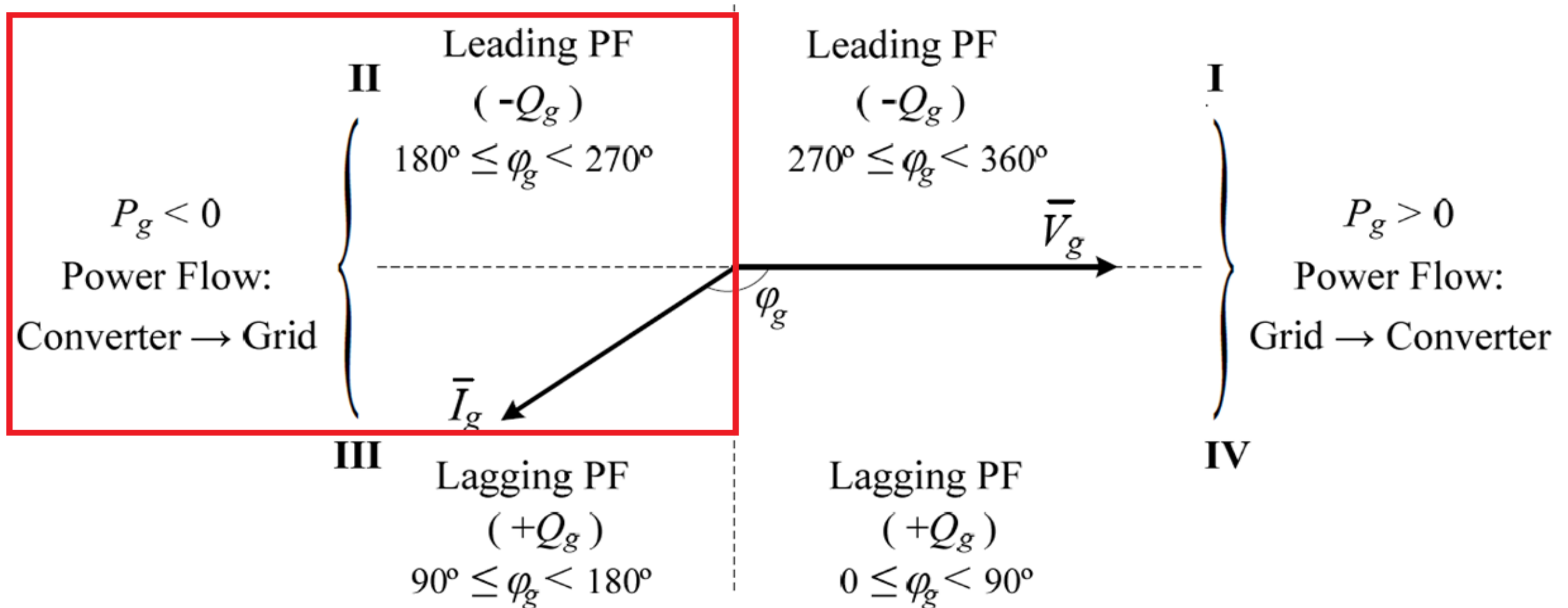

Answers:

a) $i_g = 1360.8 \text{ A}$, $\varphi_g = 154.16^\circ$ (2.691 rad), $v_{ag} = -563.38 \text{ V}$

$v_{bg} = 281.69 \text{ V}$, $v_{cg} = 281.69 \text{ V}$, $i_{ag} = -1224.7 \text{ A}$, $i_{bg} = -98.67 \text{ A}$, $i_{cg} = -1126.1 \text{ A}$

b) $v_\alpha = -563.38 \text{ V}$, $v_\beta = 0 \text{ V}$, $\theta_g = -180^\circ$ ($-\pi$ rad)

c) $v_{dg} = 563.38 \text{ V}$, $v_{qg} = 0 \text{ V}$, $i_{dg} = -1224.7 \text{ A}$, $i_{qg} = -593.171 \text{ A}$

d) $P_g = -1035 \times 10^3 \text{ W}$ (-0.45 pu), $Q_g = 501.27 \times 10^3 \text{ VAR}$ (0.2179 pu)

e) $V_{dc} = 1220 \text{ V}$, $I_{dc} = -848.53 \text{ A}$

f) $v_{di} = 542.92 \text{ V}$, $v_{qi} = 42.25 \text{ V}$, $v_{ai}^* = -542.92 \text{ V}$, $v_{bi}^* = 234.87 \text{ V}$, $v_{ci}^* = 308.05 \text{ V}$