

Home assignment

Obtain slip at maximum torque $s_{T\max}$ by setting $dT_m / ds = 0$?

$$T_m = \frac{1}{\omega_s / P} \times \frac{3V_s^2}{(R_s + R_r / s + R_{eq} / s)^2 + (X_{ls} + X_{lr} + X_{eq} / s)^2} \times \frac{R_r + R_{eq}}{s}$$

$$s_{T\max} = \pm \sqrt{\frac{(R_r + R_{eq})^2 + X_{eq}^2}{R_s^2 + (X_{ls} + X_{lr})^2}}$$

8-4 (Solved Problem) Consider a 1.0MW/575V/60Hz/2160rpm DFIG WECS. The parameters of the generator are given in Table B-6 of Appendix B. Generator operates with an MPPT scheme & its stator power factor is unity. At a given wind & generator speed, equivalent resistance R_{eq} & reactance X_{eq} for rotor side converter & maximum torque to mechanical torque ratio T_{max}/T_m are found to be 0.03778Ω , 0.02165Ω & 4.4123 respectively.

Calculate following:

- a) maximum torque & corresponding slip,
- b) generator mechanical torque & power,
- c) rotor mechanical & electrical speeds & slip,
- d) rms stator current &
- e) rms rotor current and voltage.

Generator Type	DFIG, 1.0MW/575V/60Hz	
Rated Mechanical Power	1.0 MW	1.0 pu
Rated Stator Line-to-line Voltage	575 V (rms)	
Rated Stator Phase Voltage	331.98 V (rms)	1.0 pu
Rated Rotor Phase Voltage	67.97 V (rms)	0.2047 pu
Rated Stator Current	829.2 A (rms)	0.8258 pu
Rated Rotor Current	882.2 A (rms)	0.8786 pu
Rated Stator Frequency	60 Hz	1.0 pu
Rated Rotor Speed	2160 rpm	1.0 pu
Nominal Rotor Speed Range	1350–2160 rpm	0.625–1.0pu
Rated Slip	-0.2	
Number of Pole Pairs	2	
Rated Mechanical Torque	4.421 kN.m	1.0 pu
Stator Winding Resistance R_s	3.654 m Ω	0.0111 pu
Rotor Winding Resistance R_r	3.569 m Ω	0.0108 pu
Stator Leakage Inductance L_{ls}	0.1304 mH	0.1487 pu
Rotor Leakage Inductance L_{lr}	0.1198 mH	0.1366 pu
Magnetizing Inductance L_m	4.12 mH	4.6978 pu
Base Current $I_B = 1\text{MW}/(\sqrt{3} \times 575\text{V})$	1004.1 A (rms)	1.0 pu
Base Flux Linkage λ_B	0.8806 Wb (rms)	1.0 pu
Base Impedance Z_B	0.3306 Ω	1.0 pu
Base Inductance L_B	0.877 mH	1.0 pu
Base Capacitance C_B	8022.93 μF	1.0 pu

Solution:

- a) +ve values for $R_{eq} = 0.03778\Omega$ & $X_{eq} = 0.02165\Omega$ indicate super-synchronous mode of operation.
- -ve values indicate sub-synchronous operation.
 - 0 value for X_{eq} indicate synchronous operation.

Slip at which the maximum torque occurs can be obtained

Stator Leakage Inductance L_{ls}	0.1304 mH
Rotor Leakage Inductance L_{lr}	0.1198 mH

$$R_{eq} = 0.03778\Omega \text{ \& } X_{eq} = 0.02165\Omega$$

$$s_{T \max} = \pm \sqrt{\frac{(R_r + R_{eq})^2 + X_{eq}^2}{R_s^2 + (X_{ls} + X_{lr})^2}} = -0.4944$$

($s = +0.4944$ is omitted because of the super - synchronous mode of operation)

The maximum torque:

$$T_{\max} = \frac{1}{2\omega_s / P} \times \frac{3V_s^2}{R_s + \frac{(X_{ls} + X_{lr})X_{eq}}{R_r + R_{eq}} - \sqrt{\left((X_{ls} + X_{lr})^2 + R_s^2\right) \times \left(1 + \frac{X_{eq}^2}{(R_r + R_{eq})^2}\right)}} = -16391 \text{ N.m} \quad (3.708 \text{ pu})$$

b) The generator mechanical torque:

$$T_{\max}/T_m = 4.4124\Omega$$

$$T_{\max} = -16391 \text{ N.m}$$

$$T_m = \frac{T_{\max}}{T_{\max}/T_m} = \frac{-16391}{4.4124} = -3714.8 \text{ N.m}$$

Generator mechanical torque can be related to pu rotor speed as

$$T_m = T_{m,R} \times (\omega_{m,pu})^2 \text{ N.m}$$

From which pu rotor speed can be calculated by

$$\omega_{m,pu} = \sqrt{\frac{T_m}{T_{m,R}}}$$

$$T_m = -3714.8 \text{ N.m}$$

Rated Mechanical Torque=4.421kN.m

$$\omega_{m,pu} = \sqrt{\frac{-3714.8}{-4421}} = 0.9167$$

Rated mechanical power:

Rated Mechanical Torque=4.421kN.m

$$P_{m,R} = \omega_{m,R} \times T_{m,R} = 2160(2\pi) / 60 \times (-4421) = -1000 \times 10^3 \text{ W}$$

Generator mechanical power at 0.91667 pu rotor speed:

$$P_m = P_{m,R} \times (\omega_{m,\text{pu}})^3 = -1000 \times 10^3 \times (0.9167)^3 = -770.26 \times 10^3 \text{ W}$$

c) Rotor mechanical & electrical speeds:

$$\omega_m = \omega_{m,R} \times \omega_{m,pu} = 2160(2\pi)/60 \times 0.9167 = 207.35 \text{ rad/sec} \quad (1980 \text{ rpm})$$

$$\omega_r = \omega_m \times P = 207.35 \times 2 = 414.7 \text{ rad/sec}$$

The slip can be obtained as:


$$s = (\omega_s - \omega_r) / \omega_s = (376.99 - 414.7) / 376.99 = -0.1$$

d) The stator current:


$$I_s = \frac{V_s \pm \sqrt{V_s^2 - \frac{4R_s T_m \omega_s}{3P}}}{2R_s} = -697.74 \text{ A (rms)} \quad (I_s = 91.55 \times 10^3 \text{ A omitted})$$

where $V_s = 575/\sqrt{3}$ V, $T_m = -3714.8$ N.m, $\omega_s = 376.99$ rad/sec, $R_s = 3.654$ m Ω and $P = 2$

e) Find I_r ?

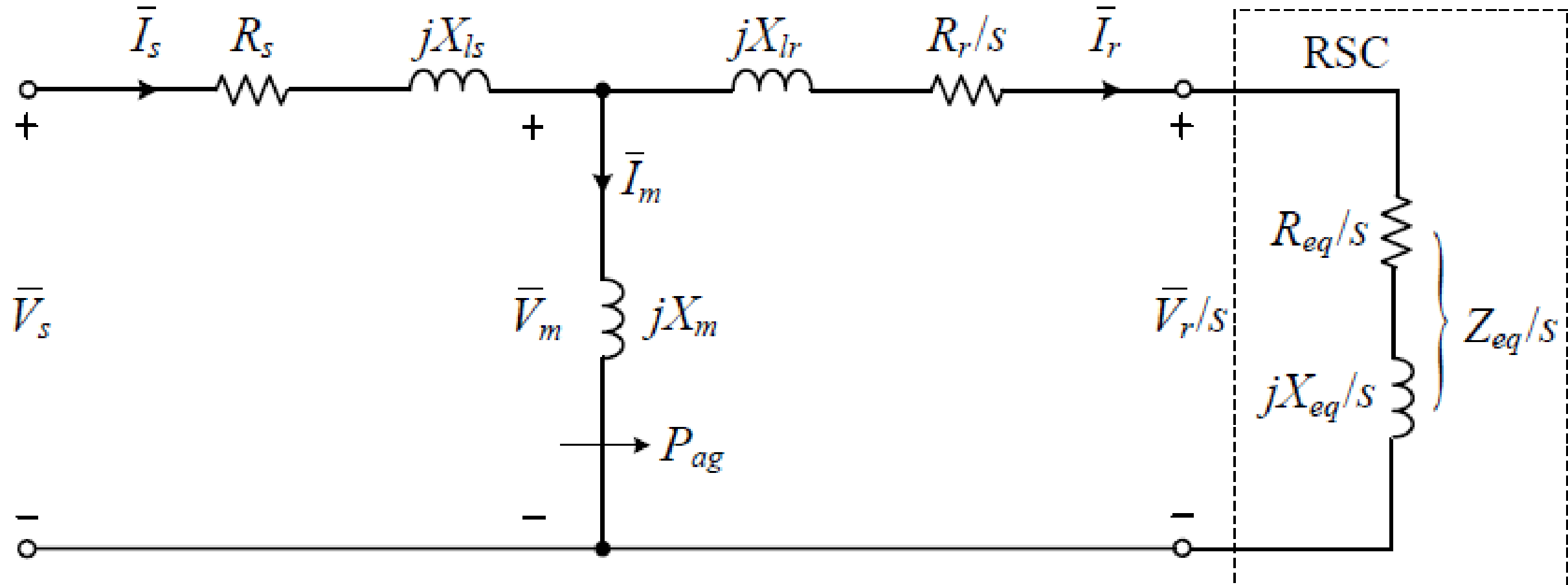

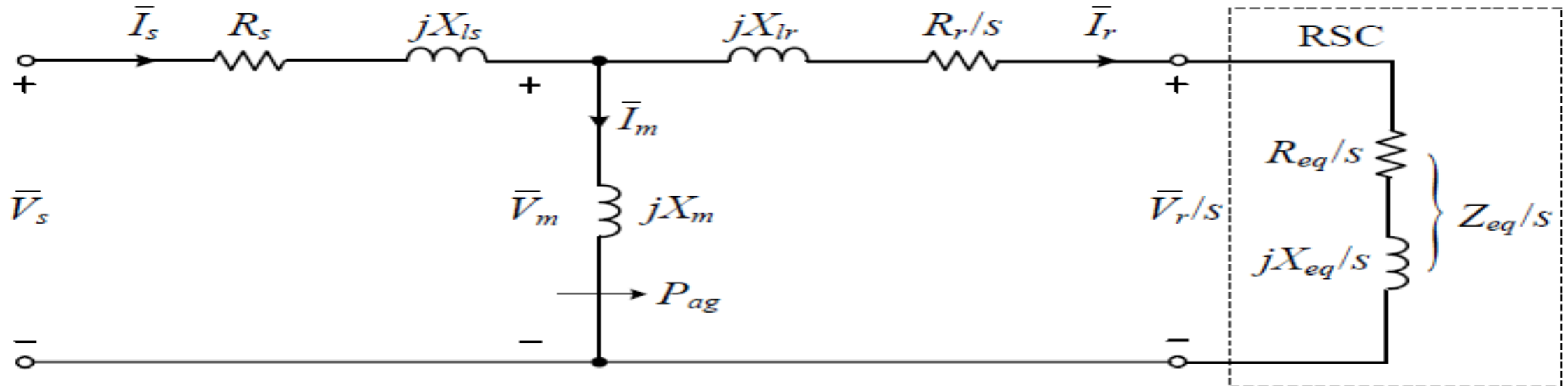e) Rotor current(I_r) can be calculated by



$$\bar{I}_r = \frac{jX_m \bar{I}_s}{jX_m + \left(\frac{R_r}{s} + jX_{lr} \right) + \left(\frac{R_{eq}}{s} + j \frac{X_{eq}}{s} \right)} = 751.35 \angle 163.34^\circ \text{ A (rms)}$$

Alternatively, rms rotor current can be found from mechanical torque equation:

$$T_m = \frac{1}{\omega_s / P} \times 3 I_r^2 (R_{eq} + R_r) / s \quad \text{N.m}$$

From above

$$I_r = \sqrt{\frac{T_m \times (\omega_s / P)}{3(R_{eq} + R_r) / s}} = 751.35 \quad \text{A (rms)}$$

Equivalent impedance for the rotor side converter:

$$\bar{Z}_{eq} = \bar{V}_r / \bar{I}_r = 0.0378 + j0.02165 = 0.04354 \angle 29.82^\circ \Omega \text{ (given)}$$

The rotor voltage can be obtained f $\bar{Z}_{eq} = \bar{V}_r / \bar{I}_r$

$$\bar{V}_r = \bar{Z}_{eq} \times \bar{I}_r = 32.72 \angle -166.84^\circ \text{ V (rms)}$$

Cross Check:

$$T_m = \frac{1}{\omega_s / P} \times 3I_r^2 (R_{eq} + R_r) / s = \frac{1}{2\pi \times 60 / 2} \times 3 \times 751.35^2 (0.0378 + 3.569 \times 10^{-3}) / (-0.1) = -3714.87 \text{ N.m, verified.}$$

$$P_m = 3I_r^2 (R_{eq} + R_r) (1-s) / s = 3 \times 751.35^2 (0.0378 + 3.569 \times 10^{-3}) (1 + 0.1) / (-0.1) = -770.26 \times 10^3 \text{ W, verified.}$$

8-5 Repeat Problem 8-4 if the R_{eq} , X_{eq} and T_{\max}/T_m are -0.0295Ω , -0.0150Ω and 6.227, respectively.

Answers:

- a) $s_{T_{\max}} = 0.3175$, $T_{\max} = -17254 \text{ N.m}$ (3.903 pu) b) $T_m = -2770.8 \text{ N.m}$, $P_m = -496.18 \times 10^3 \text{ W}$
- c) $\omega_m = 179.07 \text{ rad/sec}$ (1710 rpm), $\omega_r = 358.14 \text{ rad/sec}$, $s = 0.05$ d) $I_s = -521.43 \text{ A (rms)}$
- e) $\bar{I}_r = 579.9 \angle 158.22^\circ \text{ A (rms)}$, $\bar{V}_r = 19.18 \angle 5.17^\circ \text{ V (rms)}$

8-6 Repeat Problem 8-4 if the R_{eq} , X_{eq} & T_{\max}/T_m are -0.0937Ω , -0.05887Ω & 8.322 , respectively.

Answers:

a) $s_{T_{\max}} = 1.14$, $T_{\max} = -18459 \text{ N.m}$ (4.1754 pu) b) $T_m = -2218 \text{ N.m}$, $P_m = -355.4 \times 10^3 \text{ W}$

c) $\omega_m = 160.22 \text{ rad/sec}$ (1530 rpm), $\omega_r = 320.44 \text{ rad/sec}$, $s = 0.15$ d) $I_s = -417.9 \text{ A (rms)}$

e) $\bar{I}_r = 481.64 \angle 153.5^\circ \text{ A (rms)}$, $\bar{V}_r = 53.28 \angle 5.64^\circ \text{ V (rms)}$